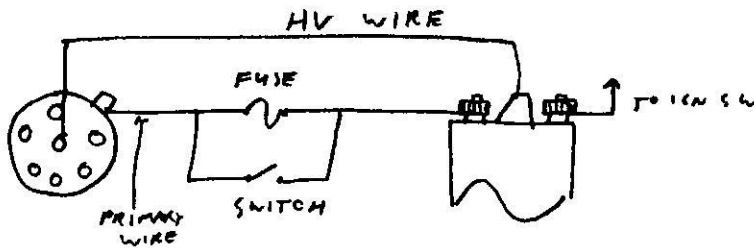


# SIMPLEST ANTI THEFT DEVICE



SWITCH IS NORMALLY CLOSED  
DEVICE IS ARMED WITH SWITCH OPEN.

1. THIEF STARTS CAR
2. AFTER 10 SEC CAR STALLS
3. ABANDONS CAR AS NON-WORKING.

FOR A V-8  $1\frac{1}{4}$  A SLO-BLO IS ADEQUATE

MAKE SURE YOU CARRY SPARE FUSES.

---

WILL NOT WORK ON CARS WITHOUT A  
DISTRIBUTOR