

A WIRELESS IDLE TACHOMETER FOR AUTO TUNE-UPS

*Eliminate risk of damage to
electronic ignition systems*

BY JOHN E. DAVIS

PERFORMING your own automobile tune-ups can be a source of personal satisfaction as well as a way to save money, but if you own a late-model car with electronic ignition, you'll find that the process is not what it used to be. Many modern ignition systems are magnetically triggered and have no points to adjust, thus relegating dwell meters to museums. However, the anti-pollution devices on modern engines have made idle speed considerably more critical than it once was, so an idle tachometer is still required. Since some of these systems can be severely damaged by momentarily grounding the tachometer tie-in point, the problem is where and how to connect the tach without damaging the ignition module.


The best way would be to avoid electrical interconnection with the ignition system entirely, and you can achieve this by building the Wireless Idle Tachometer described here. The tachometer is designed to operate with any four-, six- or eight-cylinder, four-cycle engine having spark ignition. It can be used with two-cycle engines, but the meter indications will be twice the actual engine speed.

Idle tachometers generally indicate from 0 to 1000 rpm. However, partly

for ease of calibration it was decided to extend the range of the tachometer described here to 2000 rpm.

Circuit Operation. The tachometer circuit (Fig. 1) uses a two-transistor monostable as a frequency-to-current converter. The input signal is radiated from the ignition system and picked up on a small telescoping (portable radio-type) antenna nearby; the output is displayed on a meter.

Under quiescent conditions, $Q1$ is off and $Q2$ is on. Since the collector of $Q2$ is low, there is not enough voltage to forward-bias series-connected diodes $D3$ and $D4$ and produce a current flow through $R10$, $R11$, and $M1$.

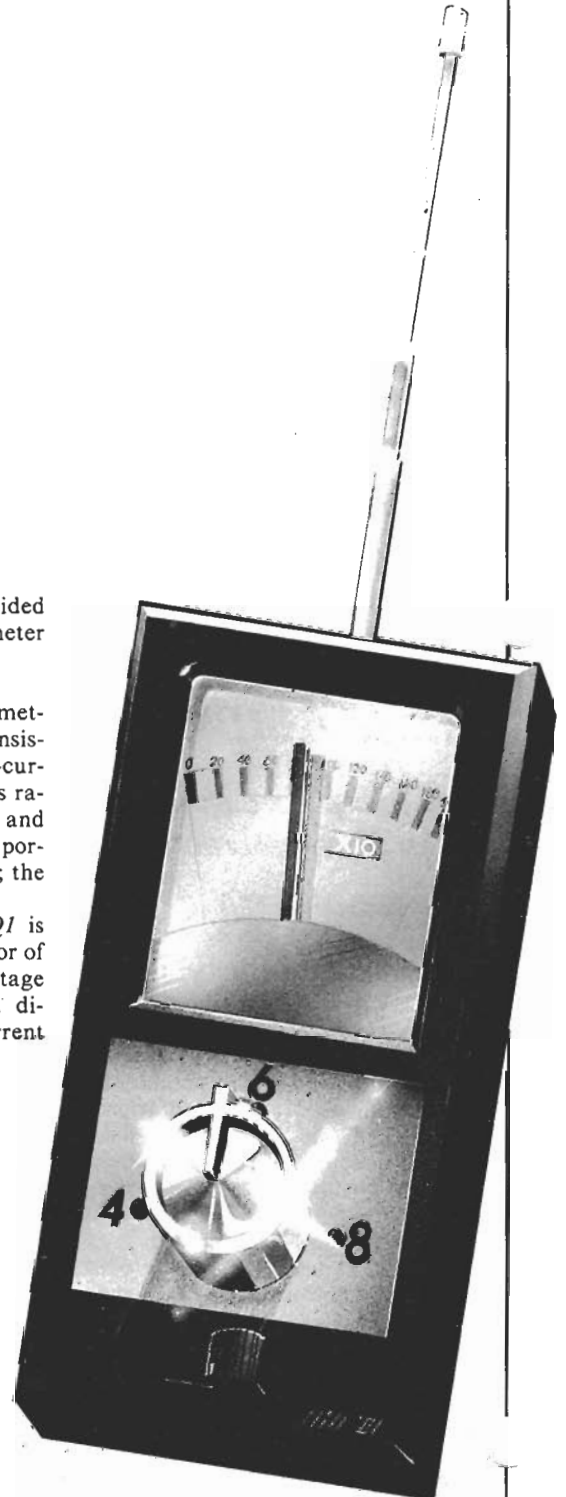

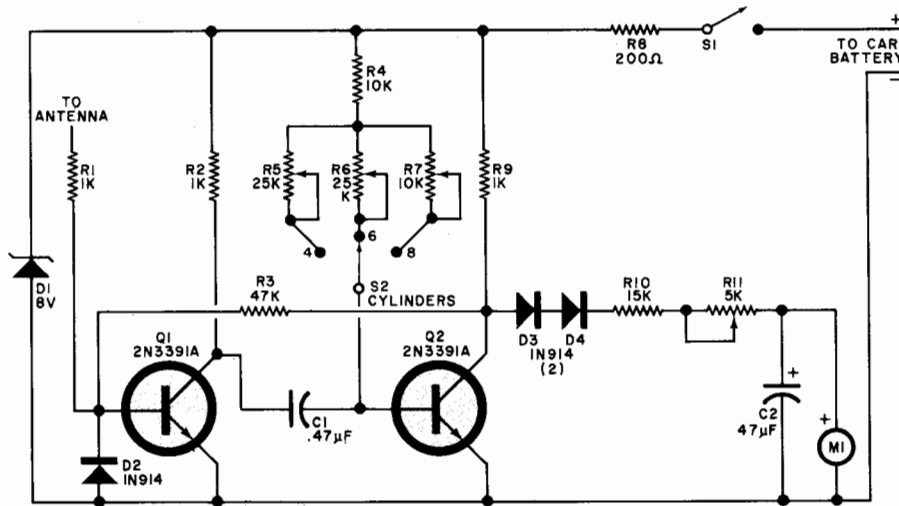


Fig. 1. The tachometer uses a two-transistor monostable circuit as a frequency-to-current converter.

PARTS LIST

- C1—0.47- μ F capacitor
- C2—47- μ F electrolytic
- D1—8-V, 1-W zener diode
- D2,D3,D4—Silicon diode (1N914 or similar)
- M1—200- μ A meter
- Q1,Q2—2N3391A transistor
- R1,R2,R9—1-k Ω , 1/2-W resistor

- R3—47-k Ω , 1/2-W resistor
- R4—10-k Ω , 1/2-W resistor
- R5,R6—25-k Ω , mini-pc potentiometer (Radio Shack #271-336 or similar)
- R7—10-k Ω mini-pc potentiometer (Radio Shack #271-335 or similar)
- R8—200- Ω , 2-W resistor

- R10—15-k Ω , 1/2-W resistor
- R11—5-k Ω linear-taper potentiometer
- S1—Spst toggle switch
- S2—Three-position rotary switch
- Misc.—Telescoping portable radio antenna, suitable plastic enclosure, two-conductor power cable, battery connector, etc.

When the antenna picks up a positive-going ignition signal, Q1 turns on and forces Q2 to turn off for an interval determined by the time-constant of C1 and the resistance selected by switch S2. The choice of time constant sets the tach for 4-, 6-, or 8-cylinder engines.

When turned off, the collector of Q2 rises to deliver a constant-voltage, constant-duration pulse to the meter network. Meter M1 will indicate the current flow. When each positive-going ignition pulse finishes, Q1 returns to its cutoff state, and Q2 reverts to its conducting state. This stops generation of the meter pulses. As the ignition system rapidly cycles on and off, the two-transistor circuit will follow, and the meter needle will flutter. This is prevented by C2 which smooths the current pulses.

Potentiometer R11 provides means to compensate for errors due to ambient temperature variations. For example, if the ambient temperature is 20°F different from the temperature at which the tachometer was calibrated, an error of about 25 rpm will be found. If you are not overly concerned about temperature variations, use a fixed 2,200 ohms for R11.

Resistor R8, in conjunction with zener diode D1, maintains a constant 8 volts for the circuit. Switch S1 is the on/off switch. Diode D2 protects Q1

from negative spikes, while R3 provides the necessary feedback.

Construction and Calibration. Circuit layout is not critical and the builder may use point-to-point wiring on perf board or the

printed circuit board shown in Fig. 2. Meter M1, switches S1 and S2, and control R11 are mounted on the top panel of the case. Capacitor C2 is mounted directly on the meter terminals. The two-conductor power cable exits the case where convenient.

continued on page 104

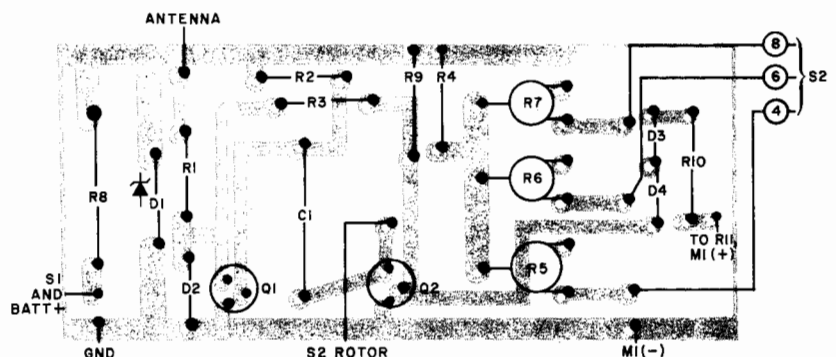
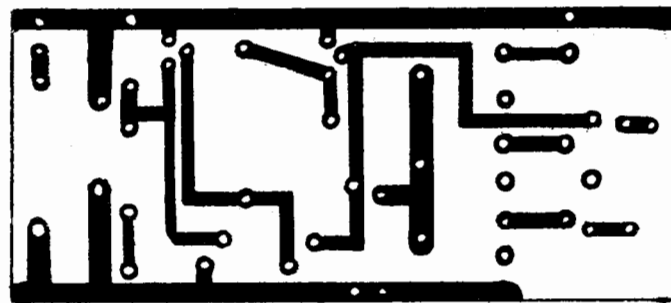


Fig. 2. Etching and drilling guide (top) and component layout diagram for a printed-circuit board for the tachometer.