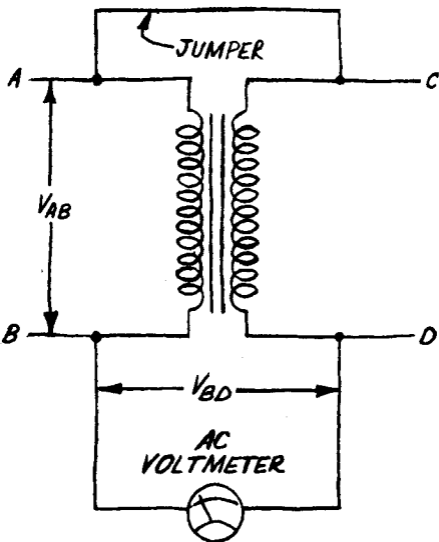


## DETERMINING TRANSFORMER POLARITIES

Here's a simple way to determine the phasing polarity of an unmarked transformer secondary. Apply an ac voltage across the



primary (points A and B) and read  $V_{AB}$  with an ac voltmeter. Then connect a jumper from point A to point C, and read  $V_{BD}$ . If this reading is higher than  $V_{AB}$ , point C has the same polarity as point B. If the reading is less, point C has the same polarity as point A. When there are more than two windings, the same test can be performed, but must be repeated for each set of coils.—*Douglas Koepke*