

# Microcontroller Interface Delivers Standard 4- To 20-mA Output

**R. JAYAPAL** | Bharat Heavy Electricals Ltd., Trichy, India  
 try\_kannajay@sancharnet.in


**Voltage-to-current converters** that feed grounded loads are common in industrial measurement and control applications. The conventional “text-book” circuit uses both positive and negative supply rails.

An earlier article by this author titled “Voltage-To-Current Converter Works From A Single Supply Rail” (Electronic Design, Feb. 17, 2003, ED Online 2985) described a circuit that could power grounded loads and needed only a positive supply rail. In a microcontroller-based application, a designer can use a digital-to-analog converter (DAC) to convert the digital data into an analog voltage and use it to create a 4- to 20-mA current output.

But Figure 1 shows a better way to generate an industry-standard 4- to 20-mA current output from 8-bit data (00–FF) in a microcontroller-based system. This simple circuit uses a digital potentiometer (AD5260) driven by the microcontroller’s serial peripheral interface (SPI) output.

Under ideal conditions, the voltages at the LM124 op amp’s inputs (inverting and non-inverting) are the same:

$$V - iR_1 = V - I(R_2 + R_V)$$

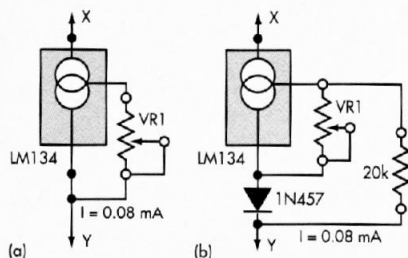

**2. An adjustable current source and 2-kΩ potentiometer can be used in place of the fixed 0.08-mA constant-current source (a). The current source can also be adapted for use in an application with varying ambient temperature by adding a diode and 20-kΩ resistor.**

**1. This simple circuit converts the digital output of a microcontroller’s SPI to an analog voltage and uses it to generate a 4- to 20-mA current.**

where  $i$  is the current through the ground-referenced load;  $I$  is the current through the digital potentiometer as set by constant-current source; and  $R_V$  is the potentiometer resistance between the wiper and one end.

Solving for  $i$ :

$$i = [I(R_2 + R_V)/R_1]$$

In the example,  $I$  is selected as 0.08 mA,  $R_1$  is 100 Ω, and  $R_2$  is 5000 Ω. Also, the AD5260 digital potentiometer’s total resistance is 20 kΩ.

Hence:

$$i = [(0.08 \text{ mA})(5000 + R_V)]/100$$

Using a routine in the microcontroller, load 00 to the digital potentiometer through the SPI, which drives the wiper to one end so that  $R_V$  is zero.


That makes:

$$i = 0.08 \times 10^{-5} (5000) = 0.004 \text{ A, or } 4 \text{ mA}$$

Load FF into the digital potentiometer and the wiper goes to the other end so that  $R_V$  is 20 kΩ. Therefore:

$$i = 0.08 \times 10^{-5} (5000 + 20,000) = 0.020 \text{ A, or } 20 \text{ mA}$$

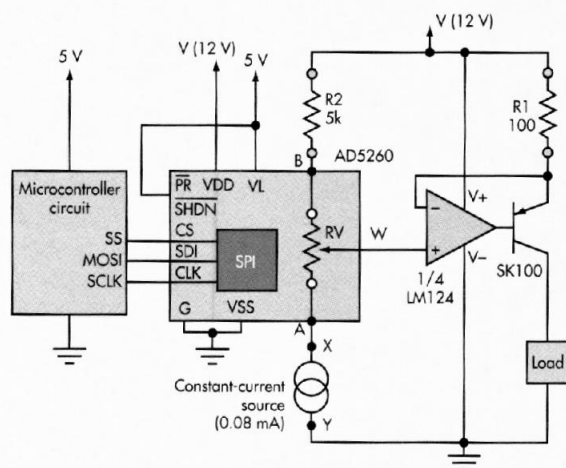As a result, for the data 00 to FF, the load current varies linearly from 4 mA to 20 mA.



However, the digital potentiometer’s wiper resistance is significant even when  $R_V$  is low, which introduces an error. To eliminate this error, the digital potentiometer is connected as a voltage divider, with the wiper resistance in series with the op amp’s non-inverting input.

If a 0.08-mA current source isn’t readily available, you can use a National Semiconductor LM134 three-terminal adjustable current source and a potentiometer (VR1) to precisely set  $I$  at 0.08 mA (Fig. 2). Similarly, if a precise 5000-Ω resistance is unavailable for  $R_2$ , a 10-kΩ multi-turn potentiometer can be employed.

The advantage of this circuit is its simplicity and the fact that it uses only three of the microcontroller’s port lines (SPI), unlike a DAC, which requires eight port lines for the 8-bit data. The circuit uses only a positive supply rail for operation. Digital potentiometers also are available with I<sup>2</sup>C interfaces, with integrated op amps, and with different resistance values. Designers can adapt this circuit for use with these digital potentiometers.

**R. JAYAPAL**, additional GM, holds a BE (Hons) from Annamalai University, India, an M. Tech from IITM, Chennai, India, and a PhD from NIT, Trichy, India. **ED ONLINE 17297**