

RS-485: Passive failsafe for an idle bus

By Thomas Kugelstadt

Senior Applications Engineer

Despite the integrated failsafe features of modern RS-485 transceivers, many applications use legacy parts lacking these features. Knowing how to provide failsafe operation, particularly during an idle-bus condition, therefore ranks at the top of the list of customer inquiries to interface-application groups worldwide. This article shows how to apply failsafe biasing for idle buses externally and also suggests low-cost solutions that integrate this feature.

Failsafe operation

RS-485 specifies that the receiver output state should be logic high for differential input voltages of $V_{AB} \geq +200$ mV and logic low for $V_{AB} \leq -200$ mV. For input voltages in between these limits, a receiver's output state is not defined and can randomly assume high or low.

Removing the uncertainty of random output states, modern transceiver designs include internal biasing circuits that put the receiver output into a defined state (typically high) in the absence of a valid input signal.

There are three possible scenarios that can cause the loss of an input signal:

- an open circuit caused by a wire break or the unintentional disconnection of a transceiver from the bus;

- a short circuit due to an insulation fault, connecting both conductors of a differential pair to one another; or
- an idle bus when none of the bus transceivers are active. (This particular condition is not a fault but occurs regularly when bus control is handed over from one driver to another to avoid bus contention.)


While modern transceiver designs provide failsafe operation for all three categories, legacy designs don't. For these components it is necessary to provide external resistor biasing to ensure failsafe operation during an idle bus.

External idle-bus failsafe biasing

Figure 1 shows an RS-485 bus with its distributed network nodes. If none of the drivers connected to the bus are active, the differential voltage (V_{AB}) approaches zero, thus allowing the receivers to assume random output states.

To force the receiver outputs into a defined state, failsafe biasing resistors, R_{FS} , are introduced that, through voltage-divider action with the terminating resistors, R_{T1} and R_{T2} , must provide sufficient differential voltage to exceed the input-voltage threshold, V_{IT} , of the receiver.

Figure 1. RS-485 network with failsafe bias resistors

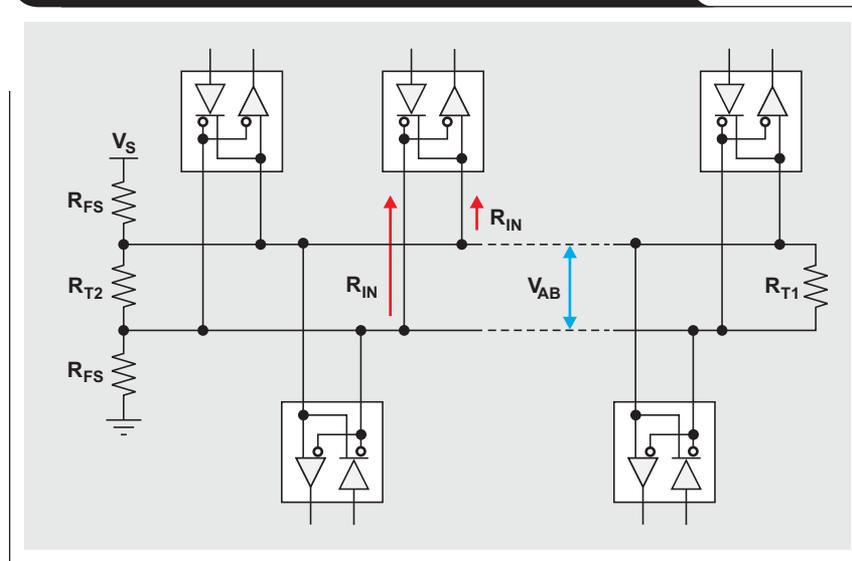

For clarity, Figure 2 shows the equivalent circuit of the RS-485 bus with the failsafe biasing resistors, R_{FS} , the terminating resistors, R_{T1} and R_{T2} , and the equivalent input resistance, R_{INEQ} , lumped together to represent the common-mode input resistance of all transceivers connected to the bus.

To find an equation that allows us to calculate the R_{FS} values, we determine the node currents in A and B (Figure 2) and solve for the respective line voltages, V_A and V_B .

Node A:

$$\frac{V_S - V_A}{R_{FS}} = \frac{V_A - V_B}{R_{T2}} + \frac{V_A - V_B}{R_{T1}} + \frac{V_A}{R_{INEQ}} \rightarrow$$

$$V_A = R_{INEQ} \times \left[\frac{V_S - V_A}{R_{FS}} - (V_A - V_B) \times \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right) \right]$$

Node B:

$$\frac{V_A - V_B}{R_{T2}} + \frac{V_A - V_B}{R_{T1}} = \frac{V_B}{R_{FS}} + \frac{V_B}{R_{INEQ}} \rightarrow$$

$$V_B = R_{INEQ} \times \left[(V_A - V_B) \times \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right) - \frac{V_B}{R_{INEQ}} \right]$$

Establishing the difference between both line voltages yields the differential input voltage,

$$V_{AB} = \frac{V_S}{R_{FS}} \times \frac{1}{\frac{1}{R_{INEQ}} + \frac{1}{R_{FS}} + 2 \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right)} \quad (1)$$

The value of R_{FS} is subject to a number of system and standard constraints:

- The RS-485 standard specifies a maximum common-mode loading (or minimum common-mode resistance) of $R_{CM} = 375 \Omega$. Because the failsafe bias resistors present a common-mode load to both the A and B wires, the parallel combination of R_{FS} and R_{INEQ} must be greater than or equal to 375Ω , which is expressed as

$$R_{FS} \parallel R_{INEQ} = R_{CM}, \text{ or } \frac{1}{R_{INEQ}} + \frac{1}{R_{FS}} = \frac{1}{375 \Omega} \quad (2)$$


- The cable end without the biasing network is usually terminated with the resistor R_{T1} , whose value matches the line impedance. For RS-485, this is

$$R_{T1} = 120 \Omega, \text{ or } \frac{1}{R_{T1}} = \frac{1}{120 \Omega} \quad (3)$$

- During normal operation, a driver output sees the series of both failsafe bias resistors in parallel to the terminating resistor R_{T2} . Thus, for line impedance matching, the parallel circuit of R_{T2} and $2R_{FS}$ should equal Z_0 :

$$R_{T2} \parallel 2R_{FS} = Z_0, \text{ or } \frac{1}{R_{T2}} = \frac{1}{120 \Omega} - \frac{1}{2R_{FS}} \quad (4)$$

Figure 2. Equivalent circuit with transceiver resistances lumped together

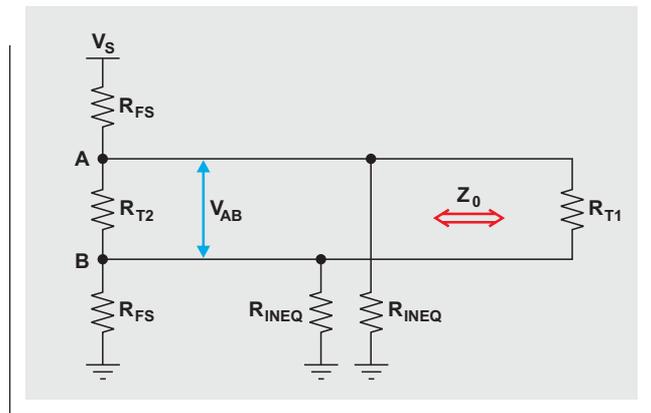

Inserting Equations 2, 3, and 4 into Equation 1 simplifies the expression for V_{AB} to

$$V_{AB} = \frac{V_S}{0.036 \times R_{FS} - 1} \quad (5)$$

Solving for R_{FS} yields

$$R_{FS} = \left(\frac{V_S}{V_{AB}} + 1 \right) \times 27.8 \Omega \quad (6)$$

Note that Equation 6 is a generic form for calculating the bias resistor value, with the constant of 27.8Ω representing the common-mode loading and line-matching constraints of an RS-485 system.

Because idle-bus failsafe must work under worst-case conditions, the values of the bias resistors must be calculated for minimum supply voltage at maximum noise. While $V_{S(\min)} = 4.75 \text{ V}$ for a standard 5-V supply with $\pm 5\%$ tolerance, the maximum noise is usually subject to measurement. For a well-balanced system, however, we can assume a differential noise of less than 50 mV, so that the sum of receiver input threshold and noise yields a differential input voltage of

$$V_{AB} = V_{IT} + V_{\text{Noise}} = 200 \text{ mV} + 50 \text{ mV} = 250 \text{ mV}.$$

Calculating R_{FS} under these conditions provides a theoretical value of

$$R_{FS} = \left(\frac{4.75 \text{ V}}{0.25 \text{ V}} + 1 \right) \times 27.8 \Omega = 556 \Omega.$$

Choosing the next lowest value of 549Ω from the E-96 series allows for a slightly higher voltage drop across R_{T2} .

With R_{FS} in place, we can now determine R_{T2} using the reciprocal of Equation 4 and the actual value of $R_{FS} = 549 \Omega$:

$$R_{T2} = \frac{1}{\frac{1}{120 \Omega} - \frac{1}{2R_{FS}}} = \frac{1}{\frac{1}{120 \Omega} - \frac{1}{2 \times 549 \Omega}} = 134 \Omega$$

Choosing the closest E-96 value makes $R_{T2} = 133 \Omega$ and the differential impedance of $R_{T1} \parallel R_{T2} \parallel 2R_{FS} = 59.7 \Omega$.

As mentioned earlier, failsafe biasing presents an additional common-mode load to both the A and B wires. To stay below the specified common-mode load of 375Ω , it is necessary to determine the maximum number of transceivers that can be connected to the bus. For this purpose we solve Equation 2 for R_{INEQ} :

$$R_{INEQ} = \frac{1}{\frac{1}{R_{CM}} - \frac{1}{R_{FS}}} = \frac{1}{\frac{1}{375 \Omega} - \frac{1}{549 \Omega}} = 1.183 \text{ k}\Omega$$

The maximum number of transceivers, n_{max} , is determined by dividing the rated number of unit loads (UL) by the value of R_{INEQ} :

$$n_{max} = \frac{UL}{R_{INEQ}} = \frac{12 \text{ k}\Omega}{1.183 \text{ k}\Omega} = 10.14$$

This result indicates that a maximum of 10 standard unit-load transceivers, $10 \times UL$, which is equivalent to $20 \times \frac{1}{2} UL$, $40 \times \frac{1}{4} UL$, or $80 \times \frac{1}{8} UL$, can be connected to the bus. The final circuit with the actual resistor values is shown in Figure 3.

Conclusion

While the calculation of a failsafe-biased network for legacy transceivers is straightforward, the use of modern RS-485 transceivers such as the SN65HVD308xE family from Texas Instruments eliminates external failsafe biasing. These low-cost devices provide integrated failsafe biasing for open-circuit, short-circuit, and idle-bus conditions as well as a rating of $\frac{1}{8} UL$, thus increasing the possible number of transceivers that can be connected to a bus to 256.

Reference

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title

TI Lit. #


1. "Interface Circuits for TIA/EIA-485 (RS-485)," Application Report. slla036d

Related Web sites

interface.ti.com

www.ti.com/sc/device/SN65HVD3080E

Figure 3. Final RS-485 network with actual resistor values

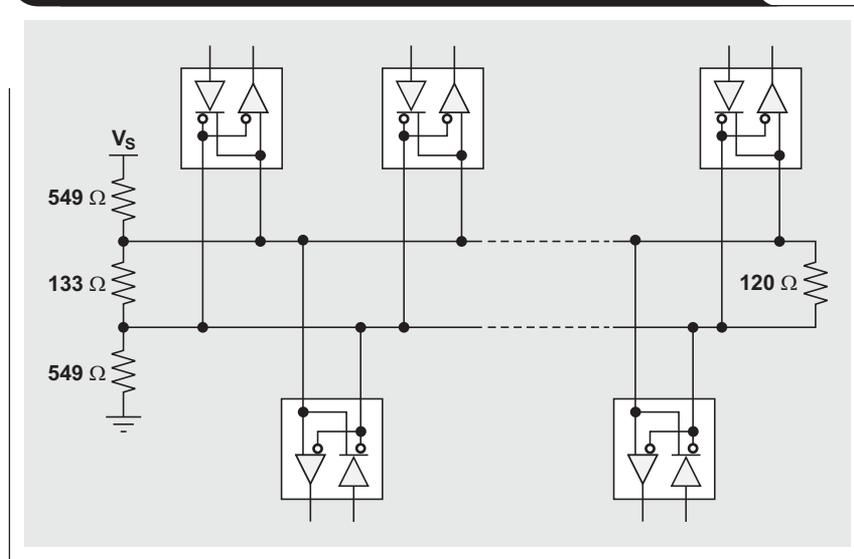

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Broadband	www.ti.com/broadband
DSP	dsp.ti.com	Digital Control	www.ti.com/digitalcontrol
Clocks and Timers	www.ti.com/clocks	Medical	www.ti.com/medical
Interface	interface.ti.com	Military	www.ti.com/military
Logic	logic.ti.com	Optical Networking	www.ti.com/opticalnetwork
Power Mgmt	power.ti.com	Security	www.ti.com/security
Microcontrollers	microcontroller.ti.com	Telephony	www.ti.com/telephony
RFID	www.ti-rfid.com	Video & Imaging	www.ti.com/video
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

E093008

All trademarks are the property of their respective owners.