

thief suppression in cars

Thefts of cars, or accessories and/or other articles in them, are becoming more and more common. By the same token, anti-theft alarms for cars are becoming more and more of a necessity

Each year an increasing number of cars are stolen. The majority of them are quickly recovered, but at best they have been abandoned on running out of petrol, and often they are a total write-off, with everything of value removed. Thefts of articles from cars are still more common, especially now that expensive in-car entertainment systems are so popular. When compared with the possible loss of property and/or no-claims bonus, the cost of installing a burglar alarm is negligible, and two designs are presented here, which should cost about 10 p and £ 10 respectively. Even with an alarm installed, however, do not ignore the simple precautions advised by the police. Lock all valuables in the boot, and make sure that all doors and windows are securely fastened.

A very simple alarm.

The simplest of the burglar alarms can be constructed from components that most enthusiasts will have in their junk box. It makes use of the door courtesy light switches and the horn relay, and the only additional components required are three diodes and a hidden switch to activate and de-activate the alarm. However, one door of the car is left unprotected.

The circuit operates as follows:

S_1 and S_2 are the courtesy light switches. When the hidden switch S_3 is closed, opening the door protected by S_2 causes the horn relay to operate via S_3 , D_2 and S_2 . When the horn relay contacts close the horn sounds and the cathode of D_3 is grounded via the relay contacts. This latches the horn relay via S_3 and its own contacts. The horn will continue to sound even if the door is closed, unless S_3 is opened. The door containing S_1 is, of course, not protected, as when S_1 is closed D_1 is reverse biased and only the interior light operates.

When the alarm is not armed (S_3 open), D_2 prevents the interior light from lighting when the horn button is pressed and D_3 prevents the horn from sounding when the interior light is switched on.

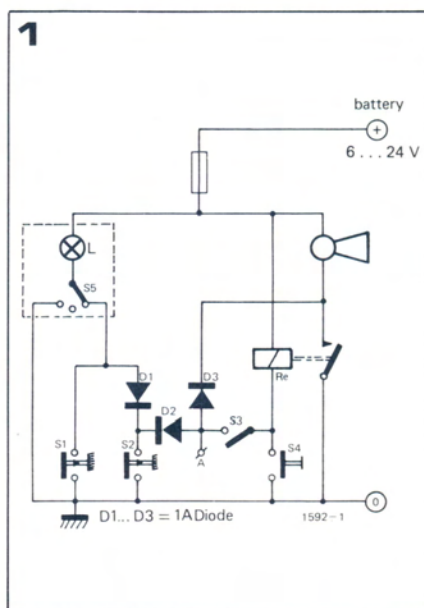


Figure 1. Circuit of the simplest burglar alarm consisting of three diodes and a switch. The door containing S_1 is not protected. Additional door switches should be wired in parallel with S_2 , other switches such as boot and glove compartment between point A' and earth.

Figure 2. Block diagram of the sophisticated alarm.

Figure 3. Timing diagram of the alarm of figure 2.

Figure 4. Circuit of the sophisticated alarm, which uses COSMOS IC's.

Figure 4a. Alternative method of wiring the horn and horn relay, for cars with one side of the horn connected to chassis.

Additional courtesy light switches (in the case of a four-door car) may be connected in parallel with S_2 , and switches to protect glove compartment and other ancillary equipment may be connected between point 'A' and ground.

This simple alarm will provide a fair degree of protection at little cost, but it should be noted that alarms which sound indefinitely after being triggered are illegal in some European countries.

A sophisticated alarm.





A block diagram of a more sophisticated burglar alarm system is given in figure 2. In many modern cars with a steering lock there is no need to have a concealed reset switch as a position is often available on the ignition switch that only opens when the switch is in the 'locked' position. It is thus possible, on entering the car, to de-activate the

alarm by inserting the ignition key and turning it to the first position (without actually switching on the ignition). On cars without a steering lock, however, it will be necessary to use a separate concealed switch - or a separate lock-switch.

A timing diagram of the alarm is given in figure 3. On removing the ignition key from the lock the driver has about one-and-a-half minutes to leave the car and lock the doors. If a door is subsequently opened there is a delay (adjustable from 5 to 15 seconds) to allow the driver to reset the alarm with the ignition key. Failing this, the alarm operates and the horn will sound continuously for 30 seconds. After this there is ten seconds silence, then short three second blasts with ten seconds silence in between until the alarm is reset or the door is closed. The complete circuit of the alarm is given in figure 4.

When S_1 is opened C_1 begins to discharge through R_1 and R_2 . When the voltage on C_1 falls below the threshold voltage of gate 2 then the flip-flop consisting of gates 1 and 2 is set.

This holds the input (pin 13) of gate 4a high, which means that when one of the door switches (represented by S_2) closes, the flip-flop consisting of gates 3a and 4a is set. The alarm is triggered, and even closing the door (opening S_2) will not reset the flip-flop. C_2 and C_3 were previously charged through R_6 and D_3 from the output of gate 1a. C_2 and C_3 now discharge through R_5 into the output of gate 4a. C_3 may be optionally switched in by S_3 to increase the delay before the alarm sounds. With S_3 closed the delay is about 15 seconds; with S_3 open the delay is only 5 seconds. If this facility is not required S_3 and C_3 may be omitted and C_2 replaced by a capacitor chosen to give the required delay.

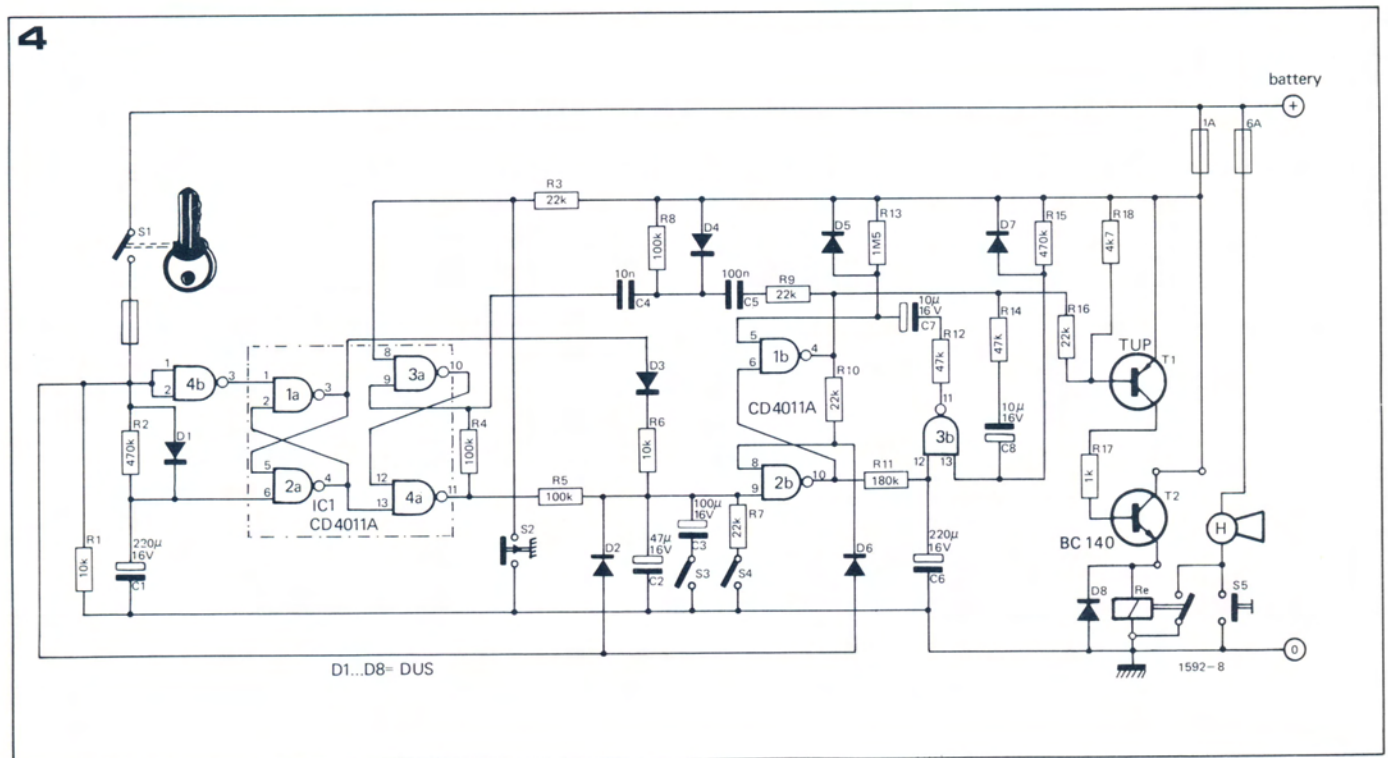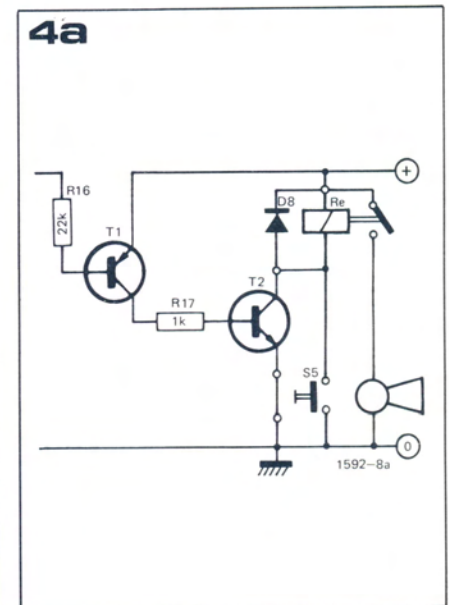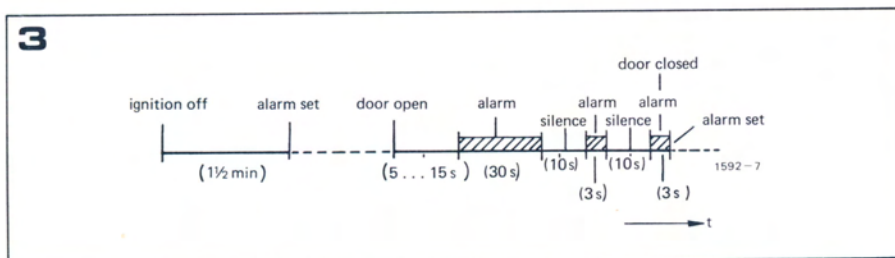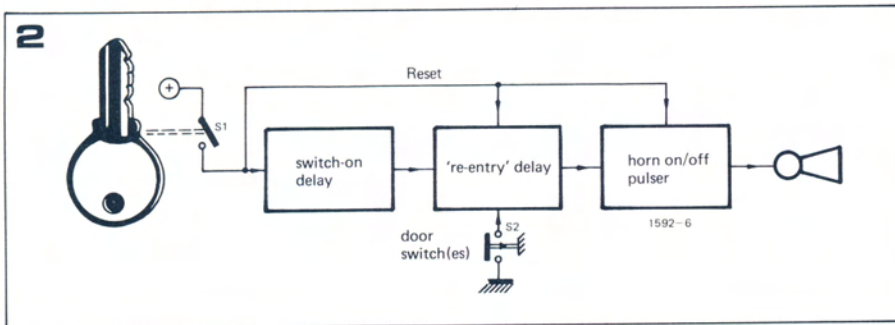

S₄ may be a trembler switch or switch(es) on glove compartment, boot etc., which will discharge C2 and C3 rapidly and trigger the alarm.

When C2 and C3 have discharged the output of gate 2b goes high. This takes pin 6 of gate 1b high. Since the other input is held high by R13 the output goes low, turning on T1 and T2 and sounding the horn. C8 charges through R14 and R15 in about 3 seconds, taking pin 13 of gate 3b high. Meanwhile C6 slowly charges through R11 and it is this time constant that determines the duration of the initial blast of the horn (about 30 seconds).

When the voltage on C6 exceeds the threshold voltage of gate 3b the output of this gate goes low, grounding pin 5 of gate 1b through C7 and R12. The output of 1b thus goes high and the horn switches off. C8 now discharges through D7, R14 and the output of gate 1b. C7 slowly charges through R13 and R12, and this time constant determines the 'off' period of the horn (about 10 seconds). When C7 has charged to the threshold voltage of gate 1b the output goes low and the horn again sounds. C8 charges through R14 and R15, and this time constant determines the subsequent 'on' periods of the horn (about 3 seconds).

After this period the output of 3b goes low, grounding pin 5 of gate 1b through R12 and C7, and the whole cycle repeats.

Gates 1b and 3b thus form an asymmetric multivibrator which causes the horn to produce short blasts at 10 second intervals. In addition, each time the horn is switched off a differentiating network consisting of R8, R9, C4 and C5 feeds a reset pulse to pin 9 of gate 3a, so that if the doors are closed during the horn 'off' period, the horn will not sound again and the alarm will be re-set.

The only disadvantage of this alarm circuit is that it cannot easily be adapted for positive earth cars. On the other hand, it has the advantage that it is insensitive to spurious pulses due to the high noise immunity of COSMOS. The circuit will operate over a wide range of supply voltages without modification (4 to 14 volts), with almost the same delays.

Installation of the alarm

To ensure reliable operation the alarm should be mounted where it cannot be disabled by a thief, but not inside the engine compartment, which gets rather hot for COSMOS. Wiring should be concealed or made as inconspicuous as possible, especially wiring into the engine compartment if the car does not have a bonnet lock. In this case it is also wise to install an alarm switch in the bonnet lid, as otherwise the alarm could be disabled simply by disconnecting the battery. Another (somewhat expensive)

possibility would be to power the alarm from a separate battery locked in the boot. Wiring from the battery to the alarm should, of course, be direct, not via the ignition switch, and the simplest way is to run cables from the battery side of the fuse box with in-line fuse holders in them.

When constructing either of these alarms it should be borne in mind that they may need to be adapted to suit particular types of car. For instance, some horn relays have one end of the coil and the contact commoned, so they would not work in the circuit of figure 1. A separate heavy-duty relay (6A contacts) would have to be used. This problem does not arise with the more sophisticated design, and a normal horn relay may be used. A printed circuit board layout is given in figure 5 for the alarm circuit of figure 4 and this has alternative sets of connections for the relay, as shown in figure 4a, to suit different car wiring. S₅ in both circuits is the original pushbutton for the horn.

Final Remarks

The designs discussed in this article give varying degrees of protection at varying cost. It should be remembered that any protection is better than none - the majority of thieves are amateurs and will be deterred by even the simpler circuit described.

