

## Dual-supply, discrete, programmable gain amplifier circuit


### Design Goals

Input		Output		Supply	
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$
-1.25V	+1.25V	-2.4V	+2.4V	+2.5V	-2.5V

Gain	Cutoff Frequency
6dB (2V/V) to 60dB (1000 V/V)	7kHz
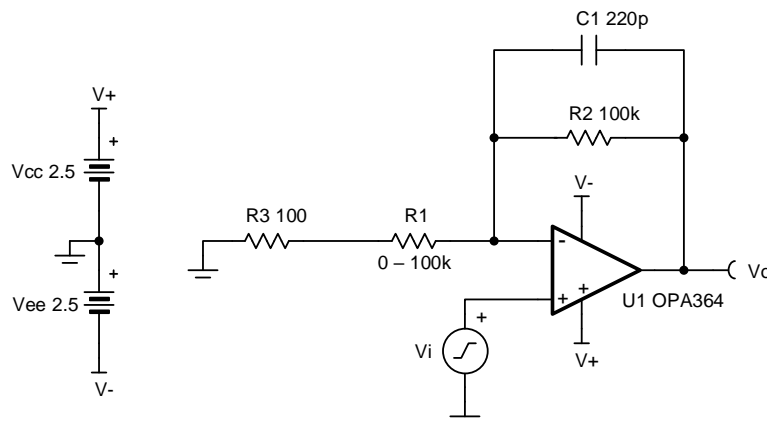
### Design Description

This circuit provides programmable, non-inverting gains ranging from 6dB (2V/V) to 60dB (1000V/V) using a variable input resistance. The design maintains the same cutoff frequency over the gain range.



### Design Notes

1. Choose a digital potentiometer, such as TPL0102 for  $R_1$  to design a low-cost digital programmable gain amplifier.
2.  $R_3$  sets the maximum gain when  $R_1$  approaches  $0\Omega$ .
3. A feedback capacitor limits the bandwidth and prevent stability issues.
4. Stability should be evaluated across the selected gain range. The minimum gain setting will likely be most sensitive to stability issues.
5. Some digital potentiometers can vary in absolute value by as much as  $\pm 20\%$  so gain calibration may be necessary.

## Design Steps

1. Choose  $R_2$  and  $R_3$ , to set the maximum gain when  $R_1$  approaches 0:

$$G_{\max} = 1 + \frac{R_2}{R_3}$$

$$G_{\max} - 1 = \frac{R_2}{R_3} \rightarrow R_2 = (G_{\max} - 1) \times R_3$$

$$\text{Set } R_3 = 100 \Omega$$

$$R_2 = (1000 \frac{V}{V} - 1) \times 100 = 99 \text{ k}\Omega \rightarrow R_2 = 100 \text{ k}\Omega \text{ (Standard value)}$$

2. Choose the potentiometer maximum value to set the minimum gain:

$$G_{\min} = 1 + \frac{R_2}{R_{1,\max} + R_3}$$

$$G_{\min} - 1 = \frac{R_2}{R_{1,\max} + R_3}$$

$$R_{1,\max} + R_3 = \frac{R_2}{G_{\min} - 1}$$

$$R_{1,\max} = \frac{R_2}{G_{\min} - 1} - R_3 = \frac{100\text{k}\Omega}{2 - 1} - 100\Omega = 99.9\text{k}\Omega \rightarrow R_{1,\max} = 100\text{k}\Omega \text{ (Standard value)}$$

$$R_{1,\min} = 0\Omega \text{ (Wiper resistance, typically } 25\Omega, \text{ will introduce some error)}$$

3. Choose the bandwidth with a feedback capacitor:

$$f_c = \frac{GBW}{G_{\max}} = \frac{7\text{MHz}}{1000 \frac{V}{V}} = 7\text{kHz}$$

$$f_c = 7\text{kHz} \rightarrow C_1 = \frac{1}{2\pi \times R_2 \times f_c} = 227\text{pF} \rightarrow C_1 = 220\text{pF} \text{ (Standard Value)}$$

4. Check for stability at minimum gain ( $2V/V$ ), which is when  $R_1=100\text{k}\Omega$ . To satisfy the requirement  $f_c$  (circuit bandwidth) must be less than  $f_{\text{zero}}$  (zero created by the resistive feedback network and the differential and common-mode input capacitances).

$$f_c = \frac{1}{2\pi \times C_1 \times R_2} = 7 \text{ kHz}$$


$$f_{\text{zero}} = \frac{1}{2\pi \times (C_{\text{cm}} + C_{\text{diff}}) \times (R_2 \parallel R_1)} = \frac{1}{2 \times \pi \times (3 \text{ pF} + 2 \text{ pF}) \times \left( \frac{100 \text{ k}\Omega \times 100 \text{ k}\Omega}{100 \text{ k}\Omega + 100 \text{ k}\Omega} \right)}$$

$$f_{\text{zero}} = 637 \text{ kHz}$$


$$7 \text{ kHz} < 637 \text{ kHz} \rightarrow f_c < f_{\text{zero}}$$

## Design Simulations

### Transient Simulation Results

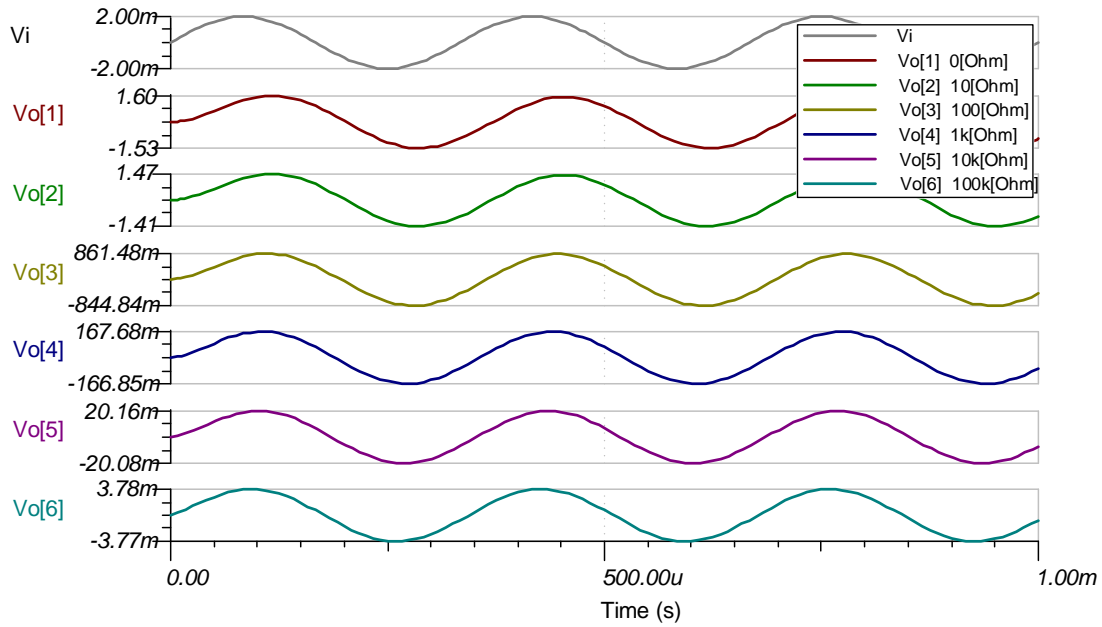

### AC Simulation Results

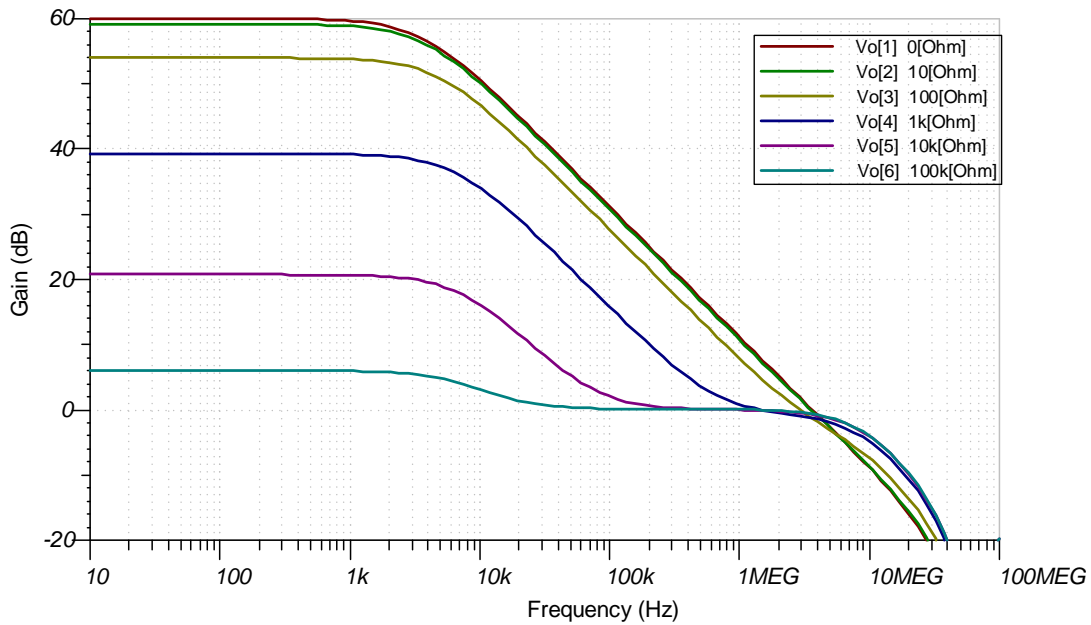

**References:**

1. [Analog Engineer's Circuit Cookbooks](#)
2. SPICE Simulation File [SBOC521](#)
3. TI Precision Designs [TIPD204](#)
4. [TI Precision Labs](#)

**Design Featured Op Amp**

OPA364	
$V_{ss}$	1.8V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	1mV
$I_q$	1.1mA
$I_b$	1pA
<b>UGBW</b>	7MHz
<b>SR</b>	5V/ $\mu$ s
<b>#Channels</b>	1, 2, 4
<a href="http://www.ti.com/product/opa364">www.ti.com/product/opa364</a>	

**Design Alternate Op Amp**

OPA376	
$V_{ss}$	2.2V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	5 $\mu$ V
$I_q$	760 $\mu$ A
$I_b$	0.2pA
<b>UGBW</b>	5.5MHz
<b>SR</b>	2V/ $\mu$ s
<b>#Channels</b>	1, 2, 4
<a href="http://www.ti.com/product/opa376">www.ti.com/product/opa376</a>	