

Diode compensates distortion in amplifier stage

S Chekcheyev, Pridnestrovye State University, Moldova

THE VOLTAGE AMPLIFIER in Figure 1 exhibits smaller nonlinear distortion than does the conventional amplifier in Figure 2. Diode D_1 compensates for the distortion inherent in the npn transistor. The voltage gain of a common-emitter amplifier depends on the transconductance of the transistor. The transconductance of the bipolar transistor is as follows:

$$S = \frac{eI}{k(273 + T^{\circ}C)} = nI,$$

where e is the charge of an electron, k is Boltzmann's constant (approximately $1.38 \times 10^{-23} \text{ J/}^{\circ}\text{K}$), $T^{\circ}C$ is temperature in degrees Celsius, I is the emitter current, and $n = e/[k(273 + T^{\circ}C)]$. So, the transconductance is proportional to the emit-

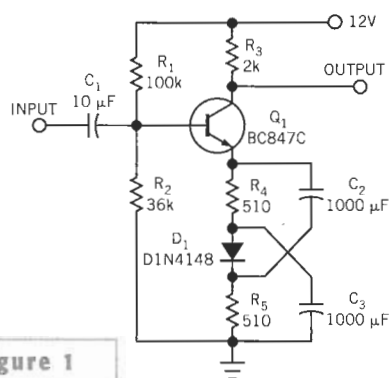


Figure 1

The addition of a simple diode in the emitter circuit yields the symmetric waveform of Figure 4.

ter current. Consequently, the instantaneous voltage-gain coefficient of the conventional common-emitter amplifier is proportional to the instantaneous emitter current. As a result, the negative half-cycle of the output signal gets more amplification than does the posi-

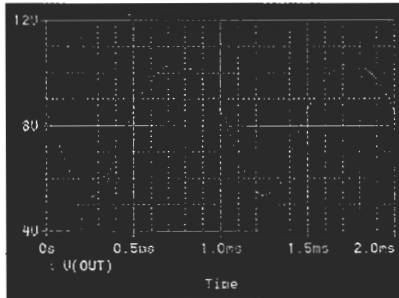


Figure 3

Nonlinearity of the transconductance of Q_1 results in this distorted waveform.

tive half-cycle (Figure 3).

The dynamic resistance of diode D_1 in Figure 1 is inversely proportional to the instantaneous current. That dynamic resistance forms part of the negative-feedback circuit of the amplifier. The average current of diode D_1 is equal to the average emitter current of transistor Q_1 . However, the instantaneous current of D_1 becomes smaller, and the instantaneous dynamic resistance of D_1 becomes larger when the instantaneous emitter current of Q_1 becomes larger, and vice versa. Therefore, the negative feedback becomes stronger during the negative half-cycle of the output signal. As a result, the output signal of the amplifier be-

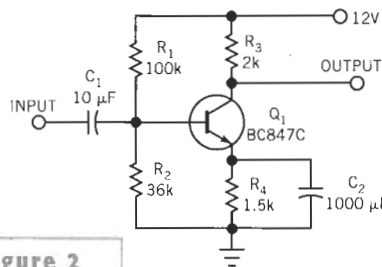


Figure 2

This amplifier circuit produces the distorted waveform of Figure 3.

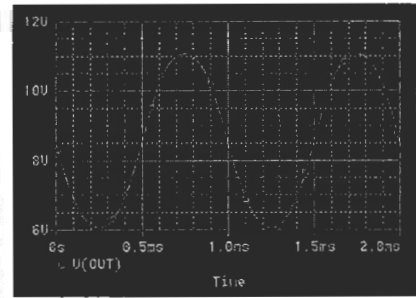


Figure 4

The diode in the circuit of Figure 1 produces varying, beneficial, negative feedback.

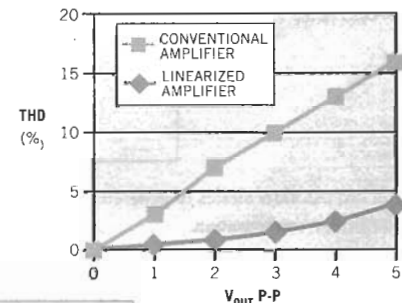


Figure 5

The linearized amplifier produces less than one-third the harmonic distortion of the conventional amplifier.

comes more symmetric (Figure 4). The circuits in figures 1 and 2 have the same average collector current and the same load resistance. Figures 3 and 4 show the results of their PSpice simulation. The amplitude of the output signal is 5V p-p in both cases with a 1-kHz sinusoidal signal applied to the input. You can see that the linearized amplifier yields a more symmetrical output signal. Figure 5 gives the quantitative results of the simulations. The improvement in harmonic distortion accrues because of the suppression of the even harmonics in the output of the linearized amplifier. □