13. A New Graduate's Guide to the Analog Interview

It wasn't that long ago that armed with a couple of engineering degrees and a snappy new suit, I walked headlong into disaster: my first technical interview. The interview was with a well-known Silicon Valley integrated circuit manufacturer, and I had no idea what was in store for me. After flailing through six one-hour grueling technical sessions and my first power lunch, I remember stumbling to my car while visions of pn junctions, amplifiers, TTL gates, and flaming airplanes in a deadly tailspin swam though my brain. What went wrong?

I didn't go into the interview unprepared. I attended the "how to interview" classes held by the career placement center. The center's staff had helped me create a resumé with plenty of style and power adjectives. I was forced to watch the videotape of my practice interview in hopes that my awkward hand gestures and use of the deadly "you know" and "uh" might improve. My girlfriend (now my wife) had picked out the tie. I had five years of engineering classes and lab experience, and had spent the last two learning about analog IC design. I had torn apart my Apple II computer, designed and built my own stereo amplifier, and knew where the power-on button of a Tektronix 547 oscilloscope was located.

What went wrong? The people in the career planning office had taught me about the generic interview, my professors had taught me about analog circuit design, but it was up to me to learn how to combine the two. It took a couple of days of "on the interview training," before I finally got the hang of it, and the interviews became easier.

Now that I am sitting on the other side of the interviewing table, I find that most students still find themselves in the position I was in 10 years ago. The first interview is tough, and the last is easy. So here are some tips that I hope will make your first interview as good as your last. All it takes is a little preparation, knowing what to expect during the interview, and being able to solve a handful of basic analog circuit problems.

Preparation

Be prepared to answer this question intelligently: what do you want to do? It is surprising how many students fumble for answers when asked this question. I have actually heard students say "uh, graduate" and "get a job." Wrong. A well-thought-out answer with a dash of enthusiasm will go a long way towards getting an offer letter. As an interviewer, I would like to hear something like, "I want to join your company so I can sit at the feet of the gurus of analog integrated circuit design," but since this has yet to happen, I would settle for someone who says he has a keen interest in analog design and is willing to work hard.

All good interviewers will ask you to describe something that you have done before, so learn one circuit or system very well. It could be from a senior project, classwork, a final exam, or simply a late-night home-brew circuit hack. Have your classmates or an advisor pepper you with questions about the circuit. "What is the bandwidth? How did you compensate this node? What is the function of this transistor?" I like to ask the following question during an interview: draw me the schematic of any amplifier that you have designed and tell me about it. I then see how far the student can go in describing the circuit. The idea is to put the student at ease by having him describe a circuit that he is familiar with, while I find out how well he really understands the circuit.

If you describe a design or research project on your resumé, you better know it backward and forward. I occasionally interview a student whose resumé claims he has worked on a very challenging project, but he is unable to answer even the most basic technical questions about it. Adding a flashy project to your resumé may get you noticed, but if you are not prepared to discuss the project's technical details in depth, it is the quickest route to a rejection letter. If you don't thoroughly understand something, leave it off the resumé.

Before you go to the interview, find out what the company does. Find a data book or other literature that describes the company's products. By becoming familiar with the product line, you will be able to anticipate what technical questions you will get, and be able to ask some inspired questions. For example, when a classmate of mine was about to interview at a satellite communications company, he spent an entire day in the Stanford library reading all of the IEEE journal articles that the company's famous chief scientist had written. During the interview, my classmate was asked how he would design a certain system, so he said, "Well, at first glance I would probably do it like this . . . ," then went on to describe everything he had read in the chief scientist's articles. Of course my classmate came out of the interview looking like a genius and got the offer.

Know ahead of time what salary you want. Go to the career placement center and get a salary survey of students in your field with the same degree. It is best to know what you are worth so you can negotiate the salary you want in the beginning. Once you start working it is too late.

Prepare a set of questions that you will ask the interviewer. What is the worst and best part of his job? How does he like the company? What is the most difficult circuit he has designed? Design some questions so you get a feel for what it is like to work at that company, and whether or not you will be able to work with these people 8+ hours a day.

Finally, keep in mind that most managers think that enthusiasm, willingness to work hard, good communication skills, and amiable demeanor are much more important than the ability to solve a handful of tricky circuit problems. So when you interview, relax. Try to convey your love for analog design, your willingness to work hard, and try to stay cool. And please, remember not to call the interviewer "dude." (That actually happened more than once.)

The Interview

Most companies go through a three-step interview process. The first step is a quick on-campus interview to make sure that you are really in the electrical engineering program, you can speak in complete sentences, and you can answer some basic circuit questions. If you don't look like a complete bum, show an interest in analog design, and can recite Ohm's Law from memory, you can usually make it past this interview.

The second interview is over the phone with the hiring manager. He wants to make sure that is worth the time and effort to bring you into the plant for the final interview. The phone interview usually consists of ask-ing what classes you took, asking you to describe the project listed on the resumé, then a series of simple circuit questions.

The third and most important interview is at the factory. The hiring manager will generally warm you up with a cup of coffee, a plant tour, and a description of the work the group is doing. Then all hell breaks loose. You will have several one-hour technical interviews with different engineers, a lunch interview where the technical staff tries to determine your compatibility with the group while you bravely try to describe pn junction theory and chew at the same time, followed by an afternoon of more technical interviews. If you have an advanced degree, you will usually be required to give a lecture to the technical staff as well.

The term "technical interview" doesn't tell the whole story; "technical grilling" is more appropriate. After the usual introductions and discussion of your career goals, etc., the grilling will begin. If the interviewer is good, he will have you describe the circuit or system listed on your resumé, which you will ace because you came prepared. Then the interviewer will pull out his favorite technical questions. These are usually designed to test your basic knowledge of circuit design, and more importantly, they allow the interviewer to evaluate your approach to solving problems that you have not seen before.

Some interviewers will have you solve the problems on paper, others on a marker board on the wall, but in either case, you will be required to think on your feet. Remember that the interviewer is looking at your approach to solving the problem and doesn't always expect you to solve it completely. When trying to solve a new problem, resist the temptation to start writing equations right away. Stop and think about what is really happening in the circuit. Try to reason out the function of different sections of the circuit and decide what parts you do and don't understand. Try to describe out loud what you are thinking. For instance, "If this node goes up, then that node goes down, so the circuit is using negative feedback." Once you understand how the circuit works, and you have a plan of attack, then you can pull out the equations.

Remember that it is always much better to say that you don't understand something than to guess. You'll never get hired if a manager thinks you are trying to b.s. your way through a problem. Rather, tell the interviewer what you do know, and what you don't understand. Tell him what you will need to know in order to solve the problem.

Try to jot down some notes about each question that you are asked. If you weren't able to solve it completely, try to finish it at home. You will be surprised at how many times the same circuit problem comes up at different interviews. When I was interviewing, I heard some questions so many times that I had to force myself to prevent the answer from sounding like a tape recording. (#1 question: What are the components of the threshold voltage for a MOS transistor?)

Make sure that you get a list of the people that interviewed you and a business card from each one. It is always a good idea to write all the interviewers thank you notes a couple of days after the interview, as it provides an easy way of reminding them of who you are and that you really want a job. Even if you don't get a job offer, they may provide valuable contacts in the future.

Sample Interview Questions

Interview questions come in all shapes and forms. I had to complete a 10page exam for one interview. The first problem was trivial and each one got progressively harder, with the last one being mind-numbing. The interviewer used the exam to keep track of how well each university was preparing its students, and as a reference to remember each student. (Results: #1 UC Berkeley) Some companies, like Hewlett-Packard, like to ask tough questions that are not related to your field of expertise just to watch you sweat. I had this question while interviewing for a circuit design job: "You have a beaker of water with diameter x, water depth y, and you stir the water at a constant rotational velocity. How high does the water move up the sides of the beaker? I'll give you any equation you need to know." But you'll find that most questions are simple and keep appearing over and over. Here is a sample of common interview questions that I have accumulated over the years from my friends in the analog business (yes, the answers are in the back): Q1. If you put a 0-to-5-voltstep voltage referenced to ground into the circuits shown in Figures 13-1A and 13-1B, sketch the wave forms you would expect to see at the outputs.



Q2. As the base emitter voltage of the bipolar transistor Q1 in Figure 13–2 is increased from OV, sketch the voltage at the output node.

Figure 13-2.



Q3. Two loudspeakers with a passive input filter are shown in Figures 13-3A and 13-3B. Which one is the woofer, and which one is the tweeter?



Q4. In Figure 13–4, the diode and transistor are a matched pair. If the forward voltage of the diode is 0.7V, what is the approximate collector current in the transistor Q1?



Q5. A constant-current lo is fed into the diode connected-transistor Q1 shown in Figure 13–5. What happens to the output voltage Vo as temperature is increased?





Q6. The ideal op amps of Figures 13–6A and 13–6B are connected with feedback resistors R1 and R2. What is the closed-loop DC gain of each configuration?



- Q7. Assume that the op amps of Figures 13-6A and 13-6B have finite gain A_o. Now what is the closed-loop DC gain?
- **Q8.** The capacitor of Figure 13–7 is connected with two ideal MOS switches. Switches T1 and T2 are alternately turned on with a frequency f_c . What is the average current flowing from node 1 to node 2? What is the equivalent impedance from node 1 to node 2?



Figure 13-7.

Q9. The regulator of Figure 13–8 has an input voltage of 8V, a bias resistor R1 of 100Ω , and 10mA flowing through the 6V zener diode. Calculate the value of beta of the NPN transistor Q1 if the load current is 100mA.



Figure 13-8.

Q10. Assume that the diode D1 of Figure 13–9 is ideal. Sketch the wave form of Vo.



Figure 13-9.

Q11. The bipolar transistor of Figure 13–10 is biased so the voltage across R_L is 260mV. A small AC signal is applied to the input node. Qualitatively describe what the voltage at the output looks like. Calculate the AC gain.



- Q12. A two-pole amplifier is found to have an open-loop DC gain of 100dB, a gain-bandwidth product of 10MHz, and 45° of phase margin. Sketch the Bode plot for the open-loop amplifier, showing the gain, phase, and location of the poles.
- Q13. The Darlington pair of NPN transistors Q1 and Q2 in Figure 13–11 each have a current gain of β. What is the approximate total current gain of the pair?



Figure 13-10.



Q14. The drain current of the JFET shown in Figure 13-12 is 2.5mA when Vgs is set to -2.5V, and 2.7mA when Vgs is -2.4V. Calculate the pinch-off voltage and the drain-source saturation current.



Q15. A CMOS amplifier consisting of PMOS device Q1 and NMOS device Q2 is shown in Figure 13–13. Assuming that they both have the same gate oxide thickness, what is the approximate gain of the amplifier?



Figure 13-13.

- Q16. You are probing a square wave pulse in the lab that has a rise time of 5ns and a fall time of 2ns. What is the minimum bandwidth of the oscilloscope needed to view the signal?
- Q17. What is the thermal rms noise voltage of a 1k resistor at 300K?
- **Q18.** A transistor dissipates 25 W in an ambient temperature of 25°C. Given that the thermal resistance of the transistor is 3°C/W and the maximum junction temperature is 150°C, what is the thermal resistance of the heat sink required?
- Q19. Draw the equivalent circuit of an exclusive-nor gate using only inverters, nand, and nor gates. (Hey, even analog guys need to know some digital stuff.)
- Q20. You are offered the following jobs; which one do you take?a. Hacking C++ code for Windows
 - b. A windsurf instructor at Club Med in the Canary Islands
 - c. A roadie for the upcoming Rolling Stones tour
 - d. An analog design engineer

Figure 13-14.

Answers to Sample Interview Questions

Q1. Remember that the voltage across a capacitor cannot change instantaneously, and the time constant is 1/RC, as shown in Figure 13–14.



Q2. The output voltage has three distinct regions as shown in Figure 13–15: Q1 off, Q1 in the linear region, and Q1 saturated.



- Q3. Assuming that the filter prevents high frequencies from reaching the woofer, and low frequencies from reaching the tweeter, A is the woofer, and B is the tweeter.
- Q4. The current through the diode = (12 0.7)/11.3k = 1mA. If the diode and Q1 are a matched pair, then the circuit is a current mirror with the collector current equal to 1mA.
- Q5. With a constant collector current, the output voltage will show a slope of $\sim -2 \text{ mV/}^{\circ}\text{C}$.
- Q6. Figure A has an inverting gain of -R2/R1 and B has a noninverting gain of (1 + R1/R2).
- Q7. Figure A has an inverting gain of 1/(1/Ao + R1/Ao R1/R2). Figure B has a noninverting gain of (R2 + R1)/[(R2 + R1)/Ao + R2].

- **Q8.** For every clock cycle, a small amount of charge = C(V1 V2) is transferred to and from the capacitor. Therefore, the average current is i = q/time or i = $Cf_c(V1 V2)$. The equivalent impedance is $\Delta V/i = 1/Cf_c$
- **Q9.** The current in the resistor is (8-6)/100 = 20mA. If the zener requires 10mA to sustain 6V, then the base current of Q1 is 20mA 10mA = 10mA. The transistor is then operating with a beta of (|e/lb 1) = (100mA/10mA 1) = 9.
- Q10. With a 10:1 turns ratio, the peak voltage on the secondary side of the transformer is 12V as shown in Figure 13–16. On the positive half cycle, the diode is not conducting so the output voltage is divided in half. On the negative half cycle, the ideal diode conducts so that the full voltage appears at V_{o} .



Figure 13-16.

- **Q11.** If the input voltage is a small-signal sine wave, then the output voltage is an amplified sine wave of opposite polarity. If the output impedance of Q1 >> RL, then the gain of the circuit is to first order the g_m of Q1 times the load resistance, $A_0 = -g_m * R_L$. With $g_m = I_c/V_t$ the gain can be rewritten to $A_0 = -I_c R_L/V_t$. Recognizing that $I_c R_L = 260 \text{mV}$, the equation becomes $A_0 = -260 \text{mV}/V_t$ or $A_0 = -260 \text{mV}/26 \text{mV} = -10$.
- **Q12.** The first pole = 100Hz, the second = 10Mhz as shown in Figure 13-17.
- **Q13.** Current gain = β (β + 1)
- Q14. Knowing that $I_D = I_{DSS} (1 V_{gs}/V_p)^2$, set up simultaneous equations and solve for $I_{DSS} = 9.8$ mA and $V_p = -2.45$ V.
- Q15. The gain = $(g_m n$ -channel/ $g_m p$ -channel). Since $g_m = 2$ (K'/2 * W/L * Id)^{1/2} and the mobility of the N-channel is approximately 3 times that of the P-channel and Id is the same for both transistors, the gain = $(3 * 12)^{1/2}/(9)^{1/2} = 12$.



- Q16. The time that it takes an RC circuit to go from 10% to 90% of its final value is $\Delta t = \ln 9 * RC$. If the bandwidth of the 'scope BW = $\frac{1}{2}\pi RC$, then the bandwidth BW = $\ln \frac{9}{2\pi * \Delta t} = \frac{199}{2\pi * 2ns}$ = 174MHz. Choose a 200MHz or faster 'scope. To reduce errors, choose a 'scope 3 times faster than the calculated value, or 600MHz.
- Q17. The average noise voltage squared, $V^2 = 4kTR \Delta f$, so $V \sim 4nV/(Hz)^{1/2}$.
- **Q18.** The required $\theta = (150^\circ 25^\circ)/25 \text{ W} = 5^\circ/\text{W}$. Since the package has a thermal resistance of 3°C/W, the heat sink must be a minimum of $\theta = (5^\circ\text{C/W} 3^\circ\text{C/W}) = 2^\circ\text{C/W}$.
- Q19. The equation for an exclusive-or gate is Y = ab' + ba'. This can be rewritten as Y = [(ab')' (ba')']'. The logic diagram is shown in Figure 13-18.

Q20. b



NUMBER CORRECT RECOMMENDATION

1–5	Become a bond trader.
6-10	Buy a copy of Gray and Meyer. Memorize it.
11-15	Not bad; call up National Semiconductor.
16-19	You have a future as an analog engineer.
20	Give me a call. I know a great boardsailing spot where we can sail and discuss job opportunities.