

wireless world circard

Set 20: Transistor pairs

Tweedledum's query seems an especially appropriate way of starting the following article on transistor pairs. Not only are the advantages of each configuration not always clear, but sometimes it's difficult to see the true operational nature of the configuration. In the cards, 20 different connections of two transistors are described, excluding c.m.o.s. circuits and triple or mixed pair arrangements. This set of circuits is an important one in that many form the basic building bricks of integrated circuits—long-tailed pairs, current mirrors, and even cascode circuits and high-gain pairs. Both the article and card 4 discuss the merits of the different long-tailed pair configurations, the card giving useful formulae for gain, common-mode rejection and temperature drift. Cards 1 & 2 contain a thorough investigation of the properties of high current gain pairs—Darlington, complementary Darlington and four-terminal pairs—the results being given in the 16 graphs, all of course derived from the compiler's measurements. Various circuits can be developed by mixing various pairs and two examples are given on card 9. One uses a long-tailed pair with constant-current tail feeding a current mirror to produce a triangular-wave generator; the other is an operational amplifier using bipolar and m.o.s. devices with a single supply.

The complementary transistor switch of card 6 is the transistor equivalent of unijunction and thyristor switches, but has the advantage of being faster than either as high-speed transistors can be used. Other cards show how the current capability of a c.m.o.s. inverter can be simply increased (card 8); how a cascode circuit is re-arranged to avoid the need for a biasing voltage (card 3); and card 5 gives performance and descriptions of m.o.s. and bipolar current mirrors—now an integral part of operational amplifiers.

- High current-gain pairs—I 1
- High current-gain pairs—II 2
- Cascode amplifier 3
- Long-tailed pair 4
- Current mirrors 5
- Complementary switching transistors 6
- Complementary emitter-follower 7
- CMOS circuits 8
- Triples and mixed pairs 9
- Pot pourri 10

Transistor pairs

"Supplementary or complementary, opposites or composites?" asked Tweedledum. "Contrariwise", said Tweedledee. It is not the intention to rewrite "Alice...", but it is not always clear what the advantages are in d.c.-coupled pair configurations—voltage gain plus impedance change, super current-gains, p-n-p simulation, thermal compensation or perhaps a current source as a stabilizing network.

The *pièce de resistance* might be the long-tailed pair or differential amplifier (where would the linear i.c. be without it?) which provides some satisfying amplifying properties—some possible variations for small-signal operation are shown in Fig. 1. For example, the connection shown in Fig. 1(a) converts a signal difference between two inputs to equal, but antiphase collector signals. Signals common to both inputs (e.g. superposed noise signals from the same source) are reduced without affecting the differential gain, which is that due to a single transistor.

The ability of this amplifier to prevent amplification of a common signal is called the common-mode rejection ratio, being the ratio of the differential voltage gain to the common mode gain, usually expressed in dB. The single-ended inputs of Fig. 1(b) and (e) produce an output at Tr_2 collector, equivalent to Tr_1 as an emitter-follower driving Tr_2 as a common-base amplifier. In addition, the output of Tr_1 is equal in magnitude but antiphase to that of Tr_2 , on the assumption of constant total current (long-tail). Hence the differential output in Fig. 1(b) is twice the single-ended output. The voltage gains are approximately R/h_{ib} and $R/2h_{ib}$ for Fig. 1(b) and (e) respectively, where h_{ib} is the effective input resistance of the common base configuration. Fig. 1(c) and (f) are not used as amplifiers, but are useful as a means of determining the gain to common mode signals. This should be much less than unity to give good rejection.

The common-emitter, common-base, connection shown in Fig. 2(a) is the cascode amplifier, where the first stage transistor Tr_1 has current gain, and the second stage Tr_2 has voltage gain. The advantages are a large gain-bandwidth

product and also, for high voltage outputs, the high breakdown value of the common base transistor Tr_2 is essential.

The common collector-common collector pair of Fig. 2(b) is the familiar

Darlington connection, where the effective current would be approximately β^2 , if the transistors were identical. This would be true for short-circuit outputs, but a practical value for the β of each transistor

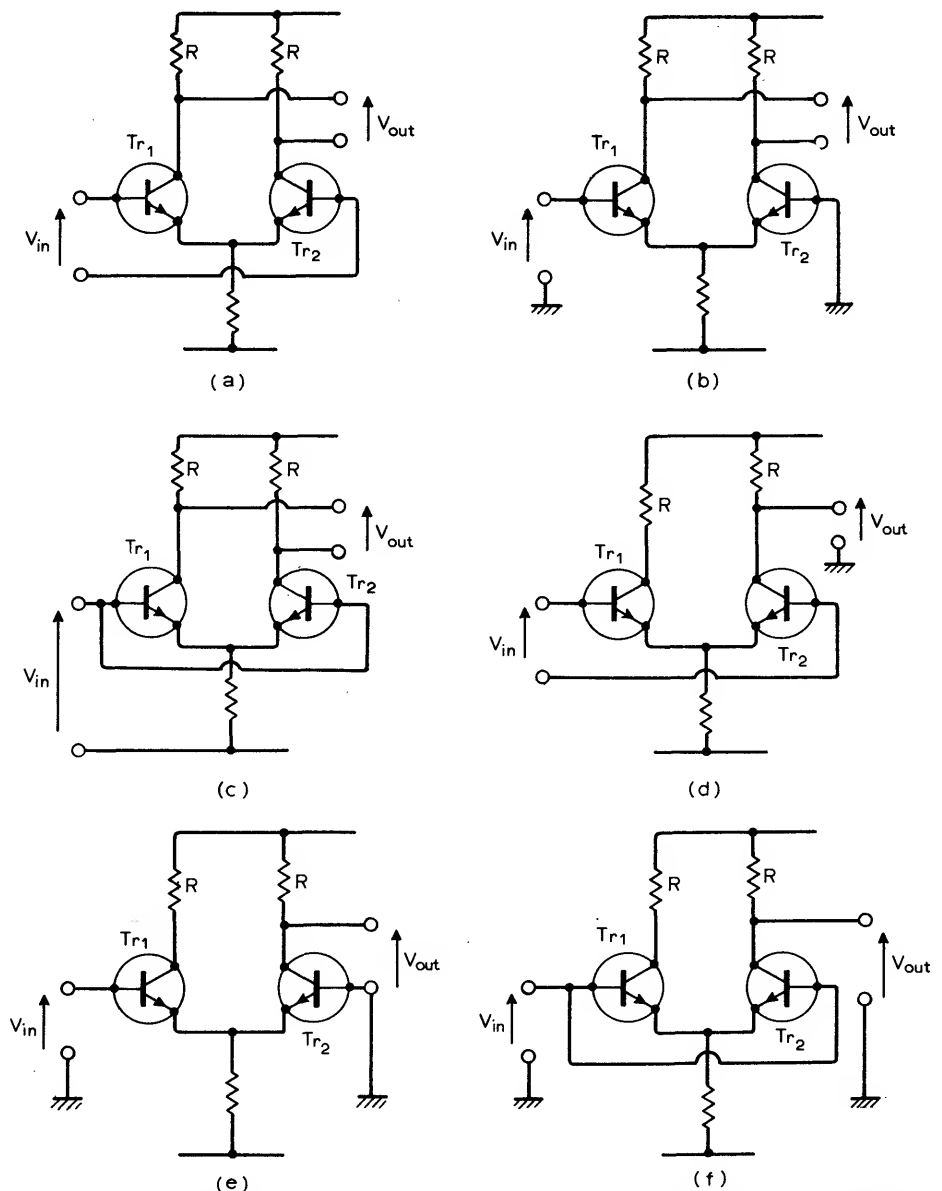


Fig. 1. Variations of the long-tailed pair include circuits with differential input, differential output (a), single input, differential output (b) & (c), differential input, single output (d), and single input and output (e) & (f).

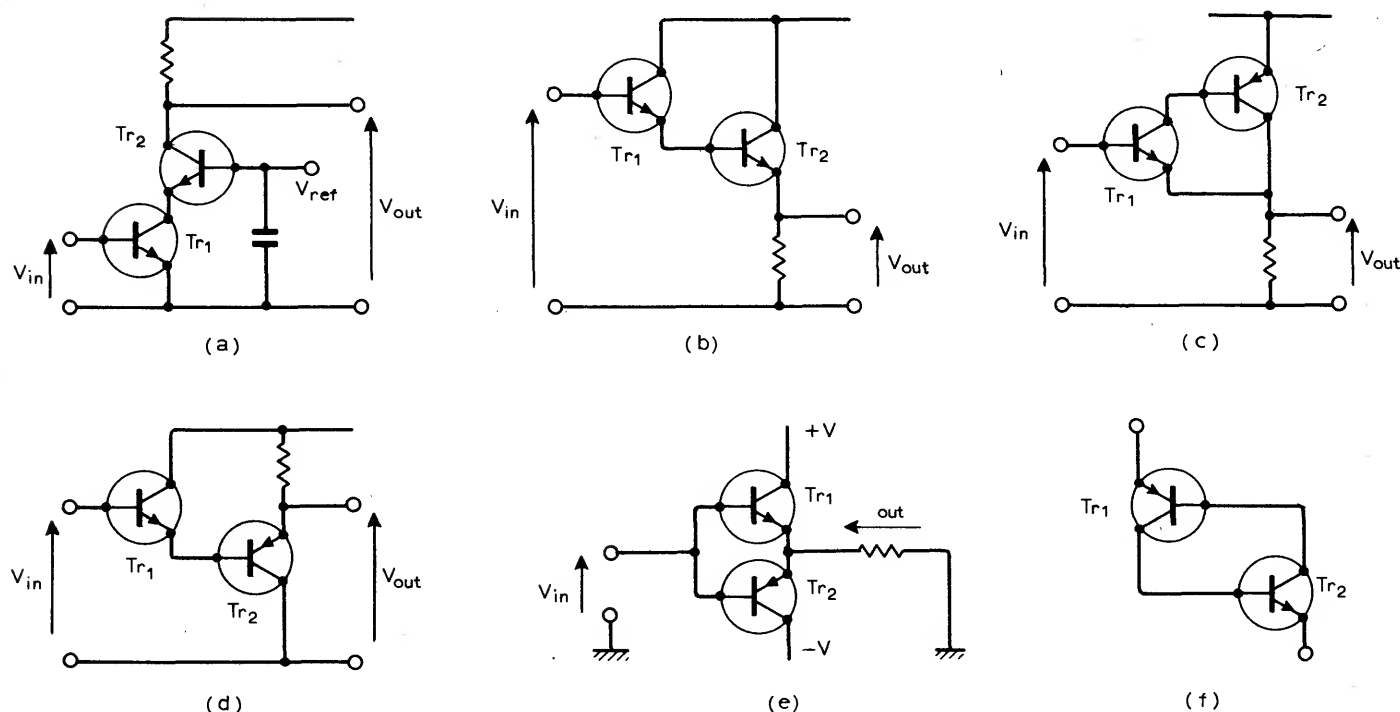


Fig. 2. Other ways of connecting two transistors are common-emitter, common-base i.e. cascode (a), common-collector pair i.e. Darlington (b), complementary pair with only one V_{be} drop (c), complementary pair with no V_{be} drop (d), symmetrical complementary pair i.e. class B amplifier (e), and the regenerative pair (f).

would be to specify the minimum value quoted by a manufacturer (assuming that discrete transistors are being discussed, because it must be remembered that super- β packages are also available with defined current gains). The complementary connection of Fig. 2(c) provides only one V_{be} drop compared with Fig. 2(b), and that of (d) cancels the V_{be} drops, but offers some second-order residual offset between input and output, and requires a separate bias path (not shown) for Tr_1 emitter current and Tr_2 base current. Complementary versions may provide an advantage, in that the transistor choice for the first stage can be that with the highest current gain at low currents.

When opposite types of transistors are connected in complementary form, such as Fig. 2(e), we have the basis of a class-B amplifier. The circuit for each half-cycle of signal is essentially identical, and the load is driven from a low-impedance source, because each transistor acts as an emitter follower. An advantage is that interstage and output transformers are not necessary when such a circuit is used at audio frequencies.

The interconnection of n-p-n and p-n-p transistors as in Fig. 2(f) provides a regenerative switching action due to the positive feedback between collectors and bases. It is similar in operation to a unijunction transistor, and there are of course similarities with the thyristor. Switching speeds can be faster than a single unijunction device because high-frequency transistors can be employed. The same arrangement is the basis for a constant-current circuit (Circards set 6, card 5), while those sources which may


be classed as current controlled tend to use the current-mirror—no self-respecting operational amplifier would be without one!

The complementary-symmetry m.o.s. pair has been an excellent addition to the pair family. Besides being the basis of several logic gates, it also has application in multivibrators and as a linear amplifier.

A close study of most linear integrated-circuits will reveal the use of two or more of the pairs mentioned, to provide a composite arrangement which offers advantages that no single transistor or pair can do.

High current-gain pairs—1

Darlington pair

 

Components


Tr₁: BFR41 Tr₂: TIP3055

Description and characteristics


A Darlington pair as shown above is a frequently used two-transistor circuit, the purpose being to obtain high gain through cascading two transistors. Because large currents are obtained in the second transistor one frequently finds this to be a power transistor and that the arrangement is used in many switching applications. As the circuit has only three

terminals it can be regarded as a single high-gain transistor. The basic action is that I_B produces, through Tr₁, a large base drive for Tr₂. The total I_C is the sum of the two collector currents although the contribution of Tr₁ to I_C will be small if the gain of Tr₂ is large.


The characteristics obtained for the components quoted are as shown. From graph 1 we obtained an h_{oe} of about 25mS and an h_{fe} of about 11,000. Graph 2 shows an h_{ie} of around 70. These figures are in line with theory (see reference). Graph 2 also shows the dependence of I_C on I_B , the two graphs being indistinguishable because of the scales chosen. For switching applications the value of V_{CE} is important. V_{CEsat} is defined as that V_{CE} corresponding to an arbitrarily

 


Graph 1

 


Graph 3

 

Graph 2

 


Graph 4

 

Graph 5

low I_C/I_B ratio, in this case 1,000 (graph 3). With higher I_C/I_B ratios, corresponding to lower I_B values the value of V_{CE} will be lower. The corresponding graph of V_{BESAT} is shown in graph 4. Graph 5 shows the dependence of h_{FE} on I_C , the drop in h_{FE} at high I_C being due to saturation and that at low I_C being due to lack of base drive to Tr₁.

Complementary Darlington pair

 

Components

Tr₁: BFR81
Tr₂: TIP3055

Description and characteristics


The basic action of this circuit is the same as that of the normal Darlington pair. Note that the circuit in this format is acting as a single p-n-p transistor. An n-p-n version is shown below. It is the input transistor which indicates whether the combination is p-n-p or n-p-n but one can readily check the bias voltages.

Graph 1 shows the output characteristics: not eminently suitable for a small-signal amplifier, but as the circuit tends to be used for switching applications this is not too serious. We obtained for these components an h_{fe} of 8,500 approx and an h_{oe} of greater than 0.1S.


Graph 2 shows I_B and I_C against V_{BE} and these again coincide because of the scale chosen. Note in this case that V_{BE} during conduction is about 0.7V as opposed to 1.5V for the normal Darlington; this is due to the fact that there is only one junction between b and e. This shows up again in graph 4.

By the same token, the graph of V_{CEsat} (graph 3) is much the same as that for the normal Darlington.


Graph 5 again has much the same shape as that for the normal Darlington though with a lower maximum value, which is in line with the reduced h_{FE} .

 


Graph 1

 


Graph 3

 

Graph 2

 

Graph 4

 

Graph 5


Further reading

Burwen, E. High-gain triple Darlington has low saturation voltage, *Electronics*, 3 Oct., 1974.

Reference

Ajdler, J. Transistor circuits, *Electronic Engineering* 1965, p.757. See also p.338 and p.112, same year.

High current-gain pairs—2

 

Components

Tr₁: BFR41Tr₂: TIP3055


Performance and description

The Darlington circuits on card 1 are both super β circuits but have the additional characteristic that they only have three terminals and so can be regarded as a single transistor. The circuit shown above also has high gain but has four terminals, three of which can


be regarded as base, emitter and collector, the fourth being connected to a voltage which gives some control over the characteristics. The principal difference in performance of this circuit is that a low saturation voltage is obtained. From graph 1 we obtained an h_{fe} of 7,000 and an h_{oe} of 25mS for $V_s = 2.0V$.

Characteristics for $V_s = 4.0V$ are virtually identical. Graph 3 shows the low $V_{ce\text{sat}}$ values obtained, slightly lower values being obtained for $V_s = 4.0V$.


Graph 4 shows the expected $V_{BE\text{sat}}$ values around 1.5V since two base-emitter junctions are between b and e. Again slightly lower values are obtained for $V_s = 4.0V$. The graph of h_{FE} is shown in graph 5, the figures being in line with

 


Graph 1

 


Graph 2

 

Graph 3



 


Graph 4

 

Graph 5

   the previously obtained h_{fe} . Note that in this configuration Tr₁ will have supply voltage V_s across it and will normally require a current-limiting resistor in its collector lead.



Components

Tr₁: BFR81Tr₂: TIP3055

Circuit description

First given by Baxandall and Shallow, this circuit has a gain producing action similar to that of the Darlington's and the circuit overleaf. Base current to Tr₁ produces large base drive to Tr₂ thereby giving large gain. In this case, however, bias (I_1) must be provided for correct action. As there are more than three terminals it cannot be considered as identical to a single transistor, and it displays some characteristics

that one does not obtain with single transistors. In particular, one obtains collector current I_c in the absence of any V_1 , this being due to the action of I_1 . The characteristics shown were obtained with a V_{CE} of 1V and exhibit an overall gm of 6A/V, obtained at V_1 of zero. The components used were chosen for comparison with the other super β pairs but certain features would dictate other choices. For example, the circuit simulates a p-n-p transistor whilst having an n-p-n output stage. In monolithic i.c.s with lateral

transistors, n-p-n transistors have low gain so that Tr₁ would dictate the overall gain. As Tr₁ has a very low voltage across it, viz V_{be} of Tr₂, then Tr₁ can be made to have high gain—see MC1538R. When used as shown above right, the circuit exhibits extremely high output resistance which, allied to the high current gain, gives large voltage gain. The reason for this is that $v_1 = v_3 + v_2 + v_{in}$ and as v_3 and v_2 cancel, both being base-emitter voltages, then $v_1 = v_{in}$ and the current in R_L is thus defined by I_1 and the current in R , no matter the


value of R_L .

The circuit therefore, must have a large output resistance. Values as high as 50M Ω have been quoted.

Further reading

Baxandall, P. J. and Shallow, E. W. Constant-current source with unusually high internal resistance and good temperature stability; *Electronics Letters* vol. 2, p.351 1966. Jager, R. C. A high output resistance source, *IEEE Journal of Solid-State Circuits*, Aug. 1974, pp.192-4.

Cascode amplifier

 

Components

Tr₁, Tr₂: BFR41


V_s: 10V

Z: 660mH coil plus stray capacitance plus c.r.o. loading

C: coupling capacitor

R_B: see graph

V_o: see graph

 

Circuit description

Tr₁ is a common-emitter amplifier which is feeding Tr₂ in common-base mode. The load on Tr₁ is therefore a near short-circuit a.c.-wise. In addition, the current gain of Tr₂ is near unity but its output impedance is high, due to the common-base mode of operation. The combination therefore shows the gain characteristics of a short-circuited c.e. stage plus the output impedance characteristics of c.b. It is therefore ideally suited for the driving of tuned resonant loads or indeed of any high impedance load.

The basic equations are

$$I_c = g_m V_{in}$$

$$I_c \approx I_L$$

$$g_m = I_c / 26 \text{ mV}$$

$$V_o = Z_L I_L$$

The second equation assumes unity current gain through Tr₂ and the last equation assumes that h_{ob} (for Tr₂) is very low.

The net result is

$$V_o / V_{in} = g_m Z_L$$

Since I_c is almost linearly related to I_B , particularly if V_{CE} of Tr₁ is constant which it is in this case, then g_m is controllable by R_B . The net result is the graph shown. For each result the circuit was retuned for resonance, the change in resonant frequency being around 1.5% over the complete range.

With $R_B = 1 \text{ M}\Omega$, the resonant frequency was 924 kHz and the bandwidth 18.5 kHz giving a Q of 50. V_R is not critical—it is only required to produce correct transistor action. In these results it was 3V. A 1.5-nF supply decoupling capacitor was necessary. Note that the graph represents

a range of voltage gain from 50 dB to 71 dB and that the range of R_B is 20:1.

The circuit above has two disadvantages viz, it is not a three-terminal device and also requires a biasing voltage. The above circuit suffers from neither of these disadvantages. The circuit is self-biasing provided only that I_c is less than I_A by an amount sufficient that the resulting V_{gs} keeps the bipolar transistor well out of saturation. Typically V_{ce} would need to be in the range 0.2 to 1.0V (though a higher value would be preferable for higher gain).

This means that the operating current is restricted to the I_A of the f.e.t. with V_{gs} in the range of -0.2 to -1.0V. In practice the current is defined by some other requirement (drift, matching etc) and is often much less than I_{dss} —the f.e.t. current with $V_{gs} = 0$ (which would give no gain from the bipolar anyway). The f.e.t. will frequently be required to operate near pinch-off.


The circuit, above centre, is a less common form which loses the merit of low capacitive feedback. It does, however,

have the merit of increased current capability since the f.e.t. can operate with $V_{gs} = 0\text{V}$.

The circuit right is of a form found as the input of some commercially available differential amplifiers. Each two-transistor block can be regarded as a single transistor and the circuit is then recognisable as a long-tailed pair. The tail uses the high output impedance of the pair to provide an excellent constant-current source the other two pairs being used for their high voltage gain.


Cross references

Set 20, cards 4, 10.

 

Long-tailed pair

(a) Differential in-differential out

 


Circuit description

This emitter-coupled differential amplifier should have a large value for R_4 to provide a high common-mode rejection ratio (c.m.r.r.). This implies that the differential output voltage between collectors for a common signal at the bases, is very small and ideally zero. In general, the output signal depends on the difference between the signals at the

transistor bases. Each transistor receives half the signal i.e. the gain to each output is half of that provided by a single transistor under the same conditions.


Performance data

 Tr_1, Tr_2 : matched pair from CA3086. R_1, R_2, R_4 : 100k Ω .
 R_3, R_5 : 150k Ω , RV_1 : 1k Ω
 V_8 : $\pm 15V$



Gain slope: typically 230.
 Variation in gain: $\pm 1\%$ for several choices of CA3086.
 Reducing R_1, R_2 by similar ratios will maintain slope at same order of magnitude.

(b) Single-ended in, differential out

 

V_{in} : 10mV d.c. (20mV)
 V_{out} : 2.39V d.c. (4.79V)
 i.e. gain slope similar to (a)

$$\frac{\Delta V_{out}}{\Delta V_{in}} = 240$$


For single-ended output:

V_{out} = voltage between X and ground.

$$\frac{\Delta V_{out}}{\Delta V_{in}} = \frac{10.28V - 9.06V}{20mV - 10mV} = 122.$$

i.e. gain is halved.

(c) Common mode input

 

$$\frac{\Delta V_{xy}}{\Delta V_{in}} = \frac{0.149 - 0.142}{2 - 1} = 0.007$$

For single-ended output (terminal X to ground):

$$\frac{\Delta V_{out}}{\Delta V_{in}} = 0.0045$$

c.m.r.r. improved by trimming R_1, R_2 for zero balance. Figure of merit is c.m.r.r. or voltage gain for differential inputs divided by voltage gain for common-mode inputs that is 0.007/230.

Useful relationships

Bipolar transistor collector current related to base-emitter voltage by

$$I_C \approx I_S \exp qV_{BE}/kT$$

$$\frac{dI_C}{dV_{BE}} = \frac{qI_C}{kT} = g_m$$

At room temperature

$$g_m \approx \frac{I_C}{26} \text{ (mA/V)}$$

$$v_{C1} = -g_m \frac{v_{in}}{2} R_C$$


$$v_{C2} = -g_m \frac{-v_{in}}{2} R_C$$

Differential output given by



$$v_o = v_{C1} - v_{C2} = -g_m v_{in} R_C.$$

Voltage gain A_v
 
$$= v_o/v_{in} = -g_m R_C = -I_C R_C / 26 = -V_C / 26.$$



  Differential input signal can be considered as




This single-ended input signal can be considered as the algebraic sum of differential and common-mode signals:

$$\text{i.e. } v_{in} = v_{in}/2 + v_{in}/2$$

$$\text{and } 0 = \underbrace{v_{in}/2}_{\text{common mode}} - \underbrace{v_{in}/2}_{\text{differential mode}}$$

 If c.m.r.r. high, effect of common-mode signals negligible. Hence single-ended input equivalent to differential input.



For identical transistors the collectors are at equal potentials for common-mode signals. Hence they can be considered connected together

$$v_{out} \approx \frac{-v_{in}}{R_E} \cdot \frac{R_C}{2}$$

Note: If R_E replaced by a constant-current circuit, $v_{out(cm)}$ can be $\ll 1$.

$$\text{c.m.r.r.} = \frac{-g_m \cdot R_C}{R_C/2R_E} = \frac{-g_m R_E}{2}$$

Temperature drift

For a pair of identical transistors, balanced to provide zero difference between the base-emitter voltages of each, then the temperature drift is

theoretically zero—a basic advantage of the differential mode.

$$V_{BE} \approx \frac{kT}{q} \log \left(\frac{I_C}{A T^r} \right)$$

A is dependent on transistor area. Two transistors on same chip, but different areas, provides a V_{BE} variation given by

$$\Delta V_{BE} = \frac{kT}{q} \log \left(\frac{A_2}{A_1} \right)$$

Temperature drift is

$$\frac{d\Delta V_{BE}}{dt} = \frac{k}{q} \log \left(\frac{A_2}{A_1} \right) = \frac{\Delta V_{BE}}{T}$$

At room temperature (300K) drift is 3.3 μV /deg C for each mV of initial offset.


Further reading

Thermal variation of the emitter-base voltage of bipolar transistors. Widlar, R. J. *Proc. IEEE* Jan. 1967.

Limits of temperature drift in non-compensated d.c. amplifiers. *IEEE Journal of Solid-State Circuits*, Feb. 1970.

Cross reference
 Set 12, card 10


Current mirrors

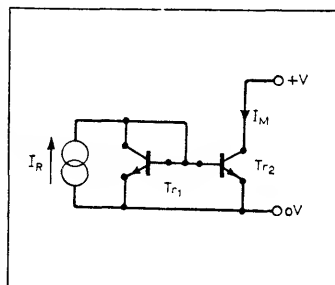

Typical data

Tr_1, Tr_2 : part of CA3086
 I_R : 1mA from commercial current generator, $\pm 0.05\%$
 I_M : measured using 4-digit multimeter.

 Curves opposite show R_o and R_D as functions of $+V$.



Description (bipolar)

The current mirror is an extremely useful two-transistor circuit extensively used as an integral part of monolithic operational amplifiers to define one current, the mirror current I_M , in terms of a reference current I_R . With identical transistors the base-emitter voltages are identical and if Tr_2 has a high current gain the collector currents I_R and I_M



are matched, to a first order. Any matched pair of n-p-n transistors may be used but those on a single chip are preferred; the variable temperature sensitivity of discrete device reduces reliability of the circuit. An important requirement in many applications of the current mirror is a high output resistance. The left-hand graph above shows that the static

output resistance ($R_o = V/I_M$) increases with V for a given reference current value. However, the right-hand graph shows that whilst the dynamic output resistance ($R_D = \delta V / \delta I_M$) also increases with V , the far more rapid rise in R_o causes the ratio of dynamic to static output resistance to fall rapidly with increasing V . Hence, a compromise must be made between the values of R_o and

R_D to be used with a given value of I_M .

For currents in the microamp range the output resistance of the current mirror can be increased by inserting a negative feedback resistor in the emitter lead of Tr_2 .

 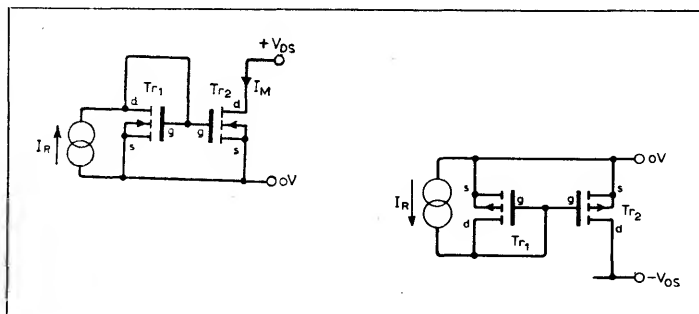For higher current requirements, transistors on the same chip can be connected in parallel to increase the junction areas.



Description (m.o.s.)

Current mirror circuits can also be produced using m.o.s. transistors, the basic form using n-channel devices shown above left. Transistor Tr_1 is diode-connected performing as a transistor with 100% feedback. Thus its drain current is still controlled by its gate-source voltage V_{GS} , i.e. $I_D \approx g_{ss} V_{GS}$ where g_{ss} is the forward transconductance. Forcing a current I_R into this diode-connected transistor causes V_{GS} to rise until a state of equilibrium is attained when Tr_1 sinks the reference current. The gate-source voltage of Tr_2

is identical to that of Tr_1 , due to the parallel connections. Hence if both have identical characteristics, Tr_2 is also capable of sinking an identical current, the mirror current I_M . A reasonably good degree of matching can be obtained between the n-channel devices on a monolithic chip, the mirror current being typically within 10% of the reference current.

A current mirror using monolithic p-channel i.g.f.e.ts, shown centre left, provides better performance than the n-channel type due to the ability to provide much closer

matching of the characteristics of p-channel devices. Such a circuit provides an I_M/I_R ratio which is to a first order independent of V_{DS} , as shown centre right.

The graph above right shows that the normalized ratio of I_M/I_R is within 1% of its nominal value over a wide range of ambient temperatures and I_R values.

Further reading

Jaeger, R. C. High output resistance current source, *IEEE Journal of Solid-State Circuits*, pp.192-4, August, 1974.

RCA Solid State Databook SSD-201B, pp.183-8 and 213-25, 1974.


Hart, B. L. Bidirectional *Wireless World*, vol. 76, 1970, pp.511-4.

Hart, B. L. Bidirectional current source, *Electronics Eng.* pp.39-41, July, 1974.

Cross references

Set 3, card 9.
 Set 6, card 4.
 Set 9, card 5.
 Set 10, cards 1, 3, 7.
 Set 12, cards 4, 7.
 Set 15, card 6.
 Set 16, card 1.

Complementary switching transistors

 


Components

Tr_1 : BFR81, Tr_2 : BFR41
 R : 1k, 10k Ω

Performance

Slope in negative resistance region 0.75k Ω and 8k Ω for $R=1k\Omega$ 10k Ω respectively (see graph).



Initially with low I , V may be considered as $V_{BE1} - V_R + V_{BE2}$. As V_R is low initially V is the sum of the two exponential emitter-base voltages. As I increases these two voltages tend to 0.6V but V_R continues to rise and because of the minus sign V starts to fall, at a value slightly less than 1.2V. The fall continues (negative resistance region) until both transistors saturate. At this point we can no longer assume that all the current is passing

 

through both collectors and R and we are best to view V as being $V_{EC1} + V_R + V_{CE2}$. Since the two transistor voltages are relatively fixed, V then starts rising again. The value of the trough is given by $V_{EC1sat} + V_{BE2sat} \approx V_{BE2sat}$. The voltage range of the circuit is readily increased by the modification shown opposite with Zener diodes appropriate to the application.

These circuits are described as being open-circuit stable, i.e. for any current drive there is a unique voltage. The dual of this is the voltage driven, short-circuit-stable device. An

  f.e.t. realization of this is shown with the corresponding characteristic (see Further reading).



Circuit description

The circuit shown overleaf, with $R=\infty$, is the basis of simulated thyristors, silicon controlled switches and simulated unijunction transistors. The action, with $R=\infty$, can be deduced from the V-I graph shown, bearing in mind that the negative resistance slope is now $-\infty$. Alternatively, the circuit above can be considered as follows. Initially Tr_1 and Tr_2 are in the non-conducting state. A positive voltage of about 0.7V on the base of Tr_2 causes that transistor to conduct and lower its collector voltage. This causes

Tr_1 to conduct and providing Tr_1 and Tr_2 produce sufficient current through R_2 and R_1 respectively to keep the transistors conducting, then the action is self-sustaining with a voltage of approximately one V_{BE} across the circuit. The circuit can thus be used as a switch, triggered by a suitable voltage at either base. With $R_1=R_2=1k\Omega$ a value of 1.3mA for I was found to be the minimum which would maintain conduction. This value is as expected as the current I will split fairly evenly between Tr_1 and R_1 and Tr_2 and R_2 . Since approximately

0.65V is required at the base of each transistor to maintain conduction, it will be provided by 0.65mA in each path.

For high-speed switching it is important to prevent the transistors from saturating. Addition of the anti-saturation diodes shown prevents the collector voltages from dropping below V_{BE} . The base lead diodes are not essential. Increasing R_1 increases the trigger voltage necessary and reduces the effect of trigger point transients.

Transients in the supply line give rise to false triggering due to rate effect. This can be reduced as R_2 is reduced although this increases the holding current necessary.


Further reading

G.E. Transistor Manual.
 Sharma, S. M. Current-controlled negative resistance circuit. *Int. J. Electronics*, 1974, vol. 37, pp.209-18.
 Negative resistance shown in dual f.e.t. device, *Electronics*, April 18, 1974, p.5E.

Cross references

Set 10, card 5.
 Set 8, card 3.
 Set 6, card 9.
 Set 3, card 4.

Complementary emitter-follower

 

Typical data

$V_s: \pm 6V$

$T_1: \text{BFR41}, T_2: \text{BFR81}$

$R_1: 330\Omega, R_2: 1k\Omega$

Signal frequency: 1kHz

Fundamental/3rd harmonic output/input shown on graphs

Circuit description

The basic circuit comprises a complementary n-p-n/p-n-p pair operating under class-C bias, and is the basis for many audio power/amplifiers. When a positive-going input signal exceeds about 0.7V, transistor Tr_1 will turn on, increasing its collector current which develops a voltage across the load R_2 , but with a voltage gain of less than unity. At the same time Tr_2 is biased off. Similarly, a negative-going input signal turns Tr_2 on and Tr_1 off, and the circuit thus provides bidirectional currents through the emitter load. The base-emitter diode characteristic is non-linear at low voltages, resulting in cross-over distortion (approximately $2V_{BE}$) across the load. The resulting distortion on a sine wave input is shown in Fig. 1. Without an additional bias network, the effect of this distortion can be minimized by ensuring that $V_s \gg V_{BE}$. Using both positive and negative power supplies permits operation down to zero frequency. For a single supply a capacitor is required in series with the load, to provide the base and collector currents of Tr_2 during negative-going input signals.

Component changes

R_2 : Range from 100 to $1k\Omega$.

Variation in gain minimal.

Frequency: Up to 30kHz, little difference from lower frequency operation.

Variation of mean current with input level in Fig. 2.

R_1 : Chosen to suppress

parasitic oscillations. Alternative may be to keep interconnections very short to minimize series inductance.

Effect of bias (Figs. 5 & 6)

R_B varied until transistors just on the point of conduction. Graph shows 3rd harmonic distortion optimized by R_B .

The above is a basic method of biasing to ensure class B or AB operation. Diodes D_1, D_2 may be chosen to achieve temperature independence of quiescent current.

Where increased current gain is needed for high power outputs, the Darlington pair of Fig. 8 (a) and compound emitter followers of (b) and (c) are useful, but may provide more difficult biasing problems.

Line driver (Fig. 7)

Driving 50- Ω cable with line capacitance slows pulse edges.

 


Fig. 5

 


Fig. 6

 


Fig. 7

 


Fig. 1

 


Fig. 2

 


Fig. 3

 


Fig. 4

Improved using complementary pair. Typical fall time $\ll 100ns$ but dependent on simulated cable capacitance ($R_o: 50\Omega$, $C: 3nF$, $t_F: 75ns$).

Further reading

Williams, P. Voltage following,

Wireless World, Sept., 1968.

Williams, G. E. Practical transistor circuit design and analysis, McGraw-Hill 1973.

Markus, T. Electronic circuits manual, McGraw-Hill.

Cross references

Set 7, cards 1, 3.

Set 20, card 1.



 


Fig. 8

 

CMOS circuits

 

Description

The c.m.o.s. inverter shown above comprises a p-type and n-type enhancement mode m.o.s. transistor on the same chip. $V_{DD} - V_{SS}$ may be in the range 3 to 15V. The pair is useful in digital circuits because of well-defined threshold that V_{in} must exceed before the device turns on.

n-type: V_{GS} positive for ON
p-type: V_{GS} negative for ON
Where the output has to sink or source current, the pair can be envisaged as the series switches. Fig. 1 is a source condition, obtained for $V_{in} = V_{SS}$ and $V_{out} = V_{DD} - I_D R_o$ where R_o is the output resistance of p-transistor in the on state. For $V_{in} = V_{DD}$, the n-type sinks current for Fig. 2; $V_{out} = I_D R_o$.

Basic i.c. package CD4007 contains one inverter and two complementary pairs with the drains unconnected. This permits a variety of interconnections: n-types are paralleled to increase sink current capability, Fig. 3. p-types are paralleled to increase source current capability, Fig. 4.

Fig. 5 is a dual bi-directional transmission gate where the two outputs and input may be interchanged for two inputs and one output. Note that the position of the transistors in the middle pair have been reversed.

The CD4049 package contains six inverters with current drive capability almost an order of magnitude greater than basic package. Parallel connection for increasing current sinking indicates typical current sharing for d.c. condition, Fig. 6.

 


Fig. 1

 


Fig. 2

 


Fig. 3

 


Fig. 4

Fig. 6

 
 


Fig. 5

CD4016 i.c. package contains four analogue switches (transmission gates). Each switch comprises an inverter and a parallel pair of n- and p-channel transistors, Fig. 7. For a threshold of approximately 2V in each

channel and control voltage 10V, the gate control voltage of the p-m.o.s. is 0V. If $V_{in} > 8V$, the n-channel will be open, but the gate-source voltage of the p-m.o.s. is $-8V$ (greater than threshold) and signal is switched through.

Because the V_{GS} of each transistor never equals the threshold of the transistors, the full supply range can be switched through.

A.C. amplifier (Fig. 9)

Best linearity and voltage swing if $V_{out} = V_{DD}/2$ and this is provided by the resistive connections (Figs. 9 & 10). Supply drain $\approx 2mA$ for 10V supply.

Further reading

RCA Solid-State Databook Series SSD—203A 1973.
Design Ideas with COS/MOS *New Electronics*, April 30, 1974.
I.C. op-amp has CMOS output *Electronics*, Sept. 19, 1974.
Fitchen, F. C. and Ellerbruch, V. G. Linear operation of the MOSFFT complementing pair, *IEEE Journal of Solid-State Circuits*, Dec., 1971.

Cross references

Set 8, card 1.
Set 10, card 7.
Set 11, card 5.
Set 12, card 1.

 


Fig. 7

 


Fig. 8

 


Fig. 10

 


Fig. 9

Triples & mixed pairs


The principle of using transistors in pairs can often be usefully extended to the use of devices in triples, the resulting equivalent transistor having a current gain equal to the product of those of the individual transistors. In all such arrangements, two of which are shown above, the equivalent transistor has the same "polarity" as the input transistor.

The three n-p-n transistors in Fig. 1 act as a compound emitter-follower having a current gain of approximately h_{fe}^3 , for large h_{fe} , and is useful for driving currents of several amps from a driver stage delivering less than a milliamp. The complementary transistor triple in Fig. 2 is useful in voltage regulators as a low-dissipation series element,

the V_{BE} and V_{CE} values of the equivalent transistor being the lowest possible for a triple. In this arrangement the temperature coefficient of only one transistor affects the output. The operating current in the input transistor will be very small, reducing its current gain. This effect can remove much of the benefit of using a triple instead of a pair. By using resistors as shown in Fig. 3 the operating currents in the earlier stages are increased and stabilized.

Thinking of the various pairs of devices discussed on other cards as elementary building blocks can prove a powerful method of developing more complicated circuit functions. For example, a long-tailed pair Tr_1 , Tr_2 and Tr_3 may be used to drive a current mirror Tr_4 and Tr_5 as shown in Fig. 4 to produce a waveform generator which provides a symmetrical

 Typical values. Supply $\pm 10V$, V_R 0V, R_1 5k Ω , R_2 2.2k Ω , R_3 4.7k Ω , C_1 33nF, D_1 1N914, D_2 1N5234, D_3 , D_4 HP5082-2800, Tr_1 , Tr_2 , Tr_3 2N3546, Tr_4 , Tr_5 $\frac{1}{2} \times$ SL301-A. triangular output when driven by input pulses. This circuit uses the long-tailed pair to



switch a defined current into two paths; which combined with a closely-matched current mirror permits the capacitor to be charged and discharged at the same rate when the charging current is varied. This concept of mixing elementary pairs of devices can be developed to build a single-supply operational amplifier using bipolar and


m.o.s. transistor pairs, as shown in Fig. 5, having a unity-gain bandwidth of about 10MHz. The operational amplifier, which requires two CA3600E and one CA3046 packages, has three stages. The differential input stage uses two p-channel m.o.s. transistors Tr_3 , Tr_4 , the second stage uses an n-p-n bipolar transistor Tr_7 , and the output stage is a complementary m.o.s. transistor pair Tr_8 , Tr_9 . The zener network, using two diode-connected transistors D_1 , D_2 of the CA3046, feeds a p-channel current mirror Tr_1 , Tr_2 that establishes a 400 μA constant current in the input

stage. This differential-input amplifier is loaded by four resistors, R_1 to R_4 , and a bipolar current mirror, Tr_5 , Tr_6 , to provide optimum balance, any voltage offset being nulled with the potentiometer R_8 . The current in the second stage, determined by R_5 , is adjusted to equal the 400- μA first-stage current to provide similar negative and positive slew rates. The output stage is biased as a class-A amplifier by R_6 and may be driven to within a few millivolts of the ground rail. The overall voltage gain varies inversely with the load resistance which, as with a monolithic operational amplifier, would have a value

of about 2k Ω . Compensation requires inclusion of the feedback capacitor C_1 , with C_2 added when using the operational amplifier as a unity-gain follower. In this configuration, R_9 and C_3 should be added to avoid the possibility of latch up and D_3 and D_4 added to the inputs to prevent negative-going input signals exceeding about 700mV which could also cause latch up. Typical values are: $V+15V$; R_1 , R_2 , R_3 , R_4 200 $\Omega \pm 1\%$; R_5 20k $\Omega \pm 1\%$; R_6 11k $\Omega \pm 1\%$; R_7 7.5k $\Omega \pm 1\%$; R_8 10k Ω ; R_9 1k Ω ; C_1 39pF; C_2 300pF; C_3 150pF; D_3 , D_4 1N914.

Further reading

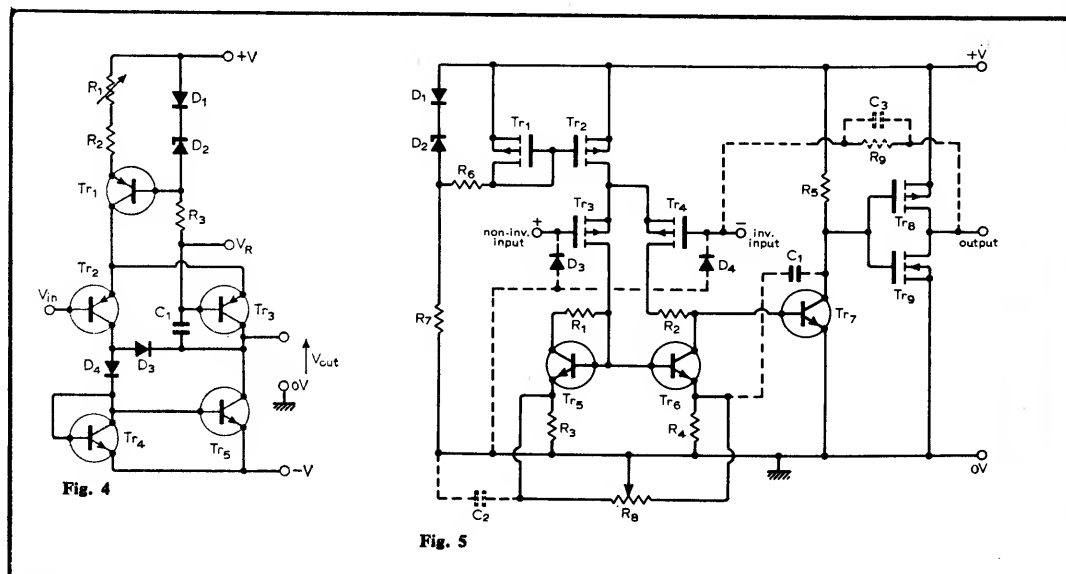Williams, P. Voltage Following, *Wireless World*, vol. 74, 1968, pp. 295-8.
Nowicki, J. R. Compound transistor connections, *Electronic Engineering*, September, 1971, p.63.
Burwen, E. High-gain triple Darlington has low saturation voltage, *Electronics*, Oct. 3, 1974.



Pot pourri


n-n-p/p-n-p simulation at high voltage

Optical couplers are used to provide fast high voltage switching with a simulated complementary pair. Transistors Tr_1 and Tr_2 are high-voltage n-p-n types: Tr_1 is on when Tr_2 is off and vice versa. With Tr_1 off, C charges to V_Z , storing charge. This is used to turn Tr_1 on fast when the optical coupler operates.

Optical coupler provides the polarity inversion when Tr_4 and Tr_5 are driven by 5V pulses.


Tr_3, Tr_4, Tr_5 : 2N2222
 R_1 : 270k Ω (10W), R_3 : 1k Ω
 R_5 : 100 Ω , R_4 : 47 Ω R_5
 R_6 : 680 Ω , C: 10nF
 D_1 : 6.8V zener, OC1: Monsanto MCO1
 Rise and fall times of around 2 μ s are claimed for components used.

Unijunction from bipolar pair

 


Tr_1 : 2N4126, Tr_2 : 2N4124
 R_1, R_2 : 4.7k Ω , V: +3 to 25V
 Because the collector current of Tr_1 is the base current of Tr_2 and vice versa, then any change of current provides a positive feedback action.
 B_1, B_2 and E are the equivalent unijunction terminals. When E is open-circuit $V_x = R_2 V / (R_1 + R_2)$.

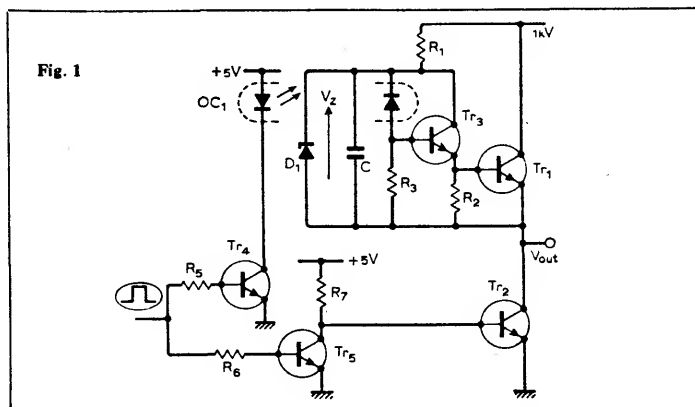When the potential at E exceeds V_{EB} and V_x , both transistors saturate, and R_2 is short-circuited. This condition is maintained for a potential at E down to $V_{EB} + V_{CESat}$ of Tr_2 . Switching speed depends on maximum frequency of operation of the transistors. For Tr_1, Tr_2 silicon drift of $V_{EB} < 3mV/deg C$.



Shunt-series d.c. feedback pair

 


Current fed back via R_f is proportional to Tr_2 collector current, and thus the circuit provides current-shunt negative feedback, which primarily controls the overall current-gain.

Effective current gain is $A_i / (1 + \beta A_i)$ where A_i is the current gain of the two stages, with R_f connected between Tr_1 base and ground. $\beta \approx R_E / R_f$. For $\beta < 0.1$, input resistance is $R_i / (1 + \beta A_i)$ where R_i is input resistance without feedback.

$$\text{Voltage gain} \approx \frac{R_f}{R_E} \cdot \frac{R_2}{R_S}$$


where R_S is source resistance. Voltage gain can be increased by by-passing R_E , or by-passing the mid-point of the feedback resistor R_f .

Series-shunt d.c. feedback pair

 


In this connection, the voltage gain is now mainly affected by the feedback, and the input resistance is increased. Voltage gain is $A_v / (1 + \beta A_v) \approx 1/\beta$ if A_v is large. A_v is the product of the gains of each stage, with R_f connected from Tr_2 collector to ground, and $\beta = R_E / R_f$. Input resistance is $R_i (1 + \beta A_v)$, where R_i is effective input resistance of the first stage. Note: Biasing networks for those CE-CE amplifiers are not shown.

 Common emitter pairs with composite transistors



 Tr_1, Tr_2 : 2N4355
 V_{CC} : 15 to 30V
 Voltage gain ≈ 100
 Cut-off frequency $\approx 10kHz$
 Input resistance $> 200k\Omega$
 By sacrificing voltage gain, a high input impedance can be obtained with the circuit shown below.



Tr_1, Tr_2 : 2N4355
 V_{CC} : +10 to 30V
 Voltage gain ≈ 10
 Input impedance: 5M Ω


Further reading for circuits 1-6

1. Mitchell, P. & Robbins, K. Simulating an npn/pnp pair for high voltage switching. *Electronics*, Aug. 22, 1974.
2. Shyne, N. A. Bipolar pair simulates unijunction, *Electronics*, Jan. 24, 1974.
- 3, 5, 6. Cowles, L. G. Transistor circuit design, Prentice-Hall, 1972.
4. Millman & Halkias, Electronic Devices and Circuits, McGraw-Hill, 1967, p.502.

Cross references

- Set 20, cards 6, 7.
 Set 12, card 9.

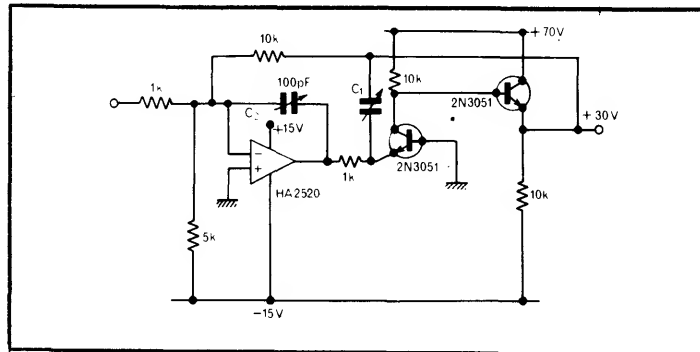1. The common-base and common-collector pair used in the d.c. feedback pair configuration has a low input impedance, low output impedance and wide bandwidth. Using high voltage transistors it is suitable as a pulse-amplifier to produce very fast positive edges even into capacitive loads (a complementary class B output stage would be needed to make the falling edge equally fast). It lacks d.c. stability but can be combined with a high speed op-amp as shown to give an output slew rate claimed in



the reference to be $200\text{V}/\mu\text{s}$ and full power output of 60V peak to peak at 1MHz . The overall feedback brings the


output stage within the loop reducing the offset and drift to that of the op-amp. The latter provides current drive

into the c.b. stage but does not need to supply a large voltage swing reducing the demands on its slew rate. The reference describes other more complex circuits capable of extending the small-signal bandwidth to 20MHz and slew-rate to $1200\text{V}/\mu\text{s}$ or even higher using special amplifiers. Precautions on layout and decoupling are given.

Reference

Bunin, H. Low-cost v.c.o. driver amplifiers really perform if designed right, *EDN*, 1974, Oct. 5, pp. 51-5.

 2. A recent paper has considered the complex behaviour of apparently simple m.o.s. transistors. If the substrate connection is available, then for a p-channel enhancement mode f.e.t. that substrate also acts as the base of a p-n-p transistors with source and drain representing the emitter and collector respectively. To a first-order approximation the devices are



shown to be independent when conducting with the total current being equal to the sum of the individual currents.


The m.o.s. action is controlled by a square-law transconductance equation, while the bipolar transistor has a collector current proportional to the base current to a first order of magnitude (low current gain in this example). Thus the waveform in a load resistor connected to a negative supply could be varied by applying an input signal separately or

jointly to the gate and substrate terminals. This parallel combination should also be amenable to other waveform processing methods by combining feedback networks with it.

Reference

Hart, B. L. and Barker, R. W. J. First-order theory of m.o.s.f.e.t. hybrid-mode operation, *Int.J. Electronics*, 1975, vol. 38, pp. 625-30.

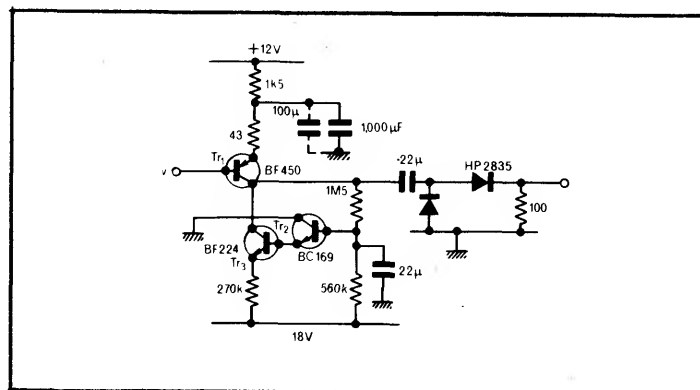3. This circuit is not strictly a two-transistor arrangement but illustrates how a circuit can be partitioned to reveal familiar pairs. It is a wide band precision rectifier that uses a high output impedance rather than negative feedback to overcome the diode non-linearities. A Darlington pair composed of Tr_2 , Tr_3 is modified to remove the collector of Tr_2 from the circuit output, by returning it to ground. This leaves Tr_3 providing a low-capacitance constant-current sink. D.c. negative feedback defines the operating points (with negligible loading because



the current gain is high allowing high-value resistors. The 43Ω resistor defines the circuit transconductance and Schottky diodes maintain

the bandwidth with minimum p.d. and hence non-linearity at low levels. Where large electrolytics are needed to extend low frequency response

(20Hz is quoted in reference) then parallel tantalum capacitors are added to maintain low impedance at high frequencies. The source has to be capable of carrying the base current of Tr_1 . The reference indicates the upper cut-off frequency as 80MHz with good accuracy to 10MHz , and good linearity and repeatability for 200mV r.m.s. full-scale.

Reference

Knott, K. F. Sensitive wideband linear a.c.-d.c. converter, *Proc.IEE*, 1975, vol. 122, pp. 249-52.