

## AC coupled (HPF) non-inverting amplifier circuit


### Design Goals

Input		Output		Supply		
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$V_{ref}$
-240mV	240mV	0.1V	4.9V	5V	0V	5V

Lower Cutoff Freq. ( $f_L$ )	Upper Cutoff Freq. ( $f_H$ )	AC Gain ( $G_{ac}$ )
16Hz	$\geq 1\text{MHz}$	10V/V
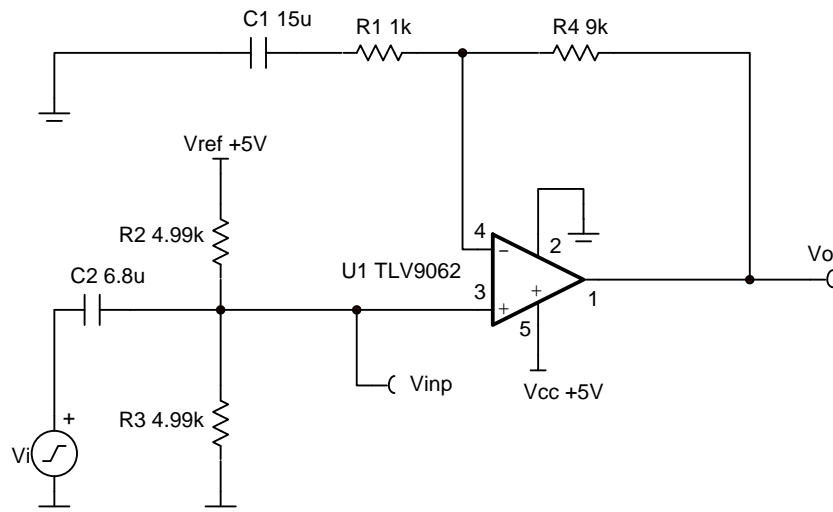
### Design Description

This circuit amplifies an AC signal, and shifts the output signal so that it is centered at one-half the power supply voltage. Note that the input signal has zero DC offset so it swings above and below ground. The key benefit of this circuit is that it accepts signals which swing below ground even though the amplifier does not have a negative power supply.



### Design Notes

1. The voltage at  $V_{inp}$  sets the input common-mode voltage.
2.  $R_2$  and  $R_3$  load the input signal for AC frequencies.
3. Use low feedback resistance for low noise.
4. Set the output range based on linear output swing (see  $A_{ol}$  specification of op amp).
5. The circuit has two real poles that determine the high-pass filter  $-3\text{dB}$  frequency. Set them both to  $f_L/1.557$  to achieve  $-3\text{dB}$  at the lower cutoff frequency ( $f_L$ ).

## Design Steps

1. Select  $R_1$  and  $R_4$  to set the AC voltage gain.

$$R_1 = 1 \text{ k}\Omega \text{ (Standard Value)}$$

$$R_4 = R_1 \times (G_{ac} - 1) = 1 \text{ k}\Omega \times (10^{\frac{V}{V}} - 1) = 9\text{k}\Omega \text{ (Standard Value)}$$

2. Select  $R_2$  and  $R_3$  to set the DC output voltage ( $V_{DC}$ ) to 2.5V, or mid-supply.

$$R_3 = 4.99\text{k}\Omega \text{ (Standard Value)}$$

$$R_2 = \frac{R_3 \times V_{ref}}{V_{DC}} - R_3 = \frac{4.99\text{k}\Omega \times 5V}{2.5V} - 4.99\text{k}\Omega = 4.99\text{k}\Omega$$

3. Select  $C_1$  based on  $f_L$  and  $R_1$ .

$$f_L = 16\text{Hz}$$

$$C_1 = \frac{1}{2 \times \pi \times R_1 \times \left(\frac{f_L}{1.557}\right)} = \frac{1}{2 \times \pi \times 1 \text{ k}\Omega \times 10.3\text{Hz}} = 15.5\mu\text{F} \approx 15\mu\text{F} \text{ (Standard Value)}$$

4. Select  $C_2$  based on  $f_L$ ,  $R_2$ , and  $R_3$ .

$$R_{div} = \frac{R_2 \times R_3}{R_2 + R_3} = \frac{4.99\text{k}\Omega \times 4.99\text{k}\Omega}{4.99\text{k}\Omega + 4.99\text{k}\Omega} = 2.495\text{k}\Omega$$


$$C_2 = \frac{1}{2 \times \pi \times R_{div} \times \left(\frac{f_L}{1.557}\right)} = \frac{1}{2 \times \pi \times 2.495\text{k}\Omega \times 10.3\text{Hz}} = 6.4\mu\text{F} \rightarrow 6.8\mu\text{F} \text{ (Standard Value)}$$

5. The upper cutoff frequency ( $f_H$ ) is set by the non-inverting gain of this circuit and the gain bandwidth (GBW) of the device (TLV9062).


$$f_H = \frac{\text{GBW of TLV9062}}{G_{ac}} = \frac{10\text{MHz}}{10^{\frac{V}{V}}} = 1 \text{ MHz}$$

**Design Simulations**

**AC Simulation Results**

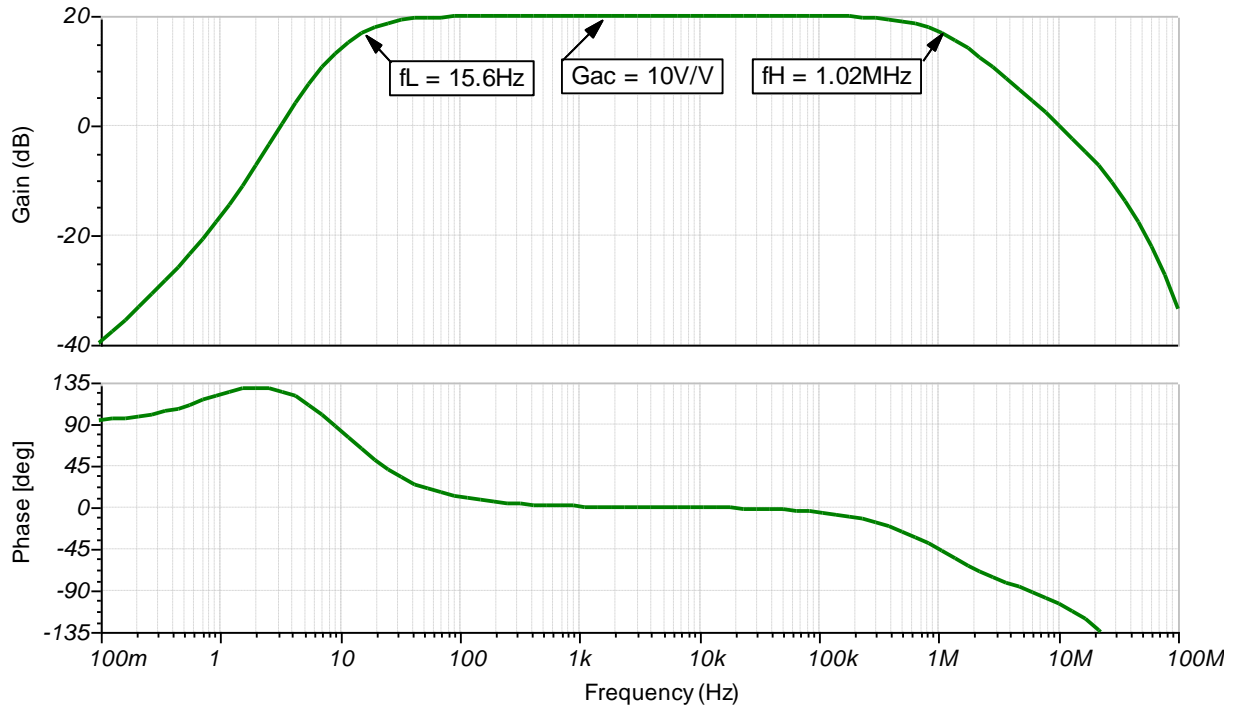

**Transient Simulation Results**

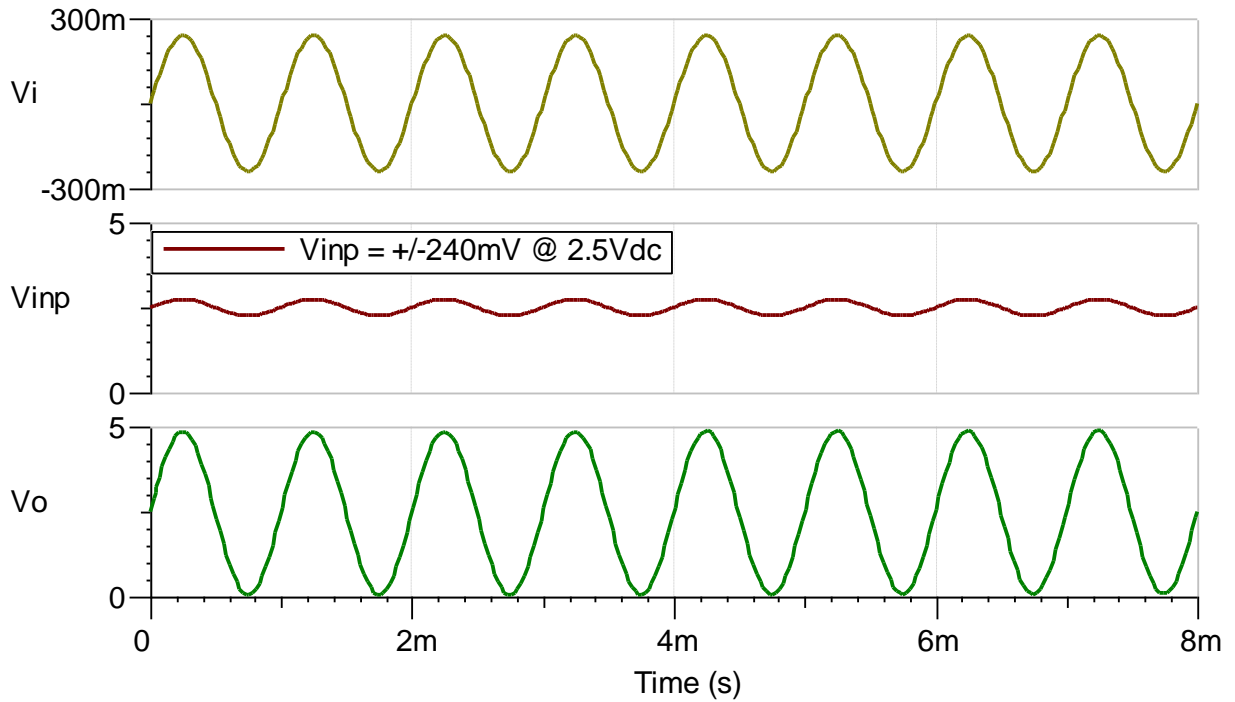

## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See circuit SPICE simulation file [SBOC505](#).

See TIPD185, [www.ti.com/tool/tipd185](http://www.ti.com/tool/tipd185).

## Design Featured Op Amp

TLV9062	
$V_{cc}$	1.8V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	300 $\mu$ V
$I_q$	538 $\mu$ A
$I_b$	0.5pA
UGBW	10MHz
SR	6.5V/ $\mu$ s
#Channels	1, 2, 4
<a href="http://www.ti.com/product/tlv9062">www.ti.com/product/tlv9062</a>	

## Design Alternate Op Amp

OPA192	
$V_{cc}$	4.5V to 36V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	5 $\mu$ V
$I_q$	1mA/Ch
$I_b$	5pA
UGBW	10MHz
SR	20V/ $\mu$ s
#Channels	1, 2, 4
<a href="http://www.ti.com/product/opa192">www.ti.com/product/opa192</a>	

## Revision History

Revision	Date	Change
A	January 2019	Downscale the title and changed title role to 'Amplifiers'. Added link to circuit cookbook landing page.