 


## D.C. level clamp


The need sometimes arises, e.g. after a stage of a.c. amplification, to clamp the minimum level of a signal voltage to a d.c. reference voltage. The circuit illustrated was developed to clamp, to the zero-volt level, signals having an amplitude of between 10mV and 10V. The familiar diode-and-capacitor clamp circuit is unsuitable here because of the diode's forward conduction characteristic.

In each cycle, the capacitor,  $C$ , charges to the peak negative value ( $V_b = -V_p$ ) of the input voltage,  $V_i$ . The voltage  $V_a$  then follows the input voltage ( $V_a = 2V_i + V_p$ ) while  $V_b$  remains at the level to which the capacitor was charged, decreasing only with a time constant

$$T \approx \frac{(R_4 + R_6) R_2 C}{R_4 + R_6 + 2R_2}$$



 Lower trace is the input signal; upper trace is the output from the restorer. Oscillogram was obtained with the circuit operating on a 150Hz signal with an amplitude of 40mV peak-to-peak.



The required voltage waveform, with its minimum d.c. level restored to zero, appears as  $V_a - V_b$ . A low-impedance single-ended output is provided by  $IC_2$  and, in this case, unity gain overall.

Using a 250- $\mu$ F electrolytic capacitor, the circuit clamps sinusoidal waveforms between 3Hz and 10kHz with little distortion. For use at higher frequencies,  $IC_1$  should have a faster slew rate. Lower distortion can be achieved if  $IC_2$  has a higher input impedance—allowing larger values of  $R_4$  and  $R_5$  to be used.

C. B. Mussell,  
United Liverpool Hospitals.