

Gain-programmable circuit offers performance and flexibility

Luo Bencheng, Key Laboratory of Mental Health, Institute of Psychology, Chinese Academy of Sciences

YOU CAN USE a standard precision instrumentation amplifier, such as the INA118 or AD623, as a gain-programmable amplifier with high accuracy and wide gain range. However, the gain range of such parts is fixed at certain values, limiting their flexibility. To solve the problem, a usual way is to use a gain-adjustable circuit controlled by a microcomputer (Figure 1).

IC₂ is a programmable 1-of-8 analog multiplexer that connects to eight weighting resistors, R₁ to R₈, to improve the gain range of the circuit based on IC₂, a general-purpose precision amplifier. The overall gain of the circuit depends on the value of the selected weighting resistor, as follows:

$$V_{OUT} = -V_{IN} \left(\frac{R_X + R_{ON}}{R_0} \right),$$

where R_{ON} is the on-resistance of IC₂, and R_X is one of the selected weighting resistors, R₁ to R₈. You control the port-select

pins Z₀ to Z₂ of IC₂ with a microcontroller to provide self-adjustable gain according to the selected weighting resistor. Unfortunately, the performance and quality of the circuit cannot provide good performance and high quality due to the on-resistance of IC₂, which you also cannot control, especially as the temperature changes.

The modified gain-adjustable amplifier circuit in Figure 2 uses the same IC₁ but changes IC₂ to a programmable 2-of-8 difference-input analog multiplexer, which connects to four balancing resistors, R₀₁ to R₀₄, and eight weighting resistors, R_{G1}

to R_{G8}, to improve the gain range of the circuit. By controlling the port-select pins Z₀ to Z₁ of IC₂ with a microcontroller, the

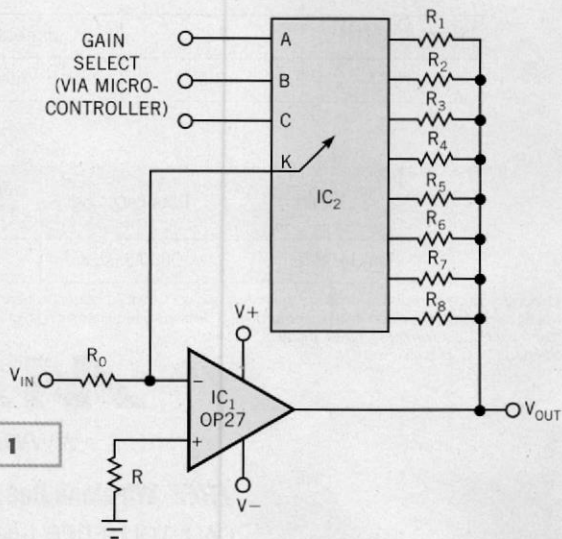


Figure 1

A basic gain-programmable amplifier circuit uses digital outputs from a microcontroller to set gain.

circuit provides self-adjustable gain with high quality. The overall gain of the circuit is:

$$V_{OUT} = V_{IN} \left(1 + \frac{R_{GB}}{R_{GA}} \right),$$

where R_{GA} is one of the selected weighting resistors, R_{G1} to R_{G4} , and R_{GB} is one of the selected weighting resistors, R_{G6} to R_{G8} .

Analog multiplexer IC₂ is on the input side of amplifier IC₁. Resistors R_{01} to R_{04} balance the signal-input channel to decrease the level-shifting because of the on-resistance of multiplexer IC₂ and minimize the effect of that resistance. Additionally, two operational amplifiers, IC₀₁ and IC₀₂, act as followers to improve the overall driver performance and common-mode-rejection capacity of the circuit. □

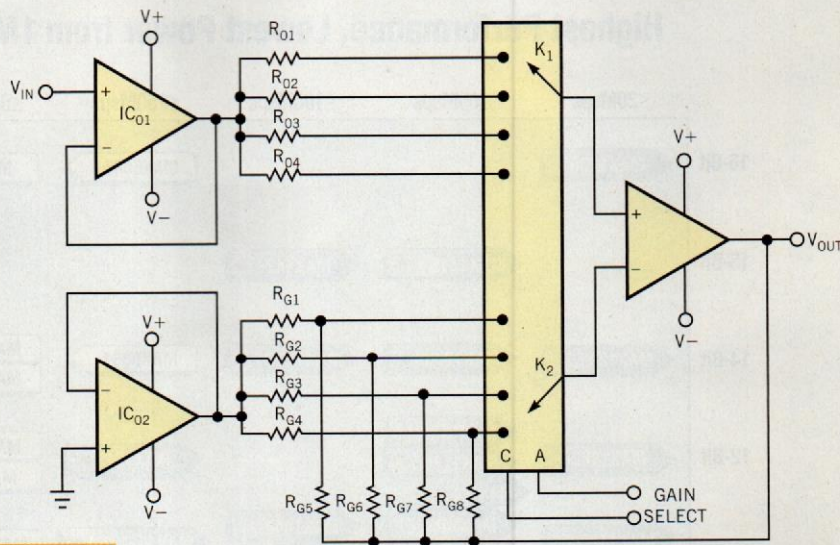


Figure 2

The modified circuit provides more flexibility, along with high performance.