

Controlled power supply increases op amps' output-voltage range

Yakov Velikson, Lexington, MA

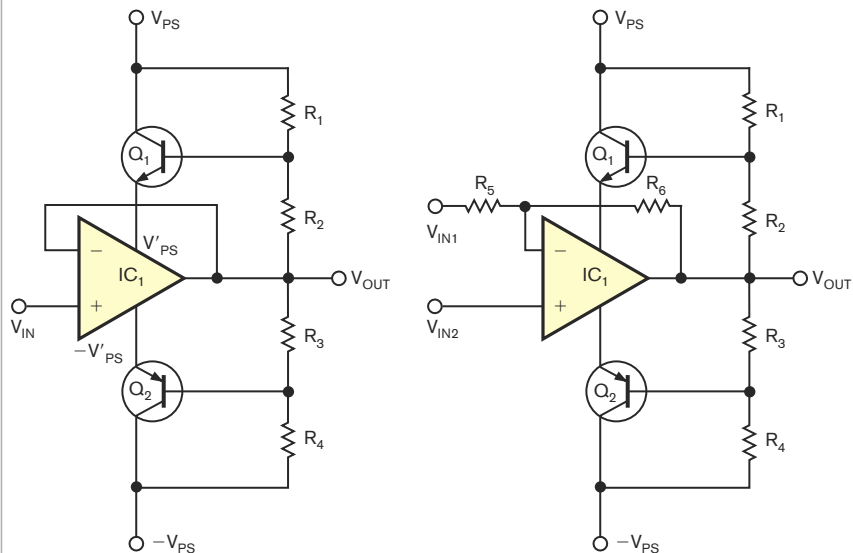


Figure 1 These simple circuits present the general methods of connecting the amplifier as an inverter or a follower to effect increased output voltage.

Increasing the output voltage of IC operational amplifiers usually involves adding high-voltage external transistors. The resulting circuit then requires correction to retain its operating characteristics. This correction is difficult, especially for precise amplifiers. This Design Idea presents an alternative: the use of a controlled power supply for the operational amplifier itself, which can increase the output voltage for many precise operational amplifiers without altering their operational characteristics. You can accomplish this task by connecting controlled transistors to the power supply of the amplifier. Resistor dividers that connect to the amplifier's output and bipolar high voltages control these transistors (Reference 1). The simple circuits in **Figure 1** present general methods of connecting the amplifier as an inverter or a follower to effect increased output voltage.

Dividers with resistors R_1 , R_2 , R_3 , and R_4 determine the scale of power supply V'_{PS} and $-V'_{PS}$ for the amplifiers. If the output voltage ranges from $\pm 22V$,

resistor $R_1=R_2=R_3=R_4=R$, and V_{PS} and $-V_{PS}$ are 28V, then voltages V'_{PS} and $-V'_{PS}$ fall in the following range, allowing for any additional loss: $V'_{PS} = V_{PS}R_7/(R_1+R_2) + V_{OUT}(-V_{OUT})R_1/(R_1+R_2)$, and $-V'_{PS} = -V_{PS}R_3/(R_3+R_4) + V_{OUT}(-V_{OUT})R_4/(R_3+R_4)$ or $3V < V'_{PS} < 25V$ and $-3V > -V'_{PS} > -25V$. However, power-supply circuits include transistors, which create junction resistance, affecting the amplifier's operation.

You can use supporting amplifiers to reduce losses and increase the quality of the output voltage of the primary amplifier. The requirements for supporting amplifiers are simple. They should have power supplies with opposite polarity from and lower applied voltage than that of the main power supply. They should provide the necessary power to the primary amplifier, and their frequency range should be slightly higher than that of the primary amplifier. You can use supporting amplifiers to eliminate the transitional resistances of transistors in power-supply connections. Thus, these circuits offer flexibility across a range of amplifier configurations (references 2 and 3).

Figure 2 shows an example of how to connect supporting amplifiers as follows. You derive output voltages V'_{PS} and $-V'_{PS}$ from resistor connections with the following equations: $V' = V_{PS1}R_7/(R_6+R_7) + V_{OUT}(-V_{OUT})R_6/(R_6+R_7)$, and $-V' = -V_{PS1}R_8/(R_8+R_9) + V_{OUT}(-V_{OUT})R_9/(R_8+R_9)$. If the supporting amplifiers have a power supply of 28V for V_{PS1} and $-2V$ for $-V_{PS2}$ for amplifier IC_2 , then $-V_{PS1} = -28V$, $V_{PS2} = 2V$ for amplifier IC_3 , and the output voltage of amplifier IC_1 , V_{OUT} is 24V or $-24V$. Also, $R_6=R_7=R_8=R_9=R$, such that $V' = 28V \times 0.5 + 24V \times 0.5 = 26V$. Further, $-V' = -28V \times 0.5 + 24V \times 0.5 = -2V$ for $V_{OUTMAX} = 24V$. $V = 28V \times 0.5 - 24V \times 0.5 = 2V$, and $-V' = -28V \times 0.5 - 24V \times 0.5 = -26V$ for $V_{OUTMIN} = -24V$. You can achieve the greatest voltage range by using separate power supplies—one for the normal voltages of the amplifier and one for the regulated part of the output voltage (Figure 3).

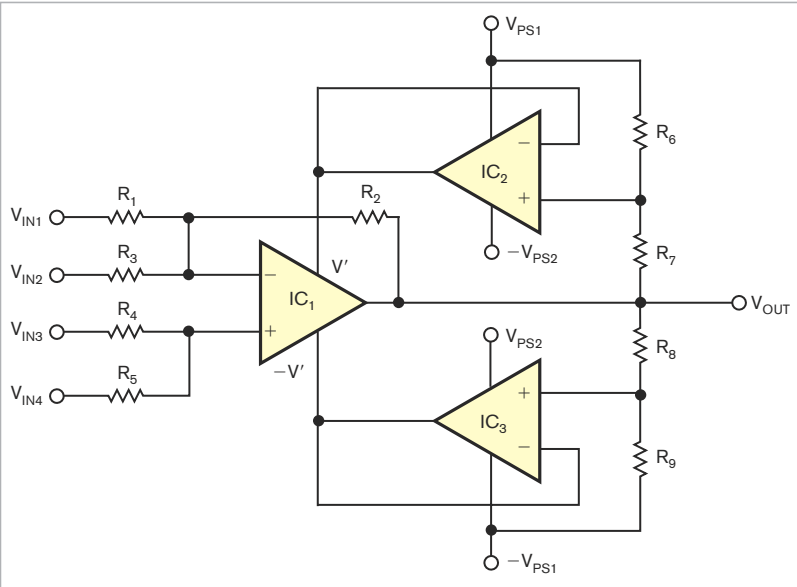


Figure 2 Replacing the transistors with op amps reduces losses and increases the quality of the output voltage of the primary amplifier.

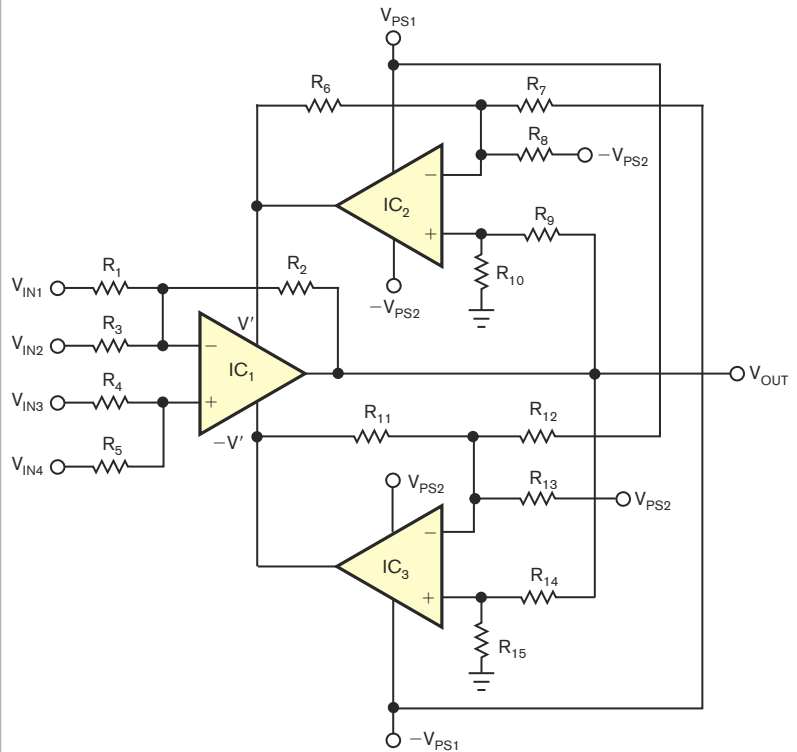


Figure 3 You can achieve the greatest voltage range by using separate power supplies—one for the normal voltages of the amplifier and one for the regulated part of the output voltage.

IC₁ is the primary amplifier. Supporting amplifiers IC₂ and IC₃ have asymmetrical power supplies. You could use many types of amplifiers in this circuit, but modern operational amplifiers may be preferable because they allow the use of the complete range of the power supply and because they handle rail-to-rail input and output. In this circuit, $V_{PS1} = 28V$, $-V_{PS1} = -28V$, $V_{PS2} = 2V$, and $-V_{PS2} = -2V$. The voltages of the primary amplifier are $V' = -(-V_{PS1})R_6/R_7 - (-V_{PS2})R_6/R_8 + (-V_{OUT})R_{10}/(R_9 + R_{10}) [R_7R_8 + R_6(R_7 + R_8)]/R_7R_8$. Further, $-V' = -(V_{PS1})R_{11}/R_{12} - (V_{PS2})R_{11}/R_{13} + (-V_{OUT})R_{15}/$

$(R_{14} + R_{15})[R_{12}R_{13} + R_{11}(R_{12} + R_{13})]/R_{12}R_{13}$. Set $R_6 = R_{10} = R_{11} = R_{15} = R$, $R_7 = R_8 = R_{12} = R_{13} = 2R$, and $R_9 = R_{14} = 3R$, such that $R_6/R_7 = R_6/R_8 = R_{11}/R_{12} = R_{11}/R_{13} = 0.5$, $R_{10}/(R_9 + R_{10}) = R_{15}/(R_{14} + R_{15}) = 0.25$, and $[R_7R_8 + R_6(R_7 + R_8)]/R_7R_8 = [R_{12}R_{13} + R_{11}(R_{12} + R_{13})]/R_{12}R_{13} = 2$. Then, substitute these values into the amplifier voltages yields $V' = 14V + 1V + (-V_{OUT})0.5$, and $-V' = -14V - 1V + (-V_{OUT})0.5$. Minimum and maximum values for each power supply are $1.5V \leq V \leq 28.5V$, and $-1.5V \geq -V \geq -28.5V$. The total voltage of the power supply has a limit of 30V, ranging from 1.5 to 28.5V and from -1.5 to -28.5V. This range

permits an increase of the output voltage of the primary amplifier by $\pm 27V$. **EDN**

REFERENCES

- 1 Velikson, Yakov, *Electronics, Information Book*, pg 138, Energoatomiztum, St Petersburg, Russia, 1996.
- 2 Velikson, Yakov, "Device for recurrence of voltage," *Bulletin of Izobreteny* (copyrights and patents), No. 3, 1991.
- 3 Velikson, Yakov, A Murigin, and V Uchno, "The multichannel conversion of a revolving sine-cosine resolver to code," *Bulletin of Izobreteny* (copyrights and patents), No. 44, 1988.