



## LOGARITHMIC VOLTAGE TO VOLTAGE CONVERTER

The output voltage is logarithmically proportional to the input voltage. The difference between this circuit and the previous is that the exponentiator is in the feedback loop of the op-amp and hence the mathematical function has been inverted. The circuit is useful for performing true logarithmic compression or for converting linear inputs into dBs.