

# Low-cost logarithmic amp works over one decade

by Christopher S. Tocci

Becton-Dickinson Medical Systems, Westwood, Mass.

If extremely high precision is unnecessary and if the required dynamic range spans no more than one decade of input voltage, then this logarithmic amplifier will serve the application well. Use of a simple exponential generator, which is ultimately required to convert a voltage into its base-10 logarithmic equivalent, makes it possible to build the amp for a mere \$3 to \$4.

The overall system is shown in (a), with the schematic of the exponential generator shown in (b). Voltage divider  $R_1$ - $R_2$  applies 0.5 volt to RC combination  $R_3$  $C_1$  through op amp  $A_2$  on power-up in order to initialize the exponential growth process. As  $C_1$  charges, the output of  $A_2$  increases as shown in the curve until the Schmitt trigger,  $A_3$ , which has a switching threshold of 10 v, fires, turning on field-effect transistor  $Q_1$  and discharg-

ing  $C_1$  to about 1.0 v. The process then repeats, with switching occurring at a rate,  $\tau$ , determined by  $C_1$  and  $R_2$ . The op amp must have a minimum slew rate of:

$$\begin{aligned} dV_o(t)_{\max}/dt &= (1/\tau) e^{V_i/\tau} \\ &= (10 \log_e 10)/\tau = 23.03 f_s \end{aligned}$$

where  $f_s$  is the switching frequency. Thus at a switching frequency of 10 kilohertz ( $C_1 = 0.01 \mu\text{F}$ ,  $R_1 = 4.32 \text{ k}\Omega$ ) the slew rate must be at least 0.23 v/microsecond.

During each switching cycle, the exponential output is compared at  $A_1$  to the instantaneous input voltage,  $V_c$ , that is to be converted into its corresponding logarithm.  $A_1$ 's on time,  $D_{V_c}$ , is thus related to input voltage  $V_c$  by:


$$D_{V_c} = (t_{\text{on}}/\tau) 100 = \tau \log_e |V_c|/\tau = 0.434 \log_e |V_c|$$

where output voltage  $V_p$  corresponds directly to  $D_{V_p}$ , ignoring a scale factor.

The active low-pass filter of gain  $k$  that follows, which should be at least a third-order type for the best results, then finds the average value of  $V_p$  from:

$$V_L = \bar{V}_p = k(0.434) \log_e |V_c|$$

Choosing  $k$  such that  $k(0.434) = k(V_{p,\text{max}}/\log_e 10) = 4.34$ , it is seen that  $V_L = 10 \log_{10} |V_c|$  for  $1 \leq V_c \leq 10$ .  $\square$

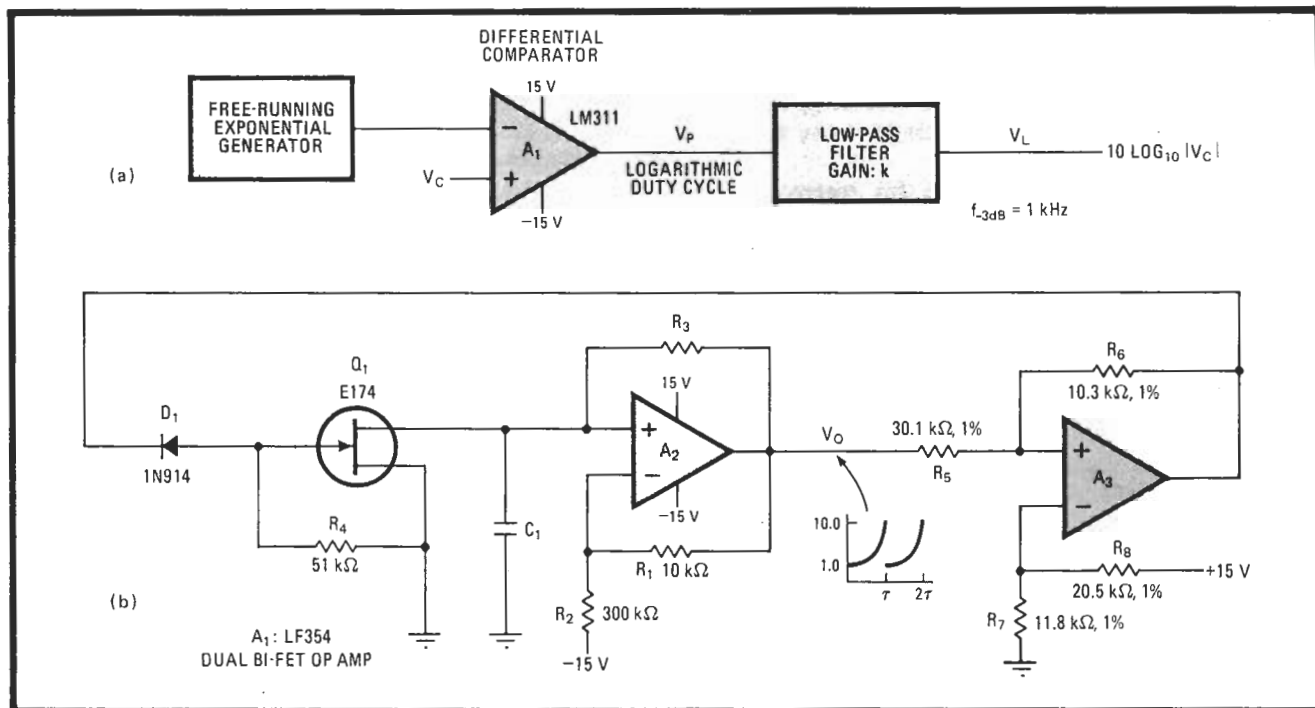

**Naturally.** Low-cost generator provides exponential waveform of sufficient accuracy in amplifier that takes logarithms over one decade of input voltage. Filter averages pulse-width-modulated equivalent of  $V_c$  produced by differential comparator,  $A_1$ , for  $V_L = 10 \log_{10} V_c$ .