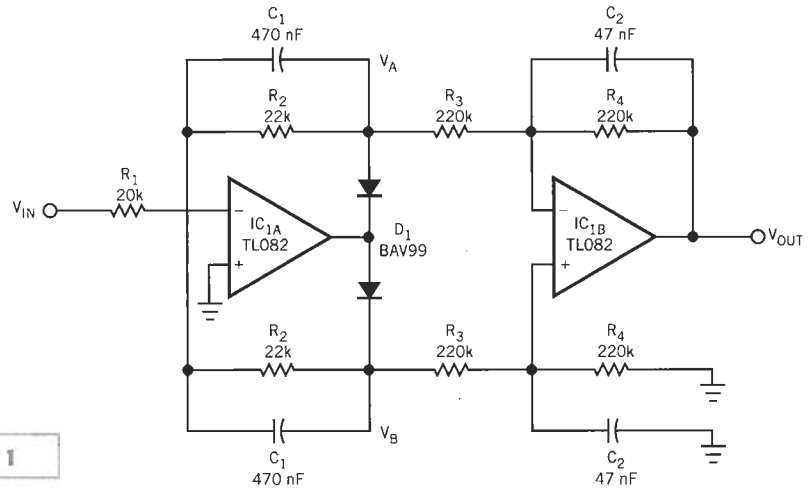


# Two op amps provide averaged absolute value

Dobromir Dobrev, Jet Electronics, Sofia, Bulgaria

**T**HE CIRCUIT in **Figure 1** is useful when you need amplitude demodulation or an averaged absolute-value conversion. The circuit comprises two stages, the first of which, IC<sub>1A</sub>, is a differential-output absolute-value converter. The second stage, IC<sub>1B</sub>, is a traditional differential amplifier. The combination of the two stages performs single-ended absolute-value conversion but only if  $R_3 \gg R_2$ . The  $C_1$  capacitors integrate the current flow and yield averaged voltages  $V_A$  and  $V_B$ . In addition, the capacitors ensure low ac-impedance points at nodes  $V_A$  and  $V_B$  when the output diodes are reverse-biased.

The additional  $C_2$  capacitors in parallel with  $R_4$  resistors impart a second-order-lowpass-filter characteristic to the circuit and remove the remaining ac signal. From a practical point of view, you can choose  $R_3$  to be five to 10 times higher than  $R_2$ . The gain of the circuit is  $(R_2 \parallel R_3 / R_1) (R_4 / R_2)$ . In most applications, you would choose the filter time con-



**Figure 1**

**This single-ended, averaged absolute-value converter is useful for amplitude demodulation.**

stants  $\tau_1 = R_2 \parallel R_3 C_1$  and  $\tau_2 = R_4 C_2$  to be equal. The circuit in **Figure 1** is simple, symmetrical, and cost-effective. It also makes it easy to calculate and adjust the gain using one resistor,  $R_1$ . Other advan-

tages are that the circuit has equal delay for positive- and negative-going signals and that it doesn't need matched diodes. □