

Use op-amp injection for Bode analysis

Martin Galinski, Micrel Semiconductor, San Jose, CA

BODE ANALYSIS is an excellent way to measure small-signal stability and loop response in power-supply designs. Bode analysis monitors gain and phase of a control loop. It performs this monitoring by breaking the feedback loop and injecting a signal into the feedback node and then comparing the injected signal with the output signal of the control loop. The method requires a network analyzer to sweep the frequency and compare the injected signal with the output signal. The most com-

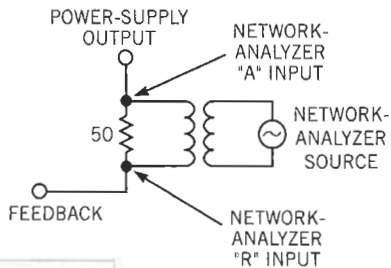


Figure 1

Bode analysis using transformer injection yields gain and phase information in a control loop.

mon method of injection is the use of transformer. **Figure 1** demonstrates how a transformer injects a signal into the feedback network. A 50Ω resistor affords impedance matching to the network-analyzer source. This method allows the dc loop to maintain regulation and allows the network analyzer to insert an ac signal on the dc voltage. The network analyzer then sweeps the source while monitoring A (voltage channel) and R (reference channel) for an A/R-ratio measurement. Although this method is

the most common for measuring the gain and phase of a power supply, it has significant limitations. First, to measure low-frequency gain and phase, the transformer needs high inductance. Frequencies lower than 100 Hz, therefore, require a large and expensive transformer.

Also, the transformer must be able to inject high frequencies. Transformers with these wide frequency ranges generally are custom-made and usually cost several hundred dollars. By using an op amp, you can avoid the cost and frequency limitations of an injection transformer. **Figure 2** demonstrates the use of an op amp in a summing-amplifier configuration for signal injection. R_1 and R_2 reduce the dc voltage from the

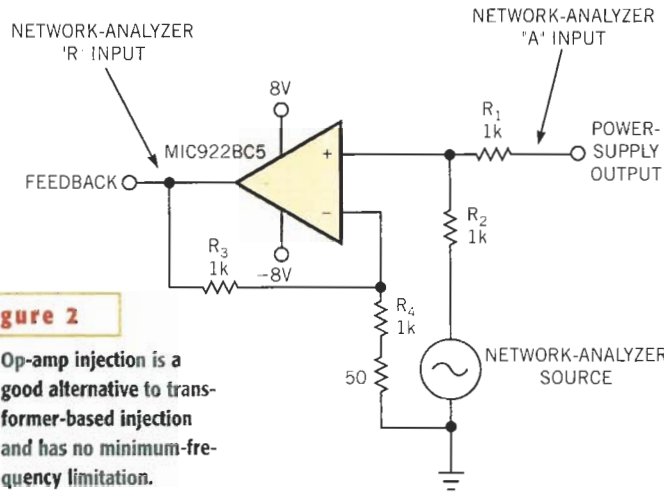



Figure 2

Op-amp injection is a good alternative to transformer-based injection and has no minimum-frequency limitation.

output to the noninverting input by half. The network analyzer is generally a 50Ω source. R_1 and R_2 also divide the ac signal from the network analyzer by half. These two signals "sum" together at half their original input. The output then gains up

by a factor of two by R_3 and R_4 and goes to the feedback output. (The 50Ω resistor balances the network analyzer's source impedance.) This action essentially breaks the loop and injects the ac signal on top of the dc output voltage and sends it to the feedback terminal. By monitoring the feedback terminal (R) and output terminal (A), the analyzer measures gain and phase. This method has no minimum frequency. Make sure that the bandwidth of the op amp is much greater than the expected bandwidth of the power supply's control loop. An op amp with at least 100-MHz bandwidth is more than adequate for most linear and switching power supplies. □

This is Not Your Father's Voltage Reference



Intersil's 1.25V and 2.50V /sub 1.5μ-watt Voltage Reference is ideal for High Accuracy Data Acquisition Systems


Intersil's new ISL60002 voltage reference brings precision performance standards to portable and battery-operated systems by offering an accurate, stable reference that essentially presents no load to the battery.

Intersil's ISL60002 with ultra-low, sub 1.5μ-watt power consumption are the first precision references that make it practical to leave the reference powered-on continuously in a battery powered system thus eliminating the time delay required for the reference to settle to its final value.

Features:

- Reference Voltage: 1.25V & 2.50V
- Absolute Initial Accuracy Options: ±2.5mV & ±5.0mV
- Supply Voltage range: 2.7V to 5.5V
- Ultra-Low Supply Current: 500nA

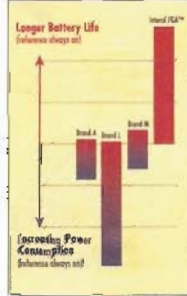Production Availability: The ISL60002C-12 & -25 and ISL60002D-12 & -25 in 8-lead SOT23 are available off the shelf with 1k unit prices starting at \$1.45 and \$0.95 respectively. The ISL60002C-12 & -25 and ISL60002D-12 & -25 in 8-lead SOIC are available off the shelf with 1k unit prices starting at \$1.50 and \$0.99 respectively.




Longer Battery Life
(reference always on)

Increasing Power Consumption
(reference always off)


Get more technical info on Intersil's complete portfolio of High Performance Analog Solutions at www.intersil.com/info

Samples at www.intersil.com/xicorsamples More info at www.intersil.com/ISL60002

©2004 Intersil Americas Inc. All rights reserved. The following are trademarks of Intersil Americas Inc.: Intersil, Intersil logo, "I" and Design. Xicor is a trademark of Intersil Corporation or one of its subsidiaries.



Amplifiers | Converters | Data Converters | DSPs/ADCs | Display Interfaces | Power Management | Switch/MUX | Timers | Voltage



HIGH PERFORMANCE ANALOG

Enter 46 at www.edn.com/info