

Precision full-wave signal rectifier needs no diodes

José M Blanes and José A Carrasco, University Miguel Hernández, Elche, Spain

Rectifier circuits based on semiconductor diodes typically handle voltage levels that greatly exceed the diodes' forward-voltage drops,

which generally don't affect the accuracy of the rectification process. However, the rectified signal's accuracy suffers when the diode's voltage drop ex-

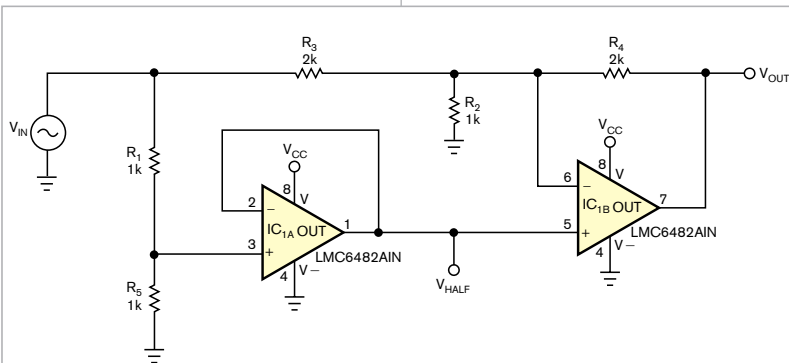


Figure 1 This precision full-wave-rectifier circuit uses two op amps and no diodes. When altering the basic design, note that resistors R_3 and R_4 are both twice the value of R_2 and that R_1 and R_5 are equal.

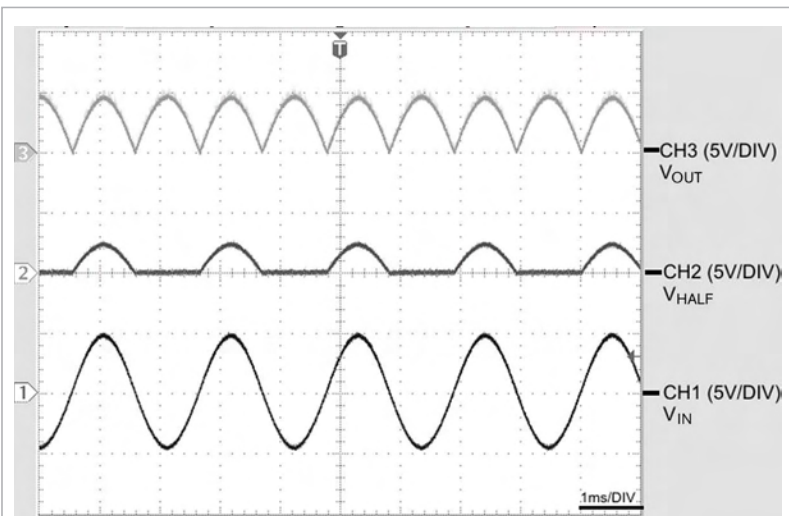


Figure 2 From bottom to top, the waveforms show V_{IN} (CH1), V_{HALF} (CH2), and V_{OUT} (CH3).

DIs Inside

82 1-Hz to 100-MHz VFC features 160-dB dynamic range

86 Cascode MOSFET increases boost regulator's input- and output-voltage ranges

ceeds the applied voltage. Precision rectifier circuits combine diodes and operational amplifiers to eliminate the effects of diode voltage drops and enable high-accuracy, small-signal rectification. By taking advantage of modern operational amplifiers that can handle rail-to-rail inputs and outputs, the circuit in **Figure 1** dispenses with diodes altogether, provides full-wave rectification, and operates from a single power supply.

The circuit operates as follows: If $V_{IN} > 0V$, then IC_{1A} 's output, V_{HALF} , equals $V_{IN}/2$, and IC_{1B} operates as a subtractor, delivering an output voltage, V_{OUT} , equals V_{IN} . In effect, the circuit operates as a unity-gain follower. If $V_{IN} < 0V$, then $V_{HALF} = 0V$, and the circuit behaves as a unity-gain inverter and delivers an output of $V_{OUT} = -V_{IN}$. **Figure 2** shows the circuit's input signal at V_{IN} ; its intermediate voltage, V_{HALF} ; and its output voltage, V_{OUT} .

The circuit uses a single National Semiconductor LMC6482 chip and operates in the linear regions of both operational amplifiers. Suggested applications include low-cost rectification for automatic gain control, signal demodulation, and process instrumentation. The circuit relies on only one device-dependent property: The amplifiers must not introduce phase inversion when the input voltage exceeds the negative power supply; the LMC6482 meets this requirement. **EDN**