

Rectifier tracks positive and negative peaks

Harry Bissell Jr, Welding Technology Corp, Farmington Hills, MI



Signals ranging from music to complex control-system waveforms may contain unequal positive and negative peak amplitudes. An “envelope-follower” circuit can track unequal peaks, but the ability to select a desired peak can enhance the circuit’s performance (**Reference 1**). The circuit in **Figure 1** applies a new twist to a classic absolute-value circuit. Applying an input signal to R_1 (full) produces an output equal to the input’s absolute value. Applying an input signal to R_6 (positive) or R_7 (negative) produces outputs of positive or negative half-cycles, respectively. **Figure 2** illustrates all three modes of operation.


Understanding the circuit is simple if you consider that op amp IC_{1A} strives

to maintain its inverting input at virtual ground. For example, applying $-1V$ to the negative input, R_7 , drives the anode of D_1 to -333 mV. IC_{1A} ’s output, Pin 1, drives D_2 ’s cathode positive enough to force D_2 ’s anode voltage to 333 mV. Because IC_{1A} ’s inputs now rest at 0V, D_1 is effectively reverse-biased and out of the circuit. The 333 mV available at D_2 ’s cathode also applies to IC_{1B} ’s noninverting input, Pin 5, and IC_{1B} must balance its input voltages by driving its output, Pin 7, to 1V. IC_{1B} ’s inverting input, Pin 6, goes to 333 mV. The voltage drop across R_4 thus equals 666 mV. One-third of the input current flows through the series connection of R_2 and R_3 , and two-thirds flows in R_4 . To achieve unity

gain, R_7 ’s value equals that of $R_2 + R_3$ in parallel with R_4 .

Applying a positive input to R_7 causes IC_{1A} ’s output to go negative by a voltage equal to one forward-diode drop and thus holds D_1 ’s anode at ground. D_2 is reverse-biased, and both of IC_{1B} ’s inputs rest at 0V. The circuit’s output is thus 0V. Applying an input voltage at R_6 yields similar operation. A positive input causes an equal-value positive output, and a negative input produces a 0V output. You can ignore the effects of IC_{1B} ’s high input impedance, which are negligible. To maintain unity gain, the value of R_6 is twice that of R_3 .

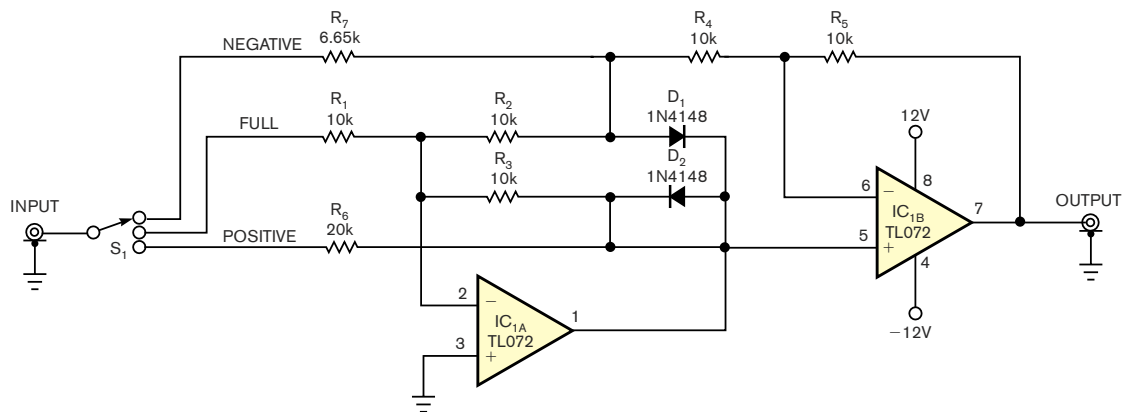Resistors $R_1, R_2, R_3, R_4,$ and R_5 are of equal value and close tolerance. Note that IC_1 ’s power-supply connections require bypass capacitors (not shown). To minimize errors, use a low-impedance source or buffer amplifier to drive the circuit. You can use a three-posi-



NOTE: SCHEMATIC DOES NOT SHOW POWER-SUPPLY DECOUPLING CAPACITORS.

Figure 1 Use this versatile precision rectifier circuit to recover a signal's positive peaks, negative peaks, or both in full-wave mode.

tion rotary switch for input-mode selection, or an on/on/on toggle switch, such as C&K Components' 7211, available from Digi-Key Corp (www.digikey.com) and other sources, or a similar switch, wired as a three-way selector. (See the manufacturer's data sheet for a connection diagram.) You can also use separate connectors for the inputs, but connect no more than one input at a time. **EDN**

REFERENCE

■ Bissell, Harry, "Envelope follower combines fast response, low ripple," *EDN*, Dec 26, 2002, pg 59, www.edn.com/article/CA265499.

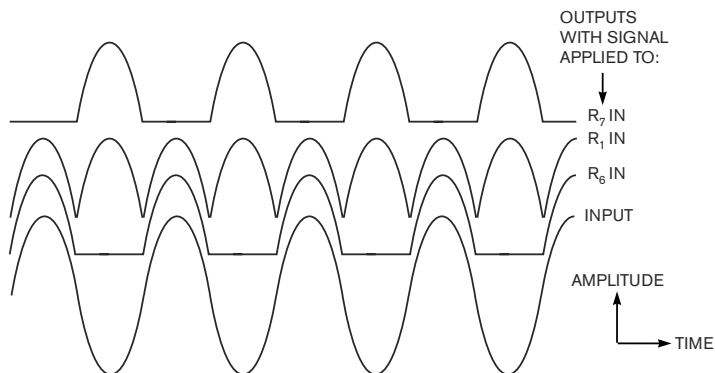


Figure 2 This waveform plot shows the circuit's outputs for a sine-wave input connected to the negative, full, and positive inputs, respectively. Traces are vertically offset for clarity.