


Paralleling decreases autozero-amplifier noise by a factor of two

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

 Autozero amplifiers have almost zero drift and input-offset values of 1 to 20 μV . You can compensate for the initial voltage offset of an autozero amp in sensitive circuits, such as dc amplifiers and integrators, requiring the

processing of voltages of 10 μV to 1 mV. Total compensation down to an offset of 0V, however, is an illusion because residual low-frequency output noise is still present in any autozero amp.

The Analog Devices (www.analog.com)

AD8628 autozero amp has a low-frequency-noise value of 0.5 μV p-p at 0.1 to 10 Hz. If your application requires zero drift and low output noise, you can use the circuit in **Figure 1**. A quad autozero amp develops a gain of almost 1000. The resistor network comprising the R_3 resistors averages the output signals of these amplifiers to create the final output voltage.

The quad autozero amps are the four sections of IC₁, an Analog Devices AD8630 (Reference 1). Quad integrated resistors having one common lead can substitute for the four R_3 resistors. The R_1 and R_2 resistors should be high-

quality, precision, film devices with 0.5% or less tolerance. The tolerance of the R_3 resistors should not exceed 1%. The basis for decreasing the circuit's noise at the output in comparison with a single amplifier of IC₁ is the principle of averaging the signals containing the same deterministic component of random noise. If you assume that the amplifiers of IC₁ represent independent or uncorrelated noise sources that obey the gaussian distribution, then the standard deviation of the average of noise outputs of these sections is:

$$\sigma_{\text{AVE2}} = \frac{\sqrt{2\sigma_X^2 + 2\sigma_Y^2}}{2},$$

where σ_X and σ_Y are the standard deviations of noise signals at outputs of the single respective amplifiers. If $\sigma_X = \sigma_Y$ —an assumption that you can make without hesitation because the op amps reside in one chip—then:

$$\sigma_{\text{AVE2}} = \frac{\sigma_X}{\sqrt{2}}.$$

If you average four amplifiers, you obtain:

$$\sigma_{\text{AVE4}} = \frac{\sigma_X}{2}.$$

If the value of output resistance of the circuit, which is about $R_3/4 \approx 38\Omega$, is too high for your application, place a voltage follower between the output terminal and the next stage. \square

REFERENCE

1 "AD8630 Quad, Zero Drift, Single-Supply, Rail-to-Rail Operational Amplifier," Analog Devices Inc, www.analog.com/en/prod/0,2877,AD8630,00.html.

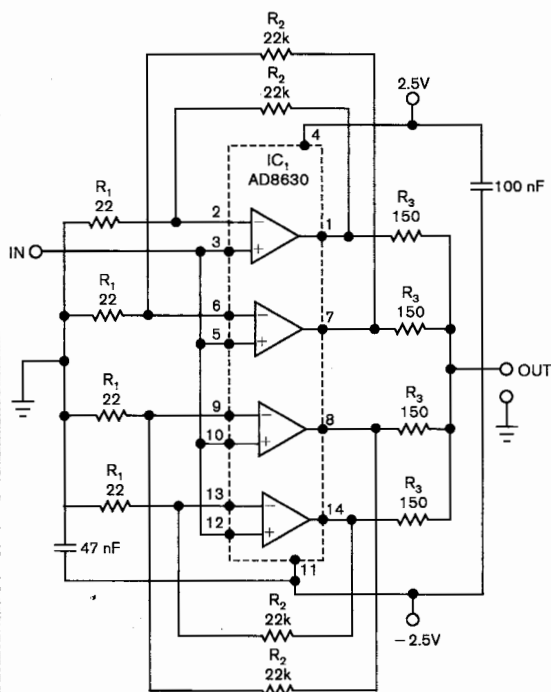


Figure 1 Use this circuit when your application requires zero drift and low output noise.