



Settling Time of Operational Amplifiers

ROBERT I. DEMROW, Applications Engineering Manager, Analog Devices, Inc.

FOREWORD

It is possible to measure voltages and currents to within small (even fractional) parts per million, traceable all the way to the Bureau of Standards. Typically, at the limits of precision, repeated measurements must be made over a period of time, after which an experienced practitioner can state with a great deal of certainty that a voltage or a current had, during that interval, an average value expressible to six or more significant figures.

That this can be accomplished is interesting, impressive, and of basic importance to all engineers, but it is of little direct relevance to a far more pervasive type of measurement. This is the measurement that calls for a more modest degree of accuracy – four significant figures at best (today), but the measurement must be completed, often within a microsecond or so, then converted, stored, and utilized by a computer. The time taken to complete the measurement to the desired degree of accuracy, be it $\pm 1\%$, $\pm 0.1\%$, $\pm 0.01\%$, or $\pm \frac{1}{2}\text{LSB}$, in terms of its final value (with the often-added provision that said final value is within a similarly small fraction of full scale of its nominal expected value) is usually called Settling Time. This interval may be quite short: at present $\pm 0.01\%$ within 0.5 to 1.0 microseconds is fashionable; next year engineers will consider an order of magnitude improvement in performance feasible (and many will attain it). Significant improvements will be reported in these pages.

The purpose of the present discussion is to provide an interpretation of Settling Time, and to set before the engineer the issues involved in terms of circuit design, hardware, specifications, applications, and measurements. We shall try, to the degree possible, to avoid the use of intimidating mathematical formulae, and to reveal practical circuits and mathematical shortcuts.

The important difference of Settling Time investigations is that, although frequency response may be a tool, the results must be either implicitly or (preferably) explicitly measurable in the Time Domain. They are in general terribly nonlinear and subject to (so it would seem) every stray nastiness that Nature has evolved, because of the combined stress on both speed and accuracy.

Thus the recently-increased use of operational amplifiers in handling data in systems calling for high-speed switching rates, especially in connection with digital computers, has led to a requirement for *time-response* characterization of general- and special-purpose operational amplifiers. A typical problem is the application of rapidly-changing signals (e.g., step functions) to a buffer amplifier, which must faithfully reproduce the input to a high degree of accuracy within a period of the order of a microsecond. This requires that the amplifier be designed and optimized for *Settling Time*. Applications requiring fast settling time to high accuracies are typified by Sample-Hold circuits, Multiplexers, and amplifiers used with A/D and D/A converters. Settling time is important in these applications because it is the principal factor which determines the maximum data or information transfer rate for a given accuracy. A tradeoff is generally possible between data rate and accuracy: viz., higher data rates are possible at the sacrifice of accuracy. It should also be noted that the buffer amplifier, as but one step in a process, is now one of the major limitations on system speed.

DEFINITION

SETTLING TIME is the time elapsed from the application of an ideal instantaneous step input to the time at which the closed-loop amplifier output has entered and remained within a specified error band, usually symmetrical about the final value. Settling time includes a very brief propagation delay, plus the time required for the output to slew to the vicinity of

(Continued on p. 2)

INTRODUCTION

Much has been written on the subject of small-signal frequency response characteristics of amplifiers; and most users of operational amplifiers are able to make use of the manufacturers' specifications to calculate closed-loop bandwidth, analyze stability, determine phase errors, etc.¹ Most manufacturers also provide data sufficient to characterize the full power response and slew rate of the amplifier.


¹Footnote references are to numbered items in the bibliography, page 11.

IN THIS ISSUE


	PAGE
<i>Settling Time of Operational Amplifiers</i>	1
<i>Applying the Analog Differentiator</i>	12
<i>Editor's Notes</i>	14
<i>Readers' Notes</i>	15
<i>Recent Publications</i>	16

DEFINITION (Continued from p. 1)

 the final value, recover from the overload condition associated with slewing, and finally settle to within the specified error. Figure 1 illustrates this definition of Settling Time.



 (a) Components of settling time (nonlinear scale)



(b) Annotated wave forms illustrating comparative settling time of two typical op amps.

Figure 1. Pictorial Definition of Settling Time

CAUTION: The above definition has been used widely in the data acquisition field for at least the past 10 years. Nevertheless, some manufacturers new to this field (but not to the tricks of "specmanship") define "settling time" as the time required to settle within the linear small-signal region only. When considering the products and applications literature of these manufacturers, it is important to realize that their term usually corresponding to Settling Time is "Acquisition Time." (Until adopted for this usage, Acquisition Time had a specialized meaning of its own: minimum time required for a Sample-Hold switch to be closed to allow re-opening without loss of information, usually without the necessity that the amplifier finish settling.) We do not know at present what standards will eventually emerge, but we shall always identify small-signal settling time by attaching the "small signal" label wherever it would be misleading to do otherwise.

Settling time may also be defined in terms of the recovery time of the amplifier from an instantaneous error caused by a step or an impulse change in load. Because Settling Time is determined by a combination of amplifier characteristics, nonlinear as well as linear, and because it is a closed-loop parameter, it cannot readily be predicted from such open-loop specifications as slew rate, small-signal bandwidth, etc.

Two frequently-occurring applications requiring fast settling time for maximum transfer rate are indicated in Figures 2 and 3. Figure 2 depicts the typical Multiplexer problem (only two channels shown, for simplicity). One line is at 0V, the other is at -10V. When switching from one channel to the other, the amplifier's input may be subjected to a 10-volt step and must recover to the millivolt level in high-accuracy systems. Figure 3 indicates a typical waveform from a high-speed D/A Converter (DAC) showing large transient spikes ("glitches") caused by time skew between turn-on and turn-off of the DAC's switches. The settling time of the amplifier used (if the DAC uses an amplifier) limits the maximum bit rate for an A/D Converter (ADC) using the DAC.

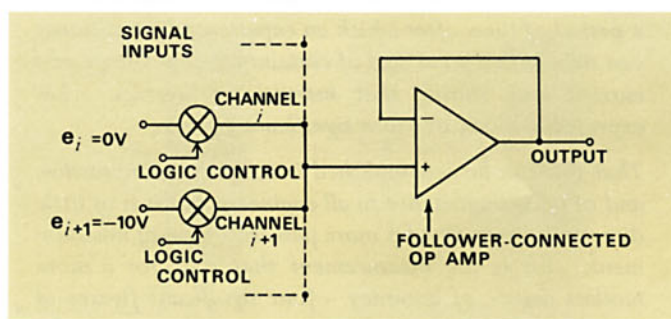


Figure 2. Simplified diagram of multiplexer circuit

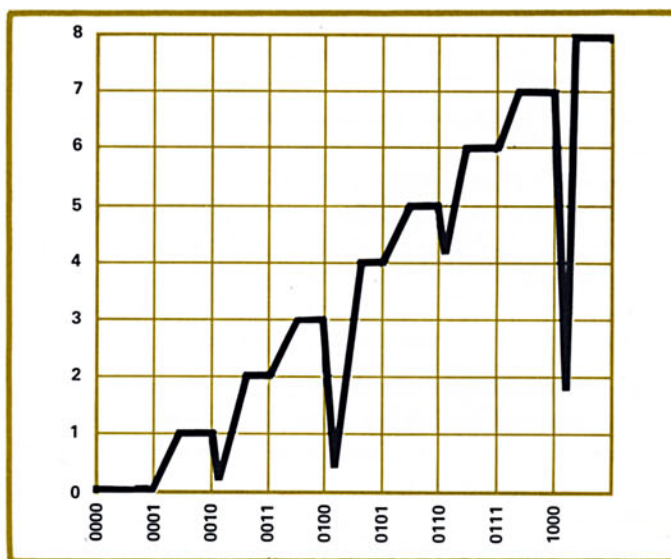


Figure 3. Output of counter-driven Fast D/A Converter showing "glitches"

AMPLIFIER DESIGN FACTORS AFFECTING SETTLING TIME

The design factors to be discussed here are those that the amplifier designer and the engineer who specifies the amplifier must consider. Other design factors concerning the circuit the amplifier is tested or used in will be discussed in a later section.

LINEAR OPERATING RANGE. Although the essence of the problem of settling time is nonlinear, the factors to be discussed in this section pertain to the all-important linear-settling "tail", which applies to both small signals and large (though not always identically). "Linear" means that the amplifier and all associated elements are operating in the linear range, i.e., the parametric relationship is independent of voltage or current level, or its previous history.

Noise. The amplifier's output can never settle within a given band of error if its output noise, however generated, is comparable to the magnitude of the band defined for settling. In addition to inherent amplifier circuit noise, the designer must also consider the effects of interference noise, whether coupled from the external environment, the power supply, the input signal, or the logic signals in the associated circuitry. For a discussion of noise in operational amplifier circuits, see *Analog Dialogue*, Vol. 3, No. 1.

DC Gain. To ensure the accuracy of the final value, the gain of an amplifier which must settle to within $\pm 0.01\%$ should be at least 10,000 for unity-gain followers, 20,000 for unity gain inverters, and more for higher-closed-loop-gain amplifiers. If the amplifier's open-loop input-output characteristic is reasonably linear, the error caused by slightly-lower gains may be compensated for under a given set of conditions by trimming the feedback ratio. For follower applications, the CMRR should be commensurate with the desired gain accuracy.

Drift and Offset. For high-precision applications, offset must be low or adjustable, and drift over the temperature range should be within the error corresponding to the desired accuracy. For example, $\pm 0.01\%$ error in $\pm 10V$ circuitry requires less than ± 1 millivolt ($\pm 1mV$ in inverter applications). Bias current drift may not be disregarded: 1 millivolt in $10k\Omega$ requires that bias current change less than 100 nanoamperes.


Dynamic Stability. Operational amplifiers designed for "optimum" response at high gains at low frequency often have transfer functions that provide only marginal stability when the loop is closed more tightly for near-unity gain and wide bandwidth. The amplifier used for fast settling to high accuracy should have a closed-loop response that is (at least theoretically) not much worse than critically-damped, as any oscillation or ringing may prolong settling time. Furthermore, in practical circuits, which have stray capacitance, the added lags caused by the external loop elements will cause an amplifier having insufficient phase margin to ring. For this reason, designers of fast-settling operational amplifiers strive to have the open-loop frequency characteristic be strongly dominated by a single time constant. This is stated in many ways, all having the same meaning: constant 90° phase shift, $-6dB/octave$ (or $-20dB/decade$) rolloff, unit lag, exponential response, etc.

Amplifiers characterized by this form of response may be considered to be integrators with limited DC gain, characterized by the following equation:*

$$A_{OL} = \frac{1}{\tau_x p} \left[\frac{A_0 \tau_x p}{1 + A_0 \tau_x p} \right] \cong \frac{1}{\tau_x p} \cong -j \frac{f_x}{f}$$

*Note: p is the Heaviside differentiation operator, corresponding roughly to s or $j\omega$, A_{OL} is open-loop gain, A_0 is DC gain, f_x is unity gain bandwidth, $\tau_x = 1/2\pi f_x$

For many non-state-of-the-art applications, the single time constant response has the further advantage of being calculable virtually by inspection. Small-signal settling time of amplifiers with more complex transfer functions does not lend itself to ready calculation. Figure 4 shows the open- and closed-loop response of an amplifier having this popular characteristic, and provides a table indicating the relationship between small-signal settling time and amplifier unity-gain bandwidth (f_x) or characteristic time (τ_x).

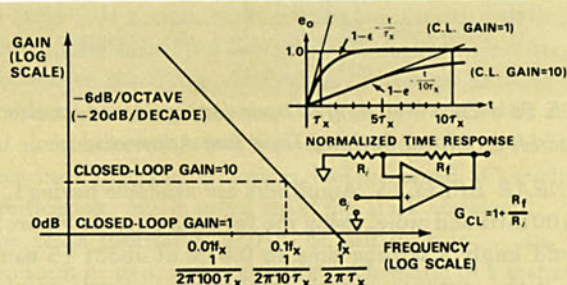

(a) Bode (amplitude vs. frequency) Plot, Feedback Circuit, Time Response

Percent error	$T_s = -2.303\tau_x \log_{10} \eta$ for τ_x (μs) or f_x (MHz)			
	Gain = 1		Gain = 10	
	T_s vs. τ_x (μs)	T_s vs. f_x	T_s vs. τ_x	T_s vs. f_x
100 η				
10 %	$2.303\tau_x$	$0.367/f_x$	$23.03\tau_x$	$3.67/f_x$
1.0 %	$4.606\tau_x$	$0.734/f_x$	$46.06\tau_x$	$7.34/f_x$
0.1 %	$6.909\tau_x$	$1.101/f_x$	$69.09\tau_x$	$11.01/f_x$
0.01%	$9.212\tau_x$	$1.468/f_x$	$92.12\tau_x$	$14.68/f_x$

(b) Settling Time vs. Fractional Error η for First-order Step Response as a Function of Open-Loop Characteristic Time (τ_x) or Unity-gain Bandwidth (f_x)

Figure 4. Closed-loop Response of Amplifier having $-6dB/Octave$ Open-Loop Amplitude Response

Well-Behaved Dynamic Response. Multistage amplifiers require the matching of poles and zeros in the linear transfer function to achieve a $6dB/octave$ characteristic.^{2,3} That is, $m = 1$ in the general expression:

$$A_{OL} = \frac{1}{\tau_x p} \left[\frac{A_0 \tau_x p}{1 + m A_0 \tau_x p} \right] \left[\frac{1 + m A_1 \tau_x p}{1 + A_1 \tau_x p} \right]$$

If the mismatch term, m , is substantially different from 1.0, and if A_1 is substantially less than the open-loop gain required for the desired degree of accuracy, the output of the amplifier will settle rapidly to within a small fraction (about $1/A_0$) of the final value, undershooting if $m > 1$, overshooting if $m < 1$, then settle exponentially to the final value with a surprisingly long time constant. (Fig. 5) The details of this consideration are described, and illustrated by scope pictures of the response of a low-speed dynamic model in the Appendix on pages 10 and 11.

Propagation Delay. At frequencies substantially beyond f_x , the amplifier's open-loop response starts to roll off more steeply and with greater phase shifts. The time-domain analogy to this is a brief interval of "dead time" of the order of nanoseconds, small compared to τ_x if the circuit is to be stable closed-loop. Because τ_x itself is not usually a limiting factor on settling time, propagation delay is even less so, in linear operation.

 


Figure 5. Pole-Zero Matching of open-loop gain and its effect on Closed-loop Linear Settling Time (see Appendix)

NONLINEAR EFFECTS. Amplifiers are available having f_x as high as 100 MHz and more. Using the formula given in Figure 4, this would imply a settling time to 0.01% of about 15 nanoseconds, if the response of such amplifier has a single unit-lag. Yet the specifications are more like 0.5 to 1.0 microseconds and more. Why? Here are some of the considerations:

Slew Rate. Within the amplifier, there are inherent semiconductor and circuit capacitances, as well as those added for stabilization; at the output, there is load capacitance. The rate of change of voltage at each point in the circuit is limited by the available current to charge the capacitance at that point ($dv/dt_{max} = I_{max}/C$). In the above example, if the amplifier were operating linearly over its whole output range, the initial rate of rise in response to a step would have to be $10V/1.6ns = 6,280$ volts per microsecond! In order to drive a 10pF load without saturating, at least 62.8mA must be available.

ΔE	f_x (MHz)				τ_x (ns)				
	0.1	1.0	10	100	3.2	10	100	1000	10 μs
10V	6.3	63	630	6,300	3,100	1000	100	10	1.0
5V	3.1	31	310	3,100	1,550	500	50	5	0.5
2V	1.3	13	130	1,300	620	200	20	2	0.2
1V	0.6	6	60	600	310	100	10	1	0.1

TABLE 1 - First-Order Response: Required Initial Rate of Change (Volts/ μs) as a Function of Step Size, f_x , and τ_x .

$$\left. \frac{de}{dt} \right|_{max} = \frac{\Delta E}{\tau_x} = \Delta E 2\pi f_x$$

C	$\frac{de}{dt}$	1	10	20	50	100	200	500	1000
10pF	10 μA	0.1	0.2	0.5	1.0	2.0	5.0	10.	20.
20pF	20 μA	0.2	0.4	1.0	2.0	4.0	10.	20.	50.
50pF	50 μA	0.5	1.0	2.5	5.0	10.	25.	50.	100.
100pF	0.1	1.0	2.0	5.0	10.	20.	50.	100.	200.
200pF	0.2	2.	4.0	10.	20.	40.	100.	200.	500.
500pF	0.5	5.	10.	25.	50.	100.	250.	500.	

TABLE II - Current (mA) to Maintain a Given Slew Rate (V/ μs) As a Function of Capacitance.

$$i = C \frac{de}{dt}$$

Tables I and II show the relationships between step size, slew rate required for exponential response, capacitor size, and required driving current, for a somewhat less exotic selection of

parametric values. Table I gives examples of the slew rate requirement for linear behavior (i.e., exponential time response) as a function of step size and either f_x or τ_x , and Table II indicates the current required to drive a given capacitive load at the appropriate value of slew rate. In practice, such slew rates (in relation to small-signal frequency response) cannot be achieved: the excessive currents required would degrade accuracy and drift specifications; also the operational amplifier would be required to respond linearly to 100% error at its input (i.e., full-scale differential input). Typically, then, the amplifier slews, at a maximum rate 5 to 100 times less than that implied by its small signal bandwidth, up to the vicinity of full scale, recovers, and settles exponentially (either aperiodically or with oscillations).

Recovery. During nonlinear slewing, saturation imposes charge changes away from normal operating values on the circuit capacitances (including minority carrier storage in semiconductors). These must be discharged back to equilibrium values before the amplifier can operate normally. Thus, there is a period of recovery which is comparable to the period of slewing, but it may be substantially greater if many internal stages are involved. Fast slew rate, therefore, is not by itself a good indicator of a fast-settling amplifier. Some amplifiers with extremely-large slew rates have excessive recovery time and greater overall settling time than other amplifiers having more modest slew rates. In Figure 6, the Model 1011 tested has a slew rate of 70V/ μs , but settles to 0.01% in 6 μs , whereas the Model 40 has a slew rate of only 10V/ μs , but settles to 0.01% in 5 μs .

 


Figure 6. Comparison of Two Amplifiers Having Similar Settling Times, But Differing Slew Rates.

OTHER EFFECTS. Dielectric absorption (hysteresis), both internal to the amplifier and inherent in external bypass capacitors, may be an important factor in circuits requiring settling to 0.01%. Most capacitors used in electronic circuits have non-negligible dielectric hysteresis when used in precision applications; the popular ceramics, for example, may have typically 5%. When a capacitor is subjected to a sudden stress, it requires a period of "soaking" to return to internal charge equilibrium.⁴ Thus the dC/dt term cannot be neglected in the definition of current, $i = dQ/dt = d(CV)/dt = C dv/dt + V dC/dt$. Dielectric absorption is responsible for the long "tails" (typically 10 to 100 μs) often greatly extending the final-settling interval for otherwise fast amplifiers. With proper attention, an amplifier's settling time to 0.01% need not greatly be affected by dielectric

absorption, and minimization of its effects in settling to 0.1% is even less difficult to achieve.

Thermal Transients ("self-heating" effects). During slewing, the normally equal distribution of dissipations in (particularly) the input stage may become grossly unbalanced. Amplifiers designed to be fast usually run at "rich" values of current (to enable rapid handling of voltage changes across circuit capacitances and keep impedance levels down), but because a differential temperature change of one degree in a bipolar transistor stage can cause about 2 millivolts of drift (0.02% of 10-volt full scale), the time required to recover thermal balance after large input transients is a factor tending to limit the choice of currents in the input stage. In addition, a large change in load current may significantly change dissipations in the output stage (and hence temperatures inside the amplifier package), and if these temperature changes are unequally conducted to the two sides of the input stage, transient, as well as steady-state unbalances can result. Input circuit effects are less serious in inverting amplifier configurations than they are in unity-gain followers, where common-mode swing (equal to full-scale input voltage swing) may cause substantial changes in input-stage dissipation. Self-heating effects will generally not affect the settling time to 0.1%, and – in well-designed amplifiers – will not substantially increase the settling time to 0.01%. However, where this design factor is neglected, they can cause "tails" exceeding milliseconds in duration.

MINIMIZING SETTLING TIME SUGGESTIONS FOR THE CIRCUIT DESIGNER

If the designer of a typical fast-settling operational amplifier has done the job properly, taking into account all the factors we have mentioned, he has made available a device that can be demonstrated to have a specified accuracy of 0.01% and settling time less than 1 μ s. However, an operational amplifier is a building block in a circuit that also has a feedback network, input connections, power supply connections, output connections, and a number of external components. What has been painstakingly gained in amplifier design can be lost in short order through careless circuit design. Some of the elements of good design are these:

CONNECTIONS. It is of utmost importance that the power supply leads be adequately bypassed directly at the amplifier's terminals* and that especial care be taken in the signal and power ground circuits to avoid inducing or generating extraneous voltages in the ground signal paths.⁵

COMPONENTS. Resistors are preferably metal film types, because they have less capacitance and stray inductance than wirewound types, and are now available with excellent accuracies and temperature coefficients.

Diodes are hot carrier types for the very fastest-settling applications, but 1N914 types are suitable for more routine uses.

Capacitors in critical locations are polystyrene, teflon, or polycarbonate, to minimize dielectric absorption.

CIRCUIT. For the fastest settling times, keep leads short, orient components to minimize stray capacitance, keep circuit

*Most well-designed discrete op amps have bypass capacitors built in, but the designer should never take it for granted that they will be adequate for his application, until he can so demonstrate.

impedance levels as low as consistent with the output capabilities of the amplifier and the signal source, reduce all external load capacitances to the absolute minimum. Don't overlook sockets or printed circuit board mounting as possible sources of dielectric absorption. Avoid pole-zero mismatches in the feedback networks used with the amplifier. Minimize noise pickup.

SPECIFYING SETTLING TIME

On page 2 is a statement relating to alternate definitions of settling time employed in some portions of the industry. When it comes to specifying settling time, there are as many formats as there are manufacturers. Until the format to be discussed and demonstrated below was developed, no known manufacturer, including Analog Devices, had presented, as a settling time specification, much more than the stark statement: "settling time as an inverter to 0.01% of full scale is . . . μ s," plus a waveform or two, and a simplified schematic of a test setup.

Important unanswered questions were: "What are the trade-offs?" How much can settling time be reduced by reducing full-scale signal level (and thus the slewing and recovery periods)? Suppose one does not desire 0.01% accuracy, but wishes instead to determine the size of error band for a given step size and settling time? Is settling time symmetrical for positive and negative excursions?

V CURVES (Figure 7)

A graphical form of specification has been developed that helps answer many of the above questions. Because of the shape of the curves when plotted linearly, they have been dubbed "V Curves." For increased information content, however, a semi-log plot has been adopted. Each curve represents the measured settling time (microseconds) vs full-scale step magnitude (volts) for a given final error band. Three error bands were chosen: ± 1 mV, ± 10 mV, ± 100 mV, corresponding to $\pm 0.01\%$, $\pm 0.1\%$, $\pm 1\%$ of full scale, respectively. The percentage error is the ratio of error band to output step. For example, $1\text{mV}/5\text{V} = 0.02\%$.

Information is given for both positive and negative step polarities; the two standard configurations shown are as unity gain inverter and unity gain follower. It is of course possible to obtain data for curves for other conditions, and we welcome comments by our readers on the adequacy and relevance of this form of specification, along with suggestions for improvements to the format.

Figure 7 shows a set of theoretical V Curves for an ideal amplifier having no slew rate difficulties whose τ_x is 100ns

 


Figure 7. Example of V Curves. Theoretical Amplifier With First-Order Linear Response.

($f_x = 1.6\text{MHz}$). Figure 8 shows the curves, accompanied by photographs of typical oscilloscope traces, for AD Model 45, a FET-input amplifier capable of settling to within $\pm 0.01\%$ of full scale in less than $1\mu\text{s}$.

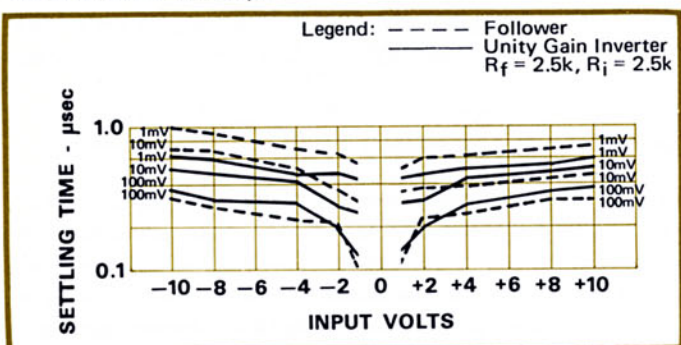


Figure 8. Example of V Curves. Model 45: a Sub-microsecond-settling FET-Input Economy Op Amp.

AMPLIFIER V-CURVES

In Figure 9 are shown V Curves for an assortment of amplifiers. Although it is evident that only a few of these types have been specifically optimized for settling time,


1. a number of them settle quickly enough to be used for a variety of less critical applications
2. others among them are general-purpose types for which detailed settling time data have simply never been available. Their wide usage and low cost make such data particularly useful.

Further, in order to assist the reader in obtaining perspective on relative amplifier behavior within the industry by a consistent set of measurements, we have included data from our measurements on several amplifier types which, though not available from Analog Devices, may be of interest to our readers. Included are:


- Fig.9a Model 40, a low-cost general-purpose FET-input type
- Fig.9b Model 149, a high-slew rate FET-input type
- Fig.9c Model 120, a bipolar-input fast feed-forward type (inverting only)
- Fig.9d Model 180, a low-drift bipolar type
- Fig.9e Model AD741, a bipolar-input general-purpose IC type
- Fig.9f Model AD503, a FET-input IC-type with 741 output stage (but increased speed!)
- Fig.9g Model $\mu\text{A}715$, a fast-settling IC type, using recommended stabilization (Fairchild Semiconductor)
- Fig.9h Model 1011, a FET-input medium fast amplifier (Teledyne Philbrick/Nexus)
- Fig.9i Model 3308, a low-cost general-purpose FET-input type (Burr-Brown)

The measurements which resulted in these curves were by and large made during the summer and fall of 1969, and so may not include amplifiers that approach the state of the art today. In addition to the curves published here for the representative selection of types, a considerable amount of data has been taken on a wide variety of other amplifier types in our product line. We will be pleased to respond to inquiries regarding specific types for which information may be available.


Figure 9. Amplifier V Curves and Typical Responses. →

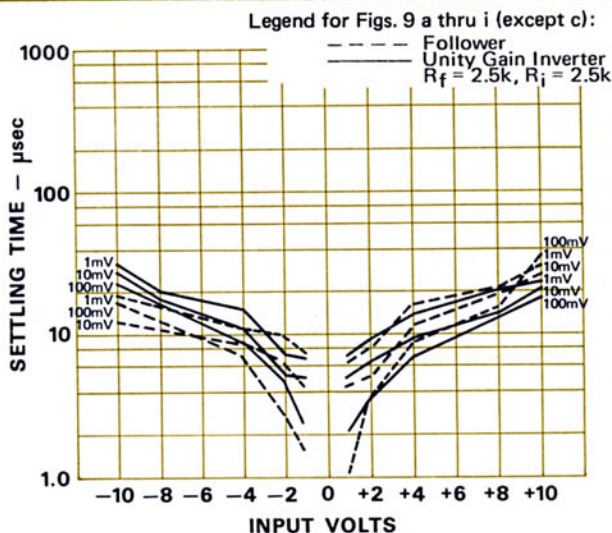


(a) Model 40

 


(b) Model 149

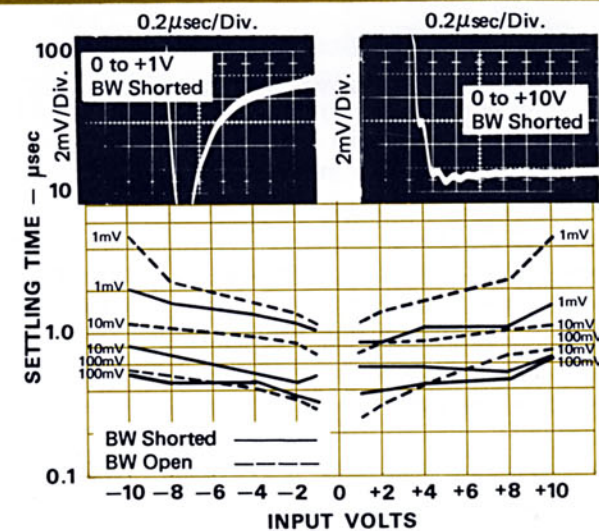


(c) Model 120 (BW Shorted and BW Open)

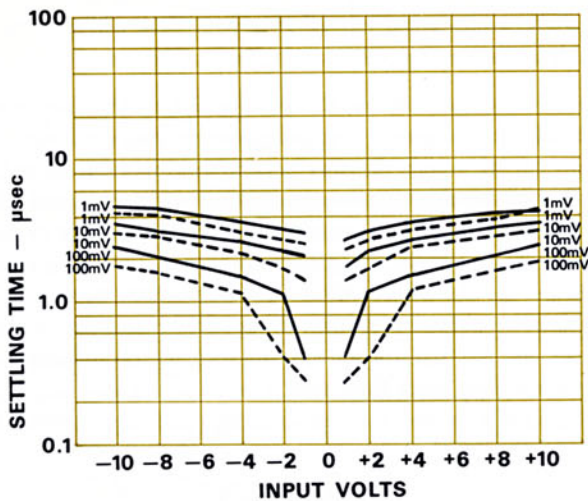


(d) Model 180

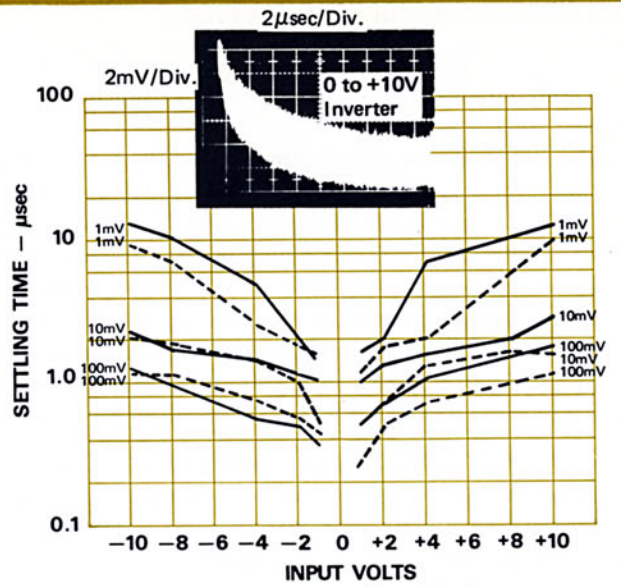


(g) Model $\mu A715$ (Fairchild)

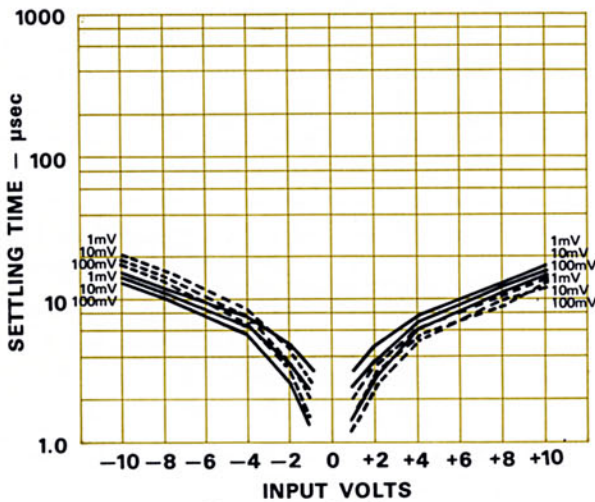


(e) Model AD741

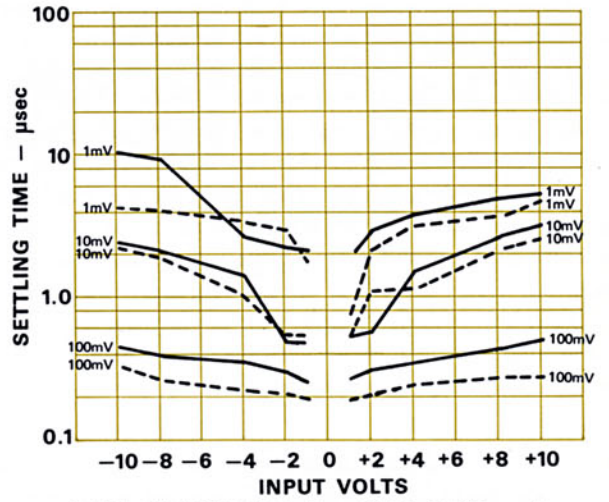

 (h) Model 1011 (Teledyne Philbrick/Nexus)



(f) Model AD503

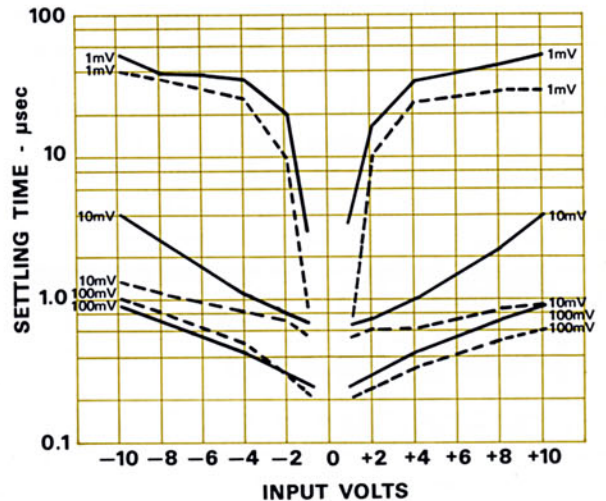

(i) Model 3308 (Burr-Brown)

LIMITATIONS OF SPECIFICATIONS

CIRCUITS STUDIED. It is usually the case that for most operational amplifiers, the fastest-settling performance will be obtained when the amplifier is operated as either a unity-gain inverter or as a follower. (*Slewing* may be more rapid, however, for some types, at high closed-loop gains). For this reason, data has been taken at unity gain using both inverter and follower configurations. The amplifiers operate with no external resistive or capacitive load, other than the comparator used for the measurement, the leads to it, and the feedback circuit impedance in the inverting configuration. The resistance component has been confined to a pair of 2.5k Ω resistors, to enable amplifiers having 5mA output current to be measured.

EXTRAPOLATION OF SETTling TIME MEASUREMENTS. Because of the many factors that influence settling time, it may be dangerous to assume that data may be interpolated (or worse, extrapolated), especially for those types having radical changes in shape between adjacent curves, or in different portions of the same curve.

AMPLIFIER STABILIZATION NETWORKS. The methods used for feedback stabilization can have quite drastic effects on the amplifier's settling time because the amplifier's settling characteristics are intimately related to the location of both the open loop and closed loop poles and zeros. Anything the user does that will reduce the amplifier's bandwidth will usually lengthen settling time. For example, multiple input summing resistors decrease loop gain; added summing point capacitance requires feedback capacitance to compensate, resulting in smoother (but often slower) settling; output cable capacitance can cause peaking, and may require a load isolation resistor, which will result in slower overall response; stray feedback capacitance. Even such a simple thing as placing a resistive load on the amplifier may reduce its open-loop gain (at all frequencies, including f_x), and thus its loop gain and settling time.

CAVEAT. Since settling time specifications cannot possibly include (or be extrapolated to) all possible situations, they should be used as a guide for preliminary selection of an amplifier to fit a given application. In all cases, and especially where the application conditions are significantly different from those used in specifying the amplifier, there can be no substitute for actual trial of the amplifier in the proposed circuit to determine whether it will perform as desired. Often, the manufacturer's experience with customers having a wide variety of applications can be helpful, and — especially where op amps are key elements in large important projects — designers are urged to make use of the manufacturer's applications engineers for helpful suggestions and judgements based on their experience.

MEASURING SETTling TIME

INVERTING CONFIGURATION

There are a number of circuit approaches that may be used for observing the settling time of an inverting amplifier. Perhaps the simplest (or at least the most obvious) consists of measuring the voltage at the amplifier's own error point. Though superficially simple, this method has several deficiencies: the added

capacitance of the measuring device affects the closed-loop dynamics, the dynamic input impedance of the amplifier may cause errors in estimating the actual gain error, and feedback circuit dynamics may introduce errors that will not be observable at the error point.

Instead of using the actual summing point of the amplifier, it is feasible to construct a quasi-summing point, as shown in Figure 10. Although measurement errors may be caused by capacitance at this quasi-summing point, it does not affect amplifier performance. Because the comparator which observes the error is comparing the proxy error signal with "ground," this is by far the easiest kind of measurement to make. The comparator's output is readily clamped to minimize overdrive of both the comparator and the monitoring oscilloscope, the comparator may have gain, and it may also settle more slowly than the amplifier under test (its settling time errors are second-order, in this case.)

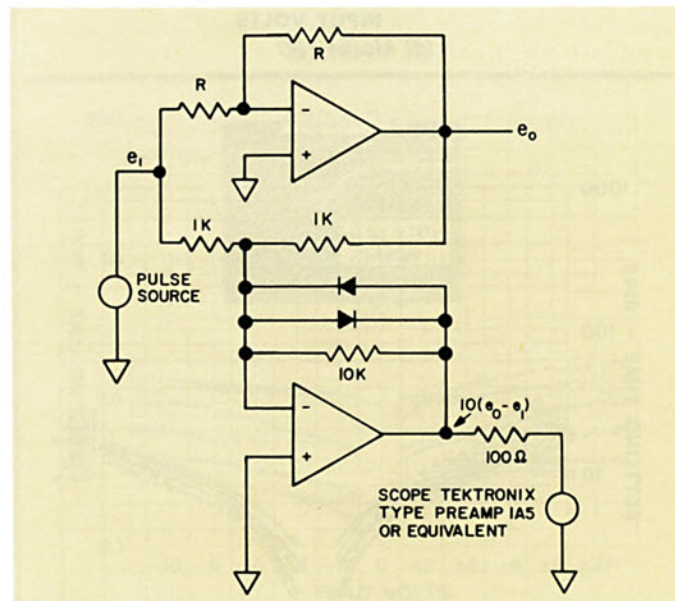


Figure 10. Settling Time Measurements at Quasi-Summing Point.

The above discussion pertains to an amplifier used with a voltage signal and input and feedback resistors. However, if the signal is a current step (amplifier used as a current-to-voltage transducer), the output step response must be compared with the expected final value. Since the comparator is taking the difference directly, rather than observing an error point, it will be subjected to wider swings, and it must settle substantially (at least 2 to 3 times) faster than the amplifier under test to avoid introducing excessive delay and time uncertainty. Needless to

IN THE NEXT ISSUE

Prediction can be dangerous in this game (as witness our prediction of four Dialogue issues in 1969, which turned out to be 25% accurate). However, for the next issue we are planning to publish two sorely-needed items:

1. A new approach to describing the performance of and specifying analog multipliers.
2. A comparative evaluation of today's electrometers, including parametrics, MOS-FET's, and some suggestions for getting the most out of parametrics in the area of femtoamp (i.e., 10^{-15} amp) resolution levels.

say (having already dwelt heavily on the problems of designing a fast-settling amplifier itself), the problem of designing and instrumenting a comparator to test settling time (and properly interpreting the results obtained with it) presents challenges that make the amplifier design job look easy.

NON-INVERTING CONFIGURATION. The most usual circuit to be tested is the unity-gain follower. It requires direct comparison between the input step and the output signal as they swing through the entire common-mode range. Thus the problem, and its instrumentation, may be similar to that of the inverter with current source.

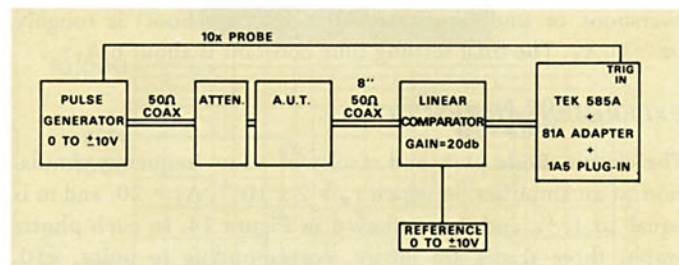


Figure 11. Instrumentation for Settling Time Measurement

EQUIPMENT. Figure 11 shows a typical measurement system for settling time. Commercially available comparators, such as the Tektronix Models W and 1A5, the Hewlett-Packard 1803A, and the Adage Ultranull NDI are useful, but their applicability is limited to settling times somewhat greater than $1\mu\text{s}$ for 0.01% measurements. As a rule, specially-designed and constructed equipment is required in order to assure oneself that the system requirements are met, including low noise, minimization of excess lead inductance, capacitance, and (naturally) adequate settling time.

The pulse generator used for the measurement should have rise times of the order of 10ns, with a flat top occurring within (say) a few hundred nanoseconds of the step transition. A square wave of about 100Hz should be applied initially to determine output amplitude and whether the amplifier exhibits slow recovery phenomena (due to thermal transients, dielectric absorption, etc.) Once the observer is satisfied of the absence of long tails, a much faster rate may be used to observe fine structure. Some low cost signal generators exhibit a degree of pulse "droop," that may cause what appear to be long tails in observations of settling time of an amplifier, especially in the follower configuration (because the amplifier output is being compared with a dc level). The dummy summing point approach of Figure 10 is less sensitive to pulse droop, because addition of input and output waveforms tends to cancel the droop, assuming that the amplifier reproduces the droop with fidelity.

Most of the measurements performed to obtain the V curves used the specially-constructed square wave source and comparator schematically illustrated in Figures 12 and 13. The square wave source is capable of supplying both positive and negative outputs variable from zero to ± 10 volts, with a rise time of about 15 nanoseconds.

The comparator shown was used for all but the fastest amplifiers. It settled in about $0.75\mu\text{s}$ for measurements in a 1mV error band, and about $0.5\mu\text{s}$ for measurements in the 10mV error band. Its performance had been intentionally compro-

mised by adjusting its input impedance so that it could be used for measuring outputs of G.P. amplifiers having only 5mA available. (Amplifiers designed for fast settling usually have outputs of 20mA or more).

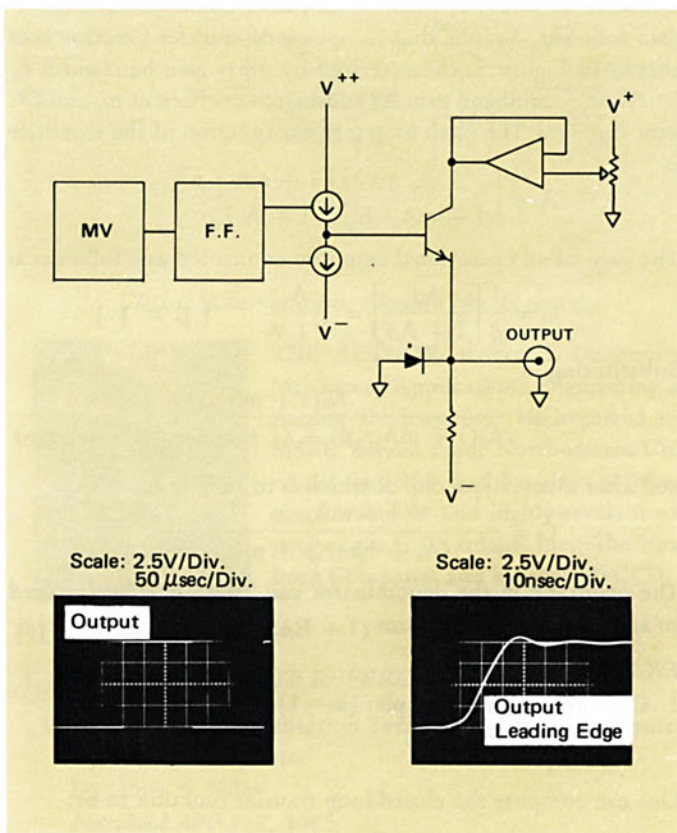


Figure 12. Square Wave Source, Simplified.

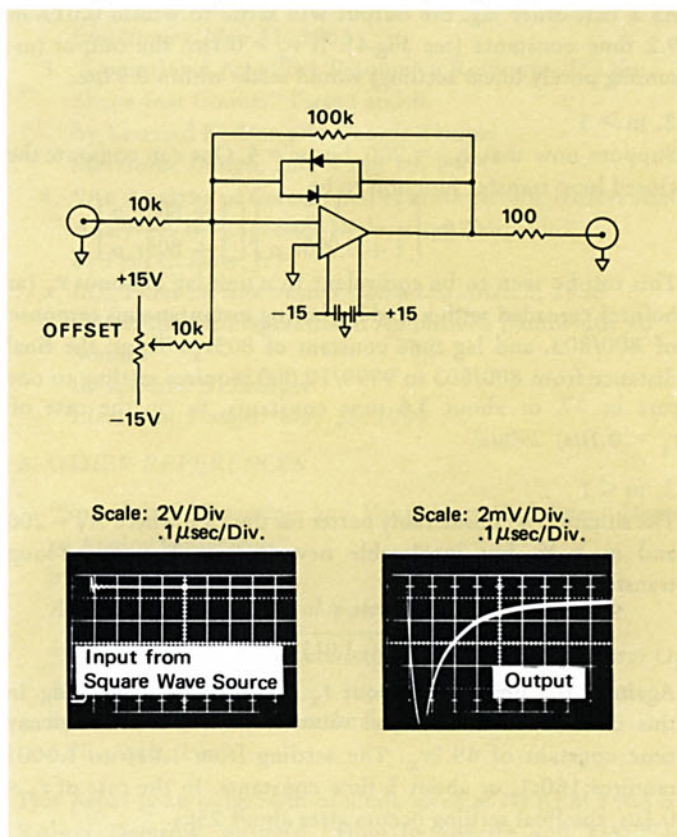


Figure 13. Comparator Simplified

EFFECTS OF POLE-ZERO MISMATCH ON LINEAR-SETTLING INTERVAL

Consider an ideal* operational amplifier connected as a unity-gain follower. Assume that its open-loop transfer function is as shown in Figure 5, characterized by unity-gain bandwidth f_x ($= 1/2\pi\tau_x$), midband gain A_1 , mismatch coefficient m , and DC gain A_0 ($\rightarrow \infty$). The open loop transfer function of the amplifier is

$$A = \left[\frac{A_0}{1 + mA_0\tau_x p} \right] \left[\frac{1 + mA_1\tau_x p}{1 + A_1\tau_x p} \right]$$

The gain of an operational amplifier connected as a follower is

$$G = \frac{1}{\beta} \left[\frac{A\beta}{1 + A\beta} \right] = \frac{A}{1 + A} \quad (\beta = 1)$$

Substituting,

$$G = \frac{A_0(1 + mA_1\tau_x p)}{A_0(1 + mA_1\tau_x p) + (1 + mA_0\tau_x p)(1 + A_1\tau_x p)}$$

and after many steps, one of which is to assume $A_0 \rightarrow \infty$,

$$G = \frac{1 + mA_1\tau_x p}{1 + (A_1 + 1)m\tau_x p + mA_1\tau_x^2 p^2}$$

The quadratic in the denominator can, of course, be factored to an expression of the form $(1 + Bp)(1 + Cp)$

EXAMPLES

1. Consider now an example: ($m = 1$)

$$A_1 = 200 \quad (A_0 \rightarrow \infty)$$

$$m = 1$$

One can compute the closed-loop transfer function to be:

$$G = \frac{1}{1 + \tau_x p}$$

As a first-order lag, the output will settle to within 0.01% in 9.2 time constants (see Fig.4). If $\tau_x = 0.1\mu s$, the output (assuming purely-linear settling) would settle within $0.92\mu s$.

2. $m > 1$

Suppose now that $A_1 = 200$, but $m = 4$. One can compute the closed-loop transfer function to be

$$G \cong \left[\frac{1}{1 + 0.996\tau_x p} \right] \left[\frac{1 + 800\tau_x p}{1 + 803\tau_x p} \right]$$

This can be seen to be equivalent to a unit-lag of about τ_x (as before) cascaded with a lead-lag having instantaneous response of $800/803$, and lag time constant of $803\tau_x$! To go the final distance from $800/803$ to $9999/10,000$ requires settling to one part in 37, or about 3.6 time constants, or (in the case of $\tau_x = 0.1\mu s$) $290\mu s$!

3. $m < 1$

The situation is considerably better for the case where $A_1 = 200$ and $m = 1/4$, but intolerable nevertheless. The closed-loop transfer function is

$$G \cong \left[\frac{1}{1 + 1.015\tau_x p} \right] \left[\frac{1 + 50\tau_x p}{1 + 49.2\tau_x p} \right]$$

Again, it is a unit lag of about τ_x , cascaded with a lead-lag. In this case, there is an initial value of $50/49.2$, with a decay time constant of $49.2\tau_x$. The settling from 1.016 to 1.0001 requires 160:1, or about 5 time constants. In the case of $\tau_x = 0.1\mu s$, the final settling occurs after about $25\mu s$.

*"Ideal" in terms of input and output impedances, CMRR, and every other respect, except gain and frequency response.


In the above examples, neglecting the initial fast settling interval accounted for a conservative 7 time constants (i.e., for settling to well within 0.1%), or about $0.7\mu s$.

APPROXIMATION



A reasonable approximation for pole-zero mismatch response calculations, especially for m closer to unity than in the exaggerated example above, is to assume that the amplifier settles to within $1/A_1$ initially in exponential manner, with time constant τ_x . The number of time constants can be estimated quickly from the table in figure 4. The amount of overshoot or undershoot (positive for overshoot) is roughly $(m - 1)/A_1$. The final settling time constant is about $m A_1 \tau_x$.

EXPERIMENTAL RESULTS



The circuit, Bode plot, and results of a low-frequency simulation of an amplifier, in which $\tau_x = 2 \times 10^{-4}$, $A_1 = 20$, and m is equal to 1, $1/2$, and 2, are shown in Figure 14. In each photograph, three traces are shown, corresponding to unity, $\times 10$, and $\times 100$ magnification of the error band (i.e., the final settling interval). In this example, the amplifier simulated was connected as a unity-gain inverter. The reason the simulation was performed at low frequency was to retain as complete as possible control over the idealized characteristic, eliminating slewing phenomena, dielectric absorption, etc.

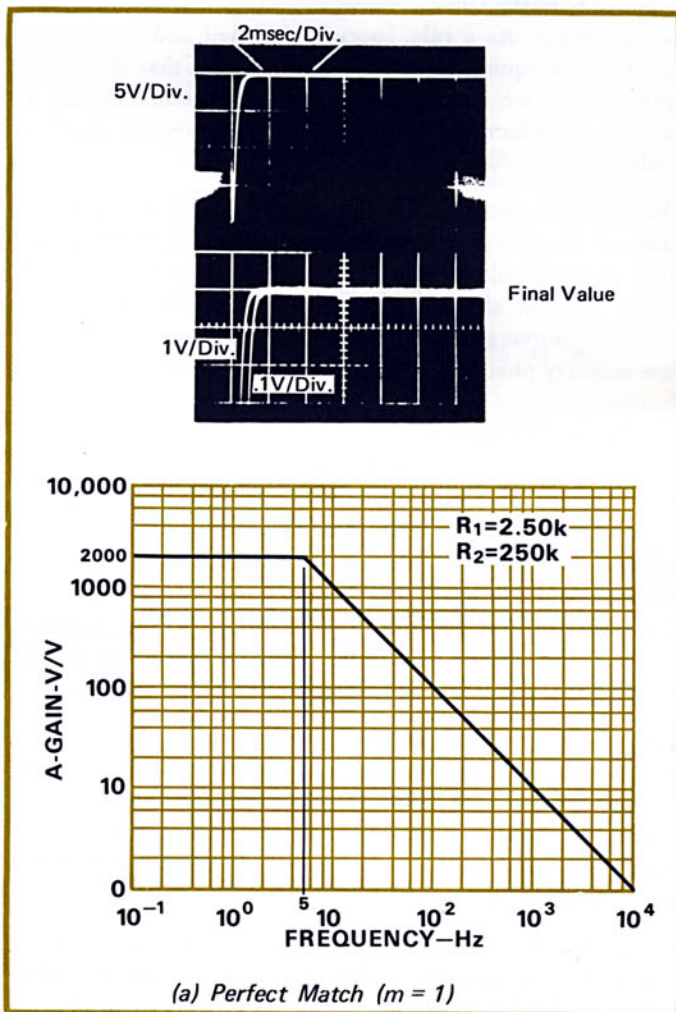

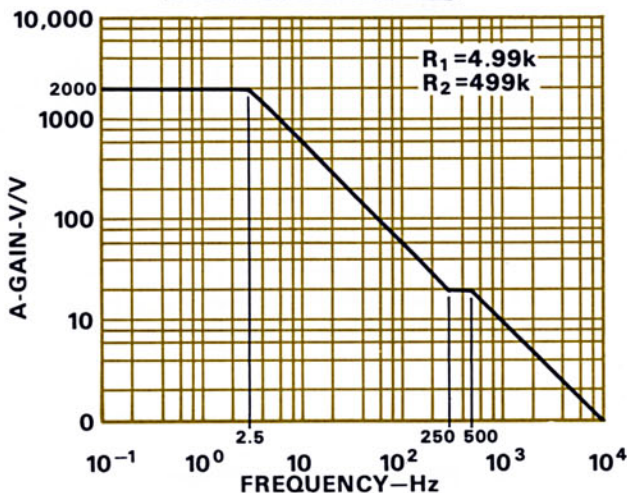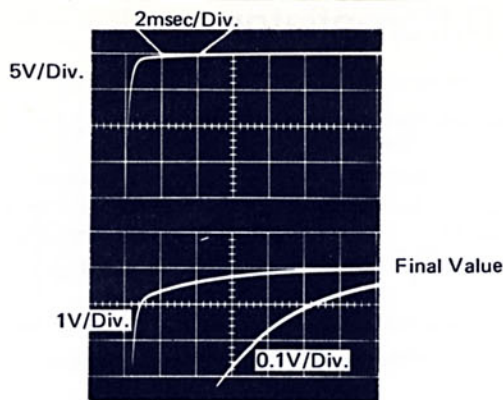
(a) Perfect Match ($m = 1$)
Figure 14. Small-Signal Settling as a Function of Pole-Zero Match (Low Frequency Model)



(b) Levelling-off of Response ($m = 2$)

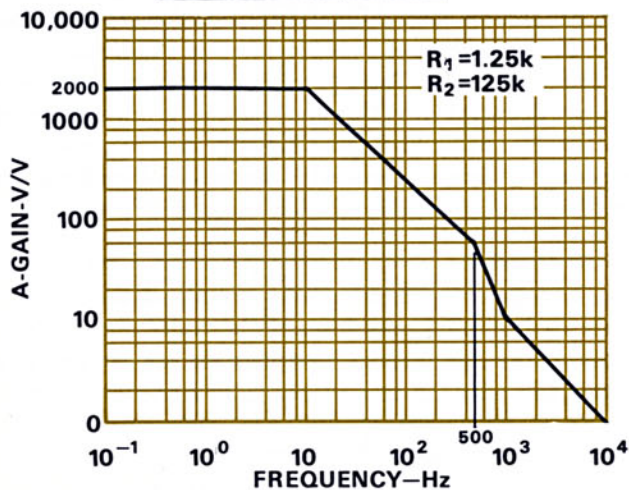 

(c) Steepening Slope ($m = \frac{1}{2}$)

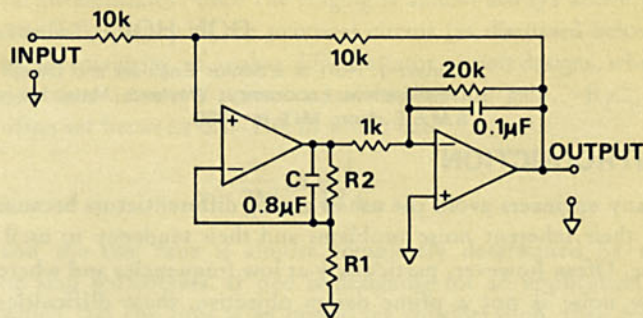

Circuit Schematic For Figures 14a, b, and c.



THE AUTHOR—Robert I. Demrow is Manager of Applications Engineering at Analog Devices, Inc. He received his MSEE degree from Northeastern University in 1958, and has since received much valuable and highly-relevant experience at G.E., Adage, Inc., The Foxboro Company, and Honeywell CCD.

BIBLIOGRAPHY

A. SPECIFIC FOOTNOTE REFERENCES

1. "Frequency Compensation Techniques For An Integrated Operational Amplifier"
by James N. Giles
Fairchild APP-117. 1965
2. "Latest Approach to Integrated Amplifier Design"
by F. D. Waldhauer
Electronics. May 31, 1963
3. "Operational Amplifier Frequency Response—It's the Shape that Counts" Parts I and II
by Leonard Kedson and George Tempei
Electronic Design. July 5 and 19, 1965
4. "An Analysis of Certain Errors in Electronic Differential Analyzers II—Capacitor Dielectric Absorption"
by Paul C. Dow, Jr.
IRE Trans on Electronics Computer. March, 1958
5. "Extending An Operational Amplifier's Bandwidth To 50mHz"
by Richard D. Brugger
Electronic Design. May 25, 1964

B. OTHER REFERENCES

- "Specifying, Measuring, and Using Very High Speed Digital to Analog Converters"
by James J. Pastoriza
Analog Devices Technical Note
- "High-Frequency Characteristics of Wide Band Inverter Op Amps"
by Heinrich Krabbe (now Analog Devices—West)
EEE. April, 1969

This paper is an outgrowth of a talk given at NEREM 1968 by Robert Demrow, entitled "How to Specify and Test Fast Settling Operational Amplifiers."