

BY BONNIE BAKER

## Transimpedance-amplifier-noise issues

How much noise is too much noise in a photodiode-preamplifier circuit? You can derive the noise performance of a transimpedance amplifier (Figure 1a) with calculations or by using a Spice simulation (Reference 1). When calculating the noise performance of the circuit, consider six regions in the frequency spectrum (Figure 1b) and add each region with a root-sum-square equation or the following equation (Reference 2):

$$V_{OUT}(\text{NOISE}_{RMS}) = \sqrt{e_1^2 + e_2^2 + e_3^2 + e_4^2 + e_5^2 + e_{RF}^2}$$

The first five regions are equal to the multiple of the areas under the closed-loop-gain and amplifier-noise-density curves. The area under the noise-density curve in the  $e_1$ , flicker-noise ( $1/f$ ), region is  $V_{1/f:FB-f_A} = A_N \sqrt{\ln(f_B/f_A)}$ , where  $A_N$  is the amplifier's input-noise-density at 1 Hz and  $f_B$  is the corner frequency where the flicker noise tapers off. For many CMOS or FET amplifiers, the flicker-noise region usually ranges from dc to 100 or 1000 Hz. A calculation proves that the contribution to noise in this low-frequency region is relatively low:

$$e_1 = (1 + R_F/R_{PD}) \times A_N \times \sqrt{\ln(f_B/f_A)}$$

where  $R_F$  is the feedback resistor and  $R_{PD}$  is the device's parallel resistance.

In the  $e_2$  region, multiply the broadband noise of the amplifier, the closed-loop dc-noise gain  $(1 + R_F/R_{PD})$ , and the square root of the region's bandwidth. Again, the contributed noise in this region is usually relatively low because of its location in the lower frequency range.

$$e_2 = (1 + R_F/R_{PD}) \times e_N \times \sqrt{f_p - f_z}$$

Calculate the noise contribution and the  $e_3$  region in the same manner with  $f_p = 1/[2\pi(R_{PD} || R_F)(C_{PD} + C_{CM} + C_{DIFF} + C_F + C_{RF})]$  and  $f_z = 1/[2\pi(R_F)(C_F + C_{RF})]$ .

$$e_3 = (1 + R_F/R_{PD}) \times e_N \times (1 \text{ Hz}/f_z) \times \sqrt{f_p/3 - f_z/3}$$

where  $C_{PD}$  is the device's capacitance and  $C_{DIFF}$  is the differential amplifier's capacitance.

The noise in regions  $e_4$  and  $e_5$  uses the higher-frequency gain of the closed-loop-gain curve with the value of  $C_1$  being the parallel combination of the input capacitors, or  $[C_{P-R1} || 2C_{CM} || C_{DIFF}]$ , and  $C_2$  is the parallel combination of  $C_F$  and  $C_{RF}$ .


$$e_4 = (1 + C_1/C_2) \times e_N \times \sqrt{f_{AOL} - f_p}$$

$$e_5 = (1 + C_1/C_2) \times e_N \times \sqrt{\pi \times (f_U - f_{AOL})/2}$$

The sixth part of the noise equation,  $e_6$ , represents the noise contribution of the feedback resistor. The amplifier does not gain the contribution of noise from the feedback resistor:

$$e_6 = \sqrt{4 \times K \times T \times R_F \times (BW)}$$

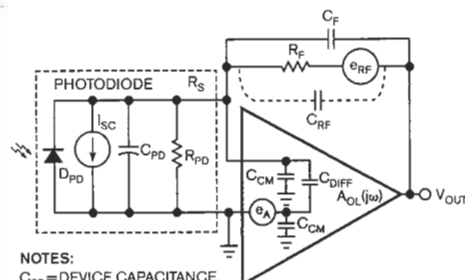where  $K$  is Boltzmann's constant, which is  $1.38 \times 10^{-23}$ ;  $T$  is temperature



## NOTES:

$C_{PD}$  = DEVICE CAPACITANCE.  
 $R_{PD}$  = DEVICE PARALLEL RESISTANCE.  
 $e_{RF}$  = RESISTOR-VOLTAGE NOISE.  
 $e_A$  = AMPLIFIER-VOLTAGE NOISE.  
 $C_F$  = FEEDBACK CAPACITOR.  
 $R_F$  = FEEDBACK RESISTOR.  
 $C_{RF}$  = FEEDBACK-RESISTOR PARASITIC CAPACITANCE.  
 $C_{CM}$  = COMMON-MODE-AMPLIFIER CAPACITANCE.  
 $C_{DIFF}$  = DIFFERENTIAL-AMPLIFIER CAPACITANCE.  
 $A_{OL}(j\omega)$  = AMPLIFIER OPEN-LOOP GAIN.

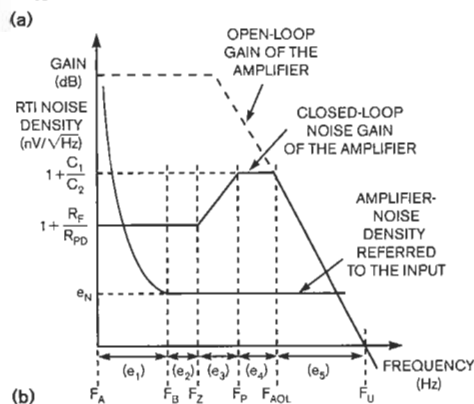


Figure 1 A typical transimpedance photo-sensing circuit (a) has five regions of overall noise response (b).

in Kelvin;  $R_F$  is the feedback resistor in ohms; and  $BW$  is the bandwidth of interest.

When asking how much noise is too much noise in this photodiode-preamp circuit, consider that a 12-bit system operating with a 5V input range has an LSB of 1.22 mV. The LSB for a 16-bit system with the same input-voltage range is 76.29  $\mu$ V. Both LSBs are peak-to-peak numbers, and the values in this column are root-mean-square values (Reference 3). **EDN**

Bonnie Baker is a senior applications engineer at Texas Instruments. She can be reached at [bonnie@ti.com](mailto:bonnie@ti.com).

For a list of the references cited in this column, go to [www.edn.com/081002bb](http://www.edn.com/081002bb).