
Increasing voltmeter input impedance to 10^{12} ohms

by J.R. Laughlin

San Jacinto College, Pasadena, Texas

Most commercial voltmeters, whether they have analog or digital readouts, provide relatively low input impedances, only on the order of 10 megohms, which makes accurate voltage measurements difficult for many circuits. But, by combining a couple of low-leakage field-effect transistors with an operational amplifier, you can

raise the input resistance of your voltmeter to approximately 1,000,000 megohms.

Any dc voltage applied to the gate of the input FET will be reproduced at the circuit's output with sufficient amplitude to drive any type of voltmeter. If Motorola's type MC1436 op amp is used with a 35-volt supply, the circuit can handle input voltages as high as 30 v without an attenuator. If a wide frequency response is desired, Signetics' type 531 op amp can be used with a lower supply voltage. And, because of its low current drain, National's type LM308 op amp is best for battery-operated voltmeters.

A voltage divider to ground at the circuit's input permits higher voltage measurements to be made, but significantly lowers the circuit's input resistance. However,

