

Advertisement



[BLOGS < HTTPS://WWW.EDN.COM/CATEGORY/BLOG/>](https://www.edn.com/category/blog/)

[THE SIGNAL < HTTPS://WWW.EDN.COM/CATEGORY/BLOG/THE-SIGNAL/>](https://www.edn.com/category/blog/the-signal/)

Op Amp Noise—but what about the feedback?



[FEBRUARY 11, 2013 <](#)

[HTTPS://WWW.EDN.COM/OP-AMP-NOISE-BUT-WHAT-ABOUT-THE-FEEDBACK/>](https://www.edn.com/op-amp-noise-but-what-about-the-feedback/)

BY [BRUCE TRUMP <](#)

[HTTPS://WWW.EDN.COM/AUTHOR/BRUCE-TRUMP/>](https://www.edn.com/author/bruce-trump/)

[COMMENTS 9 <](#)

[HTTPS://WWW.EDN.COM/OP-AMP-NOISE-BUT-WHAT-ABOUT-THE-FEEDBACK/#COMMENTS>](https://www.edn.com/op-amp-noise-but-what-about-the-feedback/#comments)



Advertisement

Last month we explored [noise of the non-inverting amplifier < http://www.edn.com/electronics-blogs/the-signal/4404375/op-amp-noise-the-non-inverting-amplifier>](#) but I dodged the issue of the feedback network's noise contribution. A reader, Jim, challenged me—he wanted more detail. So what about the noise from R1 and R2 in figure 1?

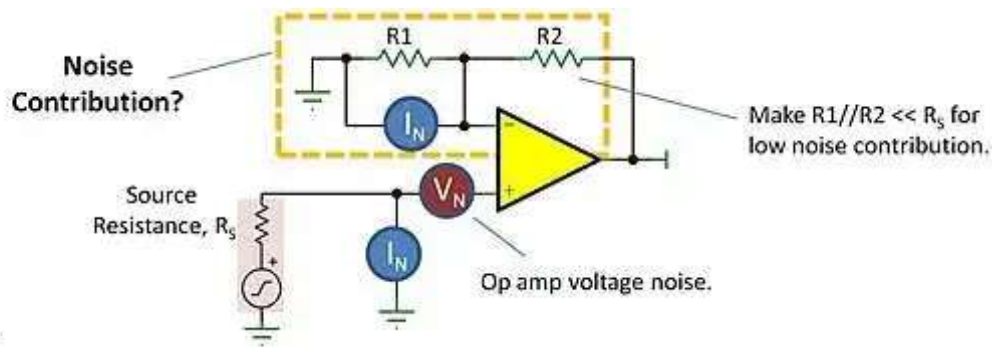


Figure 1.

The noise contribution at the inverting input is comprised of the thermal noise of the feedback resistors and op amp's current noise reacting with these components. The **output** contribution of these noise sources can be calculated using basic op amp assumptions:




Advertisement

- R1's thermal noise voltage is amplified to the output by the inverting gain of the circuit, $-R2/R1$.
- R2's thermal noise contributes directly to the output noise.
- The inverting input current noise flows through R2, resulting in an output noise contribution of $I_N \cdot R2$.

These noise sources are uncorrelated so they "add" by the root sum of the squares.

Advertisement

PARTNER CONTENT

 <p>Telink Semiconductor: Celebrating Two Billion Chips and Leading the Innovation</p>	 <p>Semihouse Electronics Components Balance Cost and Quality</p>	 <p>A Blueprint for a Connected Future in Semiconductor and Electronics</p>
--	---	--

But there's a more intuitive way to look at this. It's handy to refer the noise sources as if they all occur at the non-inverting input. Output noise contributions are divided by the non-inverting gain. This RTI (referred to input) approach makes it easy to compare noise sources and to the input signal. **The noise occurring at the inverting input relates to the parallel combination of R1 and R2.** When referred to the non-inverting input, the combined RTI thermal noise of R1 and R2 is equal to the

thermal noise of $R1//R2$. The current noise RTI contribution at the inverting input is equal to $I_N \cdot (R1//R2)$. **It's all about $R1//R2$.**

Noise contribution of $R1$ and $R2$ and inverting current noise:

$$\text{Output Noise}^2 = [V_{NR1} \cdot (R2/R1)]^2 + (V_{NR2})^2 + (I_N \cdot R2)^2 \quad (1)$$

Dividing by non-inverting gain to refer to input...

$$\text{RTI Noise}^2 = \underbrace{(V_{NR1//R2})^2}_{\text{Thermal noise of } R1//R2} + (I_N \cdot R1//R2)^2 \quad (2)$$

This result reveals an important factor for a low noise design. **Make $R1//R2$ S** and the noise contribution at the inverting input is negligible. If $R1//R2 = R_S$ then the feedback network contributes equal noise to that of the source resistance. That may be too much for some designs.

In high gains, it's easy to keep the parallel resistance low— $R1$ can be made much less than R_s and $R2$ is big. At moderate gains it gets more difficult. $G=2$ is the worst case when $R1$ and $R2$ are equal. If you want to make the parallel resistance 100Ω , for example, $R1$ and $R2$ need to be 200Ω .

The feedback network then imposes a 400Ω load on the op amp—too low in most circumstances. It gets easy again very close to $G=1$ when $R1$ is big and $R2$ small. This case is not common because you generally want significant [gain in the first low noise stage < http://e2e.ti.com/blogs-/b/thesignal/archive/2013/01/21/put-gain-up-front-waxing-philosophical.aspx>](http://e2e.ti.com/blogs-/b/thesignal/archive/2013/01/21/put-gain-up-front-waxing-philosophical.aspx).

Addressing a common concern—there is no noise inherent noise penalty in making $R2$ a high resistance. If higher gain is achieved by increasing $R2$ and decreasing $R1$, while maintaining a constant parallel resistance, noise performance remains constant.

You can download [an Excel file < http://e2e.ti.com/blogs-/b/thesignal/archive/2013/02/10/op-amp-noise-but-what-about-the-feedback.aspx>](http://e2e.ti.com/blogs-/b/thesignal/archive/2013/02/10/op-amp-noise-but-what-about-the-feedback.aspx) to calculate the noise of this commonly used input amplifier stage, including the op amp and source resistance noise. It shows the percentage contribution of each noise source and graphs the total noise over a range of source resistance. It also calculates *noise figure*, the noise (in dB) that the amplifier adds to thermal noise of the source. This is a handy measure of the noise performance of the amplifier. Tinker with it and you will quickly get a feel for the issues and trade-offs. [Download it here < http://e2e.ti.com/blogs-/b/thesignal/archive/2013/02/10/op-amp-noise-but-what-about-the-feedback.aspx>](http://e2e.ti.com/blogs-/b/thesignal/archive/2013/02/10/op-amp-noise-but-what-about-the-feedback.aspx).

Thanks for reading and your comments are welcome.

Bruce email: (Email for direct communications.)

Check out other interesting topics... [Table of Contents < http://www.ti.com/thesignal-topics>](http://www.ti.com/thesignal-topics) for all **The Signal** blogs

9 COMMENTS ON “OP AMP NOISE—BUT WHAT ABOUT THE FEEDB



ChristopherH

February 12, 2013

Thank you Bruce!

In the case of low gain, you can use a T-network in the feedback path to achieve both low-noi and high impedance load (c.f. “Op Amps For Everyone”, pg 422,

<http://www.ti.com/lit/an/slod006b/slod006b.pdf> <
<http://www.ti.com/lit/an/slod006b/slod006b.pdf>>.)

↪ [Log in to Reply.](#)



Guru of Grounding

February 12, 2013

Inserting a “T-network” in the feedback also increases gain. I understand it's usefulness in avc very high values of feedback R in high-gain circuits (to reduce capacitive parasitics and bias c induced offsets) but I don't understand how it impr

↪ [Log in to Reply.](#)



Oliver Sedlacek

February 12, 2013

I don't think that's right, a T network doesn't improve the ratio of load resistance (as seen by tl opamp output) to source resistance (as seen at the inverting input). As mentioned, the worst c is at a gain of two, but then that's a very low gain to

↪ [Log in to Reply.](#)



BradWood

February 12, 2013

Agree with Oliver and Bill here. The noise gain goes up and the loop gain goes down, making distortions and errors larger, including sensitivity to offset voltages. But yes, high-value resistc often quite a bit less than ideal, so for some appl

↪ [Log in to Reply.](#)



Sergio Franco

February 13, 2013

May I suggest using separate symbols for the inverting-input and non-inverting input noises, ϵ as INN and INP, or IN- and IN+. Using the same symbol may lead especially the beginner to erroneous simplifications such as $(R_s + R_1 // R_2)^2 \times IN^2$ instead of [

↳ [Log in to Reply.](#)



Bruce Trump

February 13, 2013

Thanks, Sergio. Yes, perhaps I should have used different variables for inverting and non-inve input current noise sources. I assume that the two are equal in magnitude and uncorrelated, ϵ assumption for virtually all common op amps, but certainl

↳ [Log in to Reply.](#)



tweet

February 14, 2013

Thermal noise isn't the only thing that can ruin the picnic. Will you be doing an article on 1/f n

↳ [Log in to Reply.](#)



Bruce Trump

February 15, 2013

Thanks, tweet, 1/f noise (also called flicker noise) would be an excellent topic. It's not importa all applications but it can be critical in slow, precision low-level measurements. Not sure I'll tal on next month but I'll put it on my short list

↳ [Log in to Reply.](#)



Sergio Franco

June 15, 2013

Ok, looks like now I am on camera too, with my own EDN blog (courtesy of Steve Taranovich). Here's more about op amp noise: <http://www.edn.com/electronics-blogs/analog-bytes/4416424/Op-amp-input-current-noise-> < [http://www.edn.com/electronics-blogs/analog-bytes/4416424/Op-amp-input-current-noise->](http://www.edn.com/electronics-blogs/analog-bytes/4416424/Op-amp-input-current-noise-)

↳ [Log in to Reply.](#)

LEAVE A REPLY

You must [Sign in](#) <

https://aspencoreb2cprod.b2clogin.com/aspencoreb2cprod.onmicrosoft.com/B2C_1_Aspencore_response_type=code&scope=openid%20offline_access&client_id=606ea8b3-c451-47e5-8db8-1aeb49207408&state=0d239414373025f8b72d7f6bb6071bd4&redirect_uri=https%3A%2F%2Fwww.connect-authorize> or [Register](#) <

https://aspencoreb2cprod.b2clogin.com/aspencoreb2cprod.onmicrosoft.com/B2C_1_Aspencore_response_type=code&scope=openid%20offline_access&client_id=606ea8b3-c451-47e5-8db8-

[1aeb49207408&state=db84403a218c8491cb96167f06d67979&redirect_uri=https%3A%2F%2Fwww.connect-authorize/](https://www.eetimes.com/1aeb49207408&state=db84403a218c8491cb96167f06d67979&redirect_uri=https%3A%2F%2Fwww.connect-authorize/) to post a comment.

[PREVIOUS POST < \[HTTPS://WWW.EDN.COM/CRYSTEK-SAMPLES-NEW-5-GHZ-C-RESONANT-OSCILLATOR/\]\(https://www.edn.com/crystek-samples-new-5-ghz-c-resonant-oscillator/\)>](https://www.edn.com/previous-post-https://www.edn.com/crystek-samples-new-5-ghz-c-resonant-oscillator/)

[NEXT POST < \[HTTPS://WWW.EDN.COM/DONT-STAND-ON-THE-CATS-WHI\]\(https://www.edn.com/dont-stand-on-the-cats-whi\)](https://www.edn.com/next-post-https://www.edn.com/dont-stand-on-the-cats-whi)

PARTNER CONTENT



[Telink Semiconductor: Celebrating Two Billion Chips and Leading the Charge in IoT Innovation <](https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/)

[https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/>](https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/)

11.06.2024



[Semihouse Electronics Components Balance Cost and Quality <](https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/)

[https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/>](https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/)

11.06.2024




[A Blueprint for a Connected Future in Semiconductor and Electronics <](https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/)

[https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/>](https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/)

≤ [connected-future-in-semiconductor-and-electronics/](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)>
[https://www.eetimes.com/a-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[blueprint-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[for-a-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[connected-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[future-in-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[semiconductor-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[and-](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)
[electronics/](https://www.eetimes.com/a-connected-future-in-semiconductor-and-electronics/)>
10.30.2024
.....

Advertisement

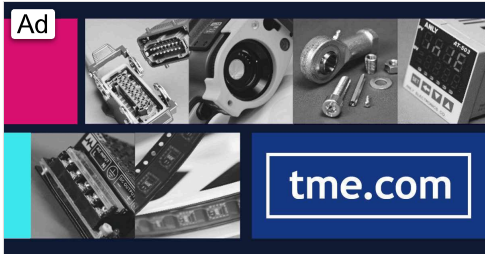

Check our offer

Shipping in 24 hrs, technical support, a trustworthy supplier, an official distributor.



Advertisement

Recent Posts

[Online tool programs smart sensors for AIoT < https://www.edn.com/online-tool-programs-smart-sensors-for-aiot/>](https://www.edn.com/online-tool-programs-smart-sensors-for-aiot/) / [Cortex-M85 MCUs empower cost-sensitive designs < https://www.edn.com/cortex-m85-mcus-empower-cost-sensitive-designs/>](https://www.edn.com/cortex-m85-mcus-empower-cost-sensitive-designs/) / [GaN flyback switcher handles 1700 V < https://www.edn.com/gan-flyback-switcher-handles-1700-v/>](https://www.edn.com/gan-flyback-switcher-handles-1700-v/) / [Data center power supply delivers 8.5 kW < https://www.edn.com/data-center-power-supply-delivers-8-5-kw/>](https://www.edn.com/data-center-power-supply-delivers-8-5-kw/) / [Sensor powers AI detection in slim devices < https://www.edn.com/sensor-powers-ai-detection-in-slim-devices/>](https://www.edn.com/sensor-powers-ai-detection-in-slim-devices/)

Archives

Select Month ▼

Categories

Select Category ▼

PODCAST

 **18:57**

**Get Powered by
Renesas: Leading
Solutions in Automotive
and Industrial
Applications**

Ivo Marocco, Vice President at
Renesas, discusses the

LISTEN



VIEW ALL
EPISODES

Search ...

SEARCH

Recent Comments

WSWoodward ON [Negative time-constant and PWM program a versatile ADC front end <
https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32233>](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <
https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/)

[32232>](#)

WSWoodward ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32231)

[32231>](#)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32230)

[32230>](#)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32229)

[32229>](#)

Advertisement