



## Other Parts Discussed in Post: [LMV844](#)

President Ronald Reagan frequently said “trust but verify” when discussing U.S. relations with the Soviet Union. Some say it comes from a Russian proverb, “doveryai no proveryai.”

Trust but verify is exactly what you should do when using SPICE [operational amplifier](#) (op amp) macromodels. For op amp stability analysis in the AC domain, you need to verify that both  $A_{ol}$  (open loop gain) and  $Z_o$  (open-loop output impedance), two key things for op amp stability analysis, are correct for the op amp macromodel.

Figure 1 shows an AC model for an op amp with  $A_{ol}$  and  $Z_o$ . Since most SPICE op amp macromodels end up being modeled correctly for  $A_{ol}$ , I'll focus on verifying  $Z_o$ , which is often not modeled correctly. Note that there is not industry consistency in terminology for open loop output impedance. Both  $R_o$  and  $Z_o$  are used.


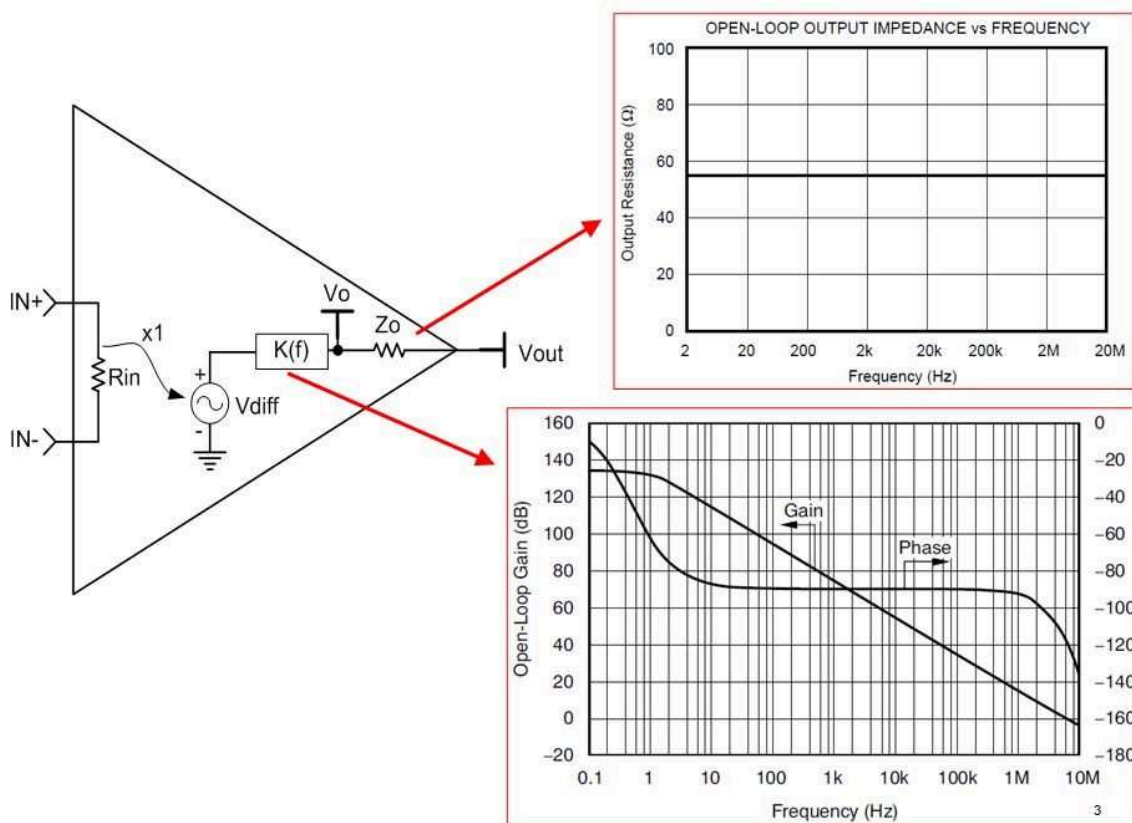


Figure 1: Op amp AC model

- Figure 2 illustrates the important differences between  $Z_O$  and  $Z_{OUT}$ .  $Z_O$  is the open-loop output impedance of an op amp.  $Z_{OUT}$  is defined as the closed-loop output impedance of an op amp.

$Z_O$  and  $Z_{OUT}$  are related.  $Z_{OUT}$  is  $Z_O$  reduced by loop gain. Figure 2 shows how the relationship between  $Z_O$  and  $Z_{OUT}$  is derived.

This simplified op amp model focuses solely on the basic DC characteristics of an op amp. A high input resistance (100mΩ to GΩ),  $R_{DIFF}$  develops an error voltage across it,  $V_E$ , due to the voltage differences between -IN and +IN. The error voltage,  $V_E$ , is amplified by the open-loop gain factor  $A_{OL}$  and becomes  $V_O$ . In series with  $V_O$  to the output,  $V_{OUT}$ , is  $Z_O$ , the open-loop output impedance. Using standard circuit analysis, the resulting relationship between  $Z_O$  and  $Z_{OUT}$  is shown.

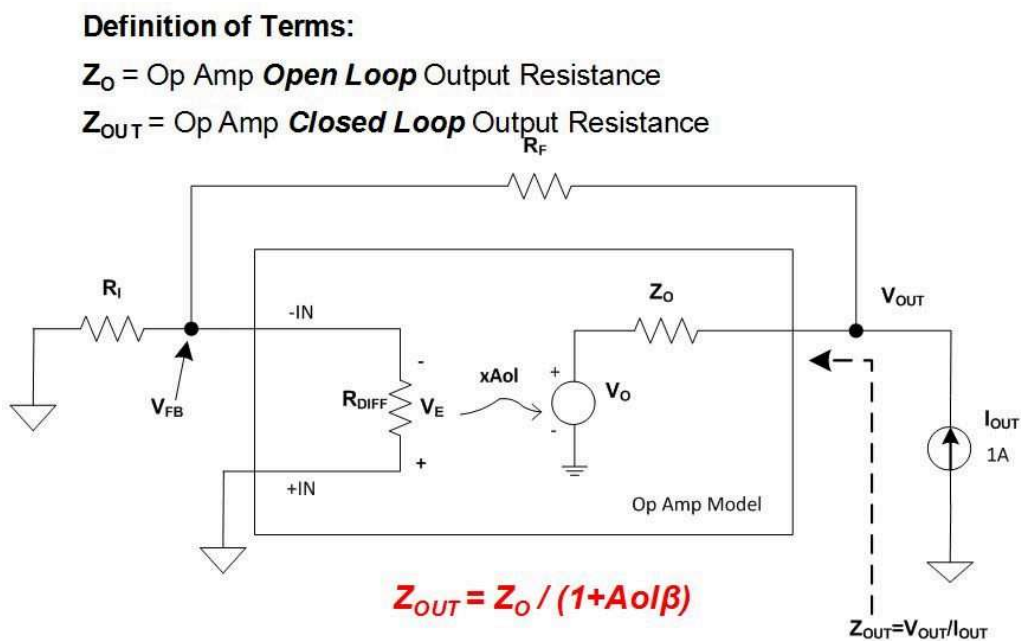

From: Frederiksen, Thomas M. Intuitive Operational Amplifiers. McGraw-Hill Book Company. New York. Revised Edition. 1988.

Figure 2:  $Z_O$  vs.  $Z_{OUT}$

Figure 3 is the SPICE circuit for testing the  $Z_{OUT}$  of an op amp. An AC current source,  $I_{OUT}$ , with the DC portion set to zero is injected into the op amp output. You do not want any DC current injected into the op amp output, since  $Z_{OUT}$  becomes lower with current in the output. The worst-case stability problems almost always occur with the highest  $Z_{OUT}$ .

For this test, I set the op amp closed-loop gain to 1 to check against the Gain = 1x test data in the data sheet. SPICE performed a DC analysis before it ran the AC analysis. You must confirm that the amplifier is not in output saturation for the DC analysis or else the AC analysis will not be meaningful.

- DC analysis showed the output of the [LMV844](#) to be  $500\mu\text{V}$  for a gain = 1, which reflects an expected input offset voltage for this part. If  $A_{ol}$  in the op amp macromodel matches the data sheet, then you know  $Z_o$  is correct based on Figure 2.  $V_{OUT}$  will become  $Z_{OUT}$  since the AC analysis will report all voltage probes relative to  $I_{OUT}$ , the excitation. The AC analysis will compute  $V_{OUT} = I_{OUT} * Z_{OUT}$  and report this as a gain of  $V_{OUT}/I_{OUT} = Z_{OUT}$ .

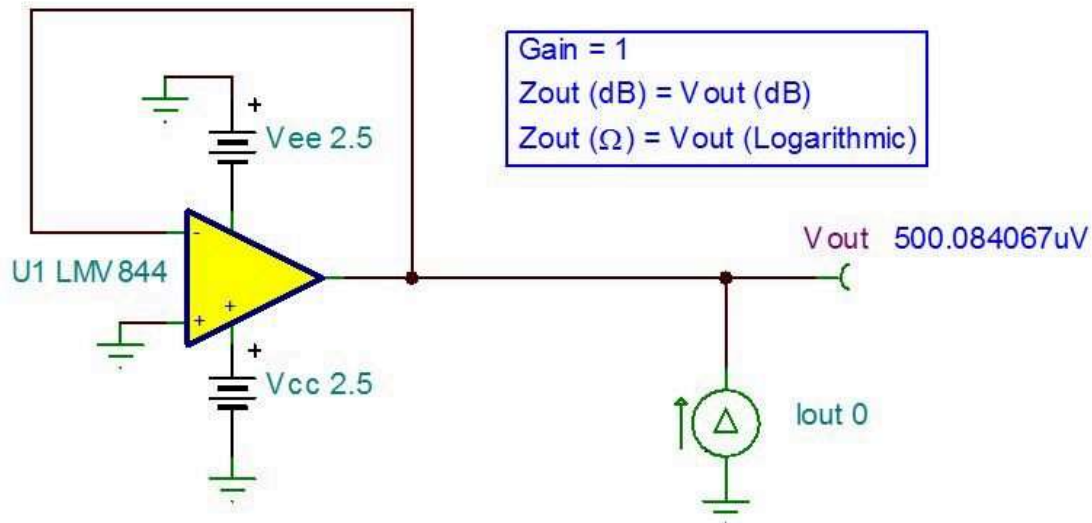


Figure 3:  $Z_{OUT}$  SPICE measure

My SPICE test result of the [LMV844](#) macromodel indicates that  $Z_{OUT}$  does not match the data sheet for a gain = 1. Figure 4 shows two slopes (+20dB/dec and +40dB/dec) on the data sheet  $Z_{OUT}$  for a gain = 1 and only one slope (+20dB/dec) for the macromodel  $Z_{OUT}$ . If you see this in your application, you will need to contact the op amp manufacturer to get a SPICE op amp macromodel with the correct  $Z_{OUT}$  for stability analysis. Like  $Z_o$ , there is not industry consistency in terminology for closed loop output impedance. Both  $R_{out}$  and  $Z_{out}$  are used.

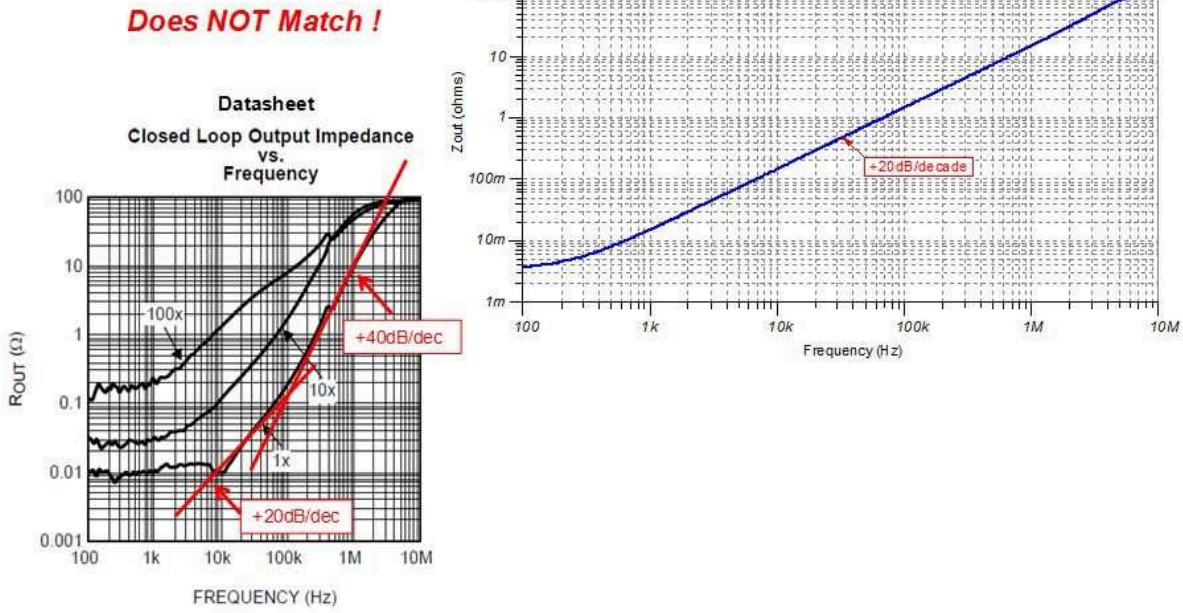


Figure 4: LMV844 macro vs. data sheet

I will use the test circuit in Figure 5 to measure  $Z_O$ , open-loop output impedance. SPICE will perform a DC analysis before it runs the AC analysis. You must confirm that the amplifier is not in output saturation for the DC analysis or else the AC analysis will not be meaningful. In the circuit of Figure 5, L1 will act as a short at DC but an open for any frequency of interest. Conversely, C1 will act as an open at DC and a short for any frequency of interest.

DC analysis shows the output of the [OPA376](#) to be at  $-25.38\mu\text{V}$  for a gain = 1, which is an expected input offset voltage for this part. Just like the  $Z_{out}$  test, use an AC current source, with DC component of it set to zero, to back-drive the output of the op amp.  $V_{OUT}$  will become  $Z_O$  since the AC analysis will report all voltage probes relative to  $I_{OUT}$ , the excitation. The AC analysis will compute  $V_{OUT} = I_{OUT} * Z_O$  and report this as a gain of  $V_{OUT} / I_{OUT} = Z_O$ .


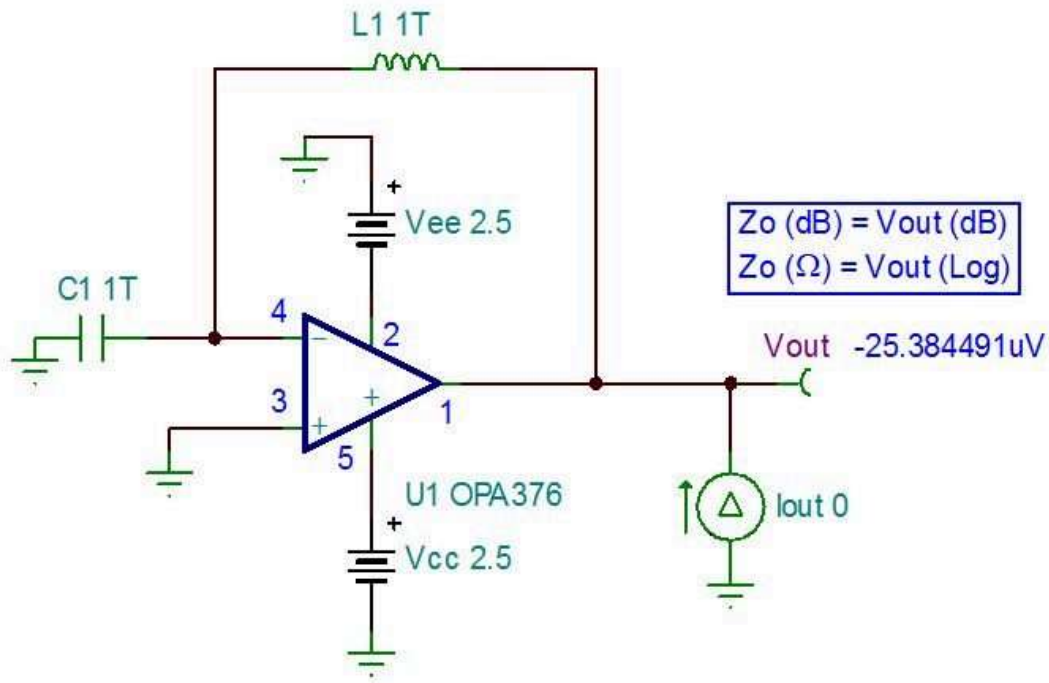
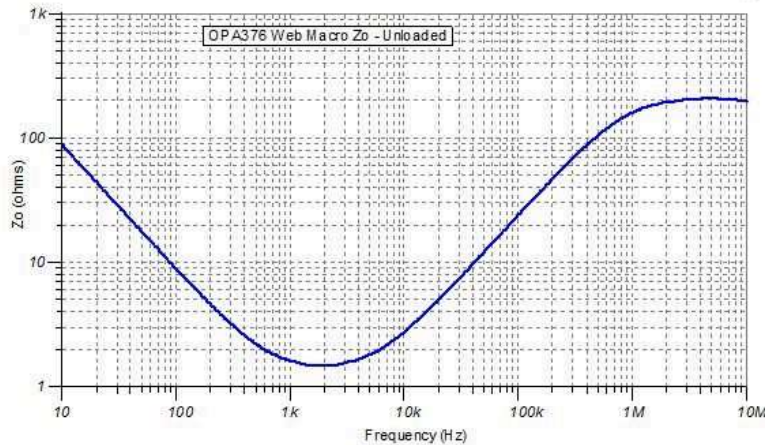


Figure 5:  $Z_0$  SPICE measure

Figure 6 confirms that the SPICE op amp macromodel does indeed match the data sheet. There are two curves for  $Z_0$  in the [OPA376](#) data sheet. Since I am interested in the unloaded  $Z_0$ , output with no load current, I will compare the SPICE simulation against the  $400\mu\text{A}$  load current  $R_o$  curve in the data sheet. Remember that  $Z_0$  decreases with current in the output stage. You need to know the largest  $Z_0$ , which will almost always cause the worst stability issues.

**Figure 6:**  
**OPA376  $Z_o$  Macro vs Datasheet**

**Does Match !**

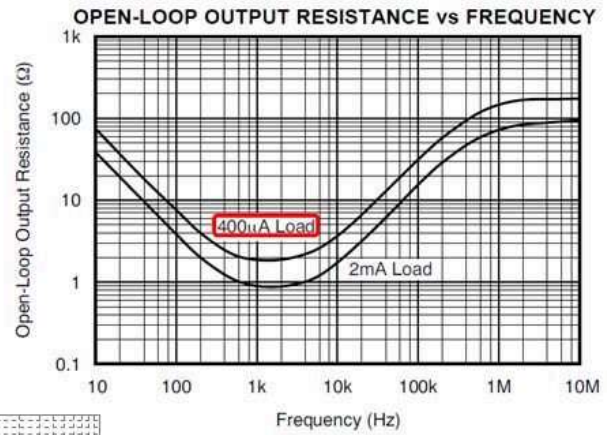

**Figure 6:** [OPA376](#) macro vs. datasheet

You now have a quick and easy way to trust but verify SPICE op amp macromodels for the proper  $Z_O$  or  $Z_{OUT}$ . The correct  $Z_O$  or  $Z_{OUT}$  will allow you to simulate, predict and build stable op amp circuits for your end applications. For more detailed information on op amp stability, check out the resources below.

### Additional resources

- Learn more about [op amp stability](#) on the TI E2E™ forum under Precision Amplifiers, Precision Amplifier Wiki.
- Check out [TI Precision Labs](#) and learn all about precision op amps.
- Take a look at our free [TI TINA-TI™ SPICE](#) simulator.
- Learn about TI's entire portfolio of [amplifier ICs](#) and find more technical resources.



0 comments 0 members are here