



Last week we looked at two very common reasons for oscillations or instability in op amp circuits. The ultimate cause of both was delay or phase shift in the feedback path. [Review it here](#). I confess that I had intended to discuss cures for both circuits this week. But to keep these blogs bite-size, I think it's best to cover just one this week. (I must control my enthusiasm!)

A simple non-inverting amplifier can be unstable or have excessive overshoot and ringing if the phase shift or delay created by the op amp's input capacitance (plus some stray capacitance) reacting with the feedback network resistance is too great. You may be able to make some improvement by reducing stray capacitance at this node, minimizing the circuit board trace area of this connection. For a given op amp, input capacitance (differential + common-mode capacitance) is a fixed value—you're stuck with it. You can, however, reduce the resistances of the feedback network proportionally to keep the gain the same. This moves the pole created by this capacitance to a higher frequency and decreases the delay time constant. Reducing the resistances to 5kΩ and 10kΩ in this example makes a big improvement but still produces approximately 10% overshoot with ringing. It also creates additional load on the op amp, so you can't take this solution too far. The sum of the two resistors is a load on the op amp and you would not want to be too low.

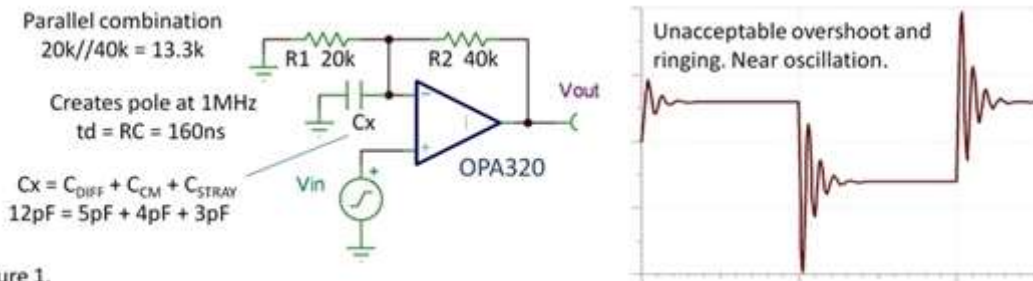


Figure 1.

The better solution is likely to be a capacitor, C_c , connected in parallel with R_2 (figure2). When $R_1 \cdot C_x = R_2 \cdot C_c$, the voltage divider is compensated and the impedance ratio is constant for all frequencies. There will be no phase shift or delay in the feedback network. :)


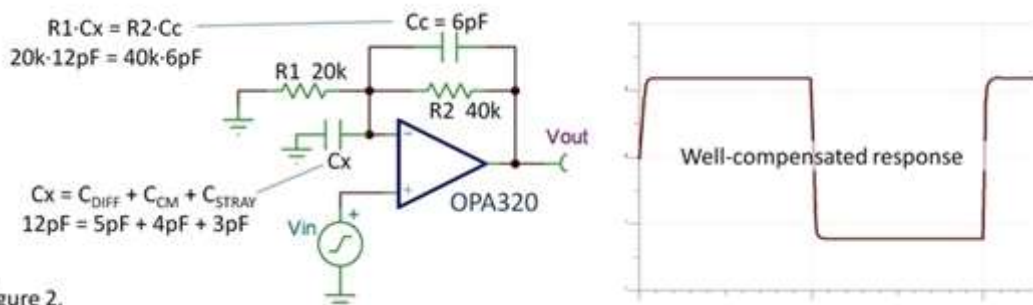


Figure 2.

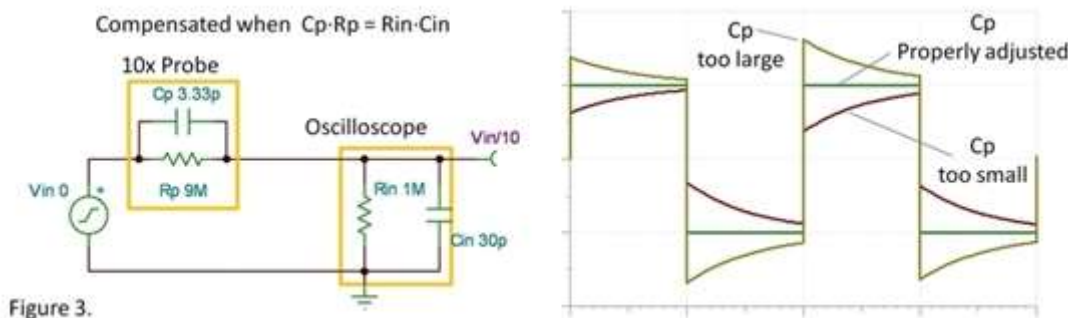- You can liken the feedback network to the compensated attenuator in a 10x oscilloscope probe (figure 3). It's the same concept. A variable capacitor in the probe allows adjustment to make the two time constants equal. Note that the response of this scope probe does not ever appear unstable even when improperly adjusted. Why? Because it is not inside a feedback loop.



Just as one of the capacitors is made adjustable in a scope probe to fine-tune the compensation, you may also need to adjust the value of C_c in figure 2. The capacitance C_x may not be precisely known due to the uncertain effects of stray capacitance. Furthermore, you may want to tune the response of the circuit to meet your requirements with a little bit of overshoot for improved speed and bandwidth.

Last week I cited another common case of instability, an op amp with capacitive load. Again, this situation produces phase shift in the loop (delayed feedback) that is the root of the problem. This one is tricky because open-loop output resistance is internal to the op amp. We can't connect a compensating capacitor across this resistor. In fact, it's not really a resistor at all; it's an *equivalent* output resistance of the op amp circuitry. So, next week, we'll look at the capacitive load problem. I'll also provide a link to a presentation with more detail on handling stability issues, so stay tuned.

Consider your last oscillating op amp. Can the problem be explained with delayed feedback?

Comments welcome and thanks for reading,

Bruce

6 comments 0 members are here



BigDogGuru *over 12 years ago*

"The Signal" is a fantastic blog Bruce and each post a true gem. Keep them coming.

Have you considered publishing your series of posts in PDF format for reference off site?

BigDog



Bruce Trump *over 12 years ago*

Thanks, BigDogGuru (I've never addressed anyone that way). I will consider your suggestion. The mechanics would not be difficult as preparation is in MS-Word with the figures dropped in. I would need to

go back a capture some minor tweaks. I always seem to find something to change when I see it in the blog format.

Regards, Bruce.



[ramin anushiravani](#) *over 12 years ago*

Thanks a lot for posting this awesome information. Quick question, can I apply my microphone to Vin with a lowpass filter on the side to the positive input? The reason I'm asking is because I tried applying to my preamp circuit (I was getting very high oscillation from OPA2134) and now I'm not getting any signal out and I still have the oscillation :(



[Bruce Trump](#) *over 12 years ago*

Ramin-- I see that Collin is assisting you on the forum so I'll let him respond. I think it's best to keep all the advice regarding your circuit in your forum thread. Thanks for reading. Bruce



[Philip Petch](#) *over 12 years ago*

The most interesting oscillating opamp problem I have had involved a 1GHz+ bandwidth current feedback with limited power supply rejection. Four such amplifiers in series formed a bandpass filter up to 160MHz with 120 times gain into a 50 ohm load. In this case the feedback path was via the power supplies and was cured with heavy filtering of the supplies to each amplifier.

Keep up the good work! PeppyKiwi

▼ [View More](#)