

# designideas

READERS SOLVE DESIGN PROBLEMS

## Comparator detects position of peaks and valleys in a waveform

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

The recent advent of Analog Devices' ([www.analog.com](http://www.analog.com)) ADCMP60x family of comparators has filled a gap between the less-than-1-nsec-response comparators consuming 100 to 200 mW and those exhibiting approximately 1- $\mu$ sec response, requiring about one-thousandth that power. The ADCMP60x comparators exhibit a low value of the product of propagation-delay-by-supply-current drain; possess rail-to-rail input and output operation; and offer a variety of options for hysteresis, latch-mode operation, and shutdown mode. Some of them

also have inherent level-translating capability. Moreover, the ratio of propagation delays for the positive and negative transitions at the output is close to the ideal value of 1 within 8% tolerance for the ADCMP600, ADCMP601, ADCMP602, and ADCMP603 and within a 6.7% tolerance for the ADCMP608 and ADCMP609 members of the family (Reference 1).

This ratio is important in applications in which both positive- and negative-output-level transitions are equally significant. Figure 1 shows one such circuit. Voltage-level transitions

### DIs Inside

104 Precision integrator sparks current-ratio-to-frequency converter


108 Accurate USB 2.0 temperature sensor needs only a handful of parts

110 Integrator enables simple ohmmeter with gigohm range

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to [edndesignideas@reedbusiness.com](mailto:edndesignideas@reedbusiness.com).

at the output of the detector indicate changing of the sign of the first derivative of the input signal; in other words, the circuit detects time positions of peaks and valleys in the input-voltage waveform. The detector circuit uses an ADCMP601 for IC<sub>2</sub>, and IC<sub>1</sub> is an Analog Devices AD8007 current-feedback amplifier. IC<sub>1</sub> connects as a voltage follower with an antiparallel combination of Schottky-barrier switching diodes, D<sub>1</sub> and D<sub>2</sub>, between the output and the inverting input of the amplifier. Comparator IC<sub>2</sub>'s inputs connect to the source of the input voltage and to the output of the current-feedback amplifier. This configuration enhances the voltage difference of V<sub>IN</sub> - V<sub>A</sub> between inputs of the comparator. It performs this enhancement in a steplike manner at the instant, or region, at which the sign of slope of the input signal changes. This voltage difference is a measure of the double-forward voltage of diodes D<sub>1</sub> and D<sub>2</sub> at their forward current, which you derive from V<sub>IN</sub>/R<sub>F</sub>.

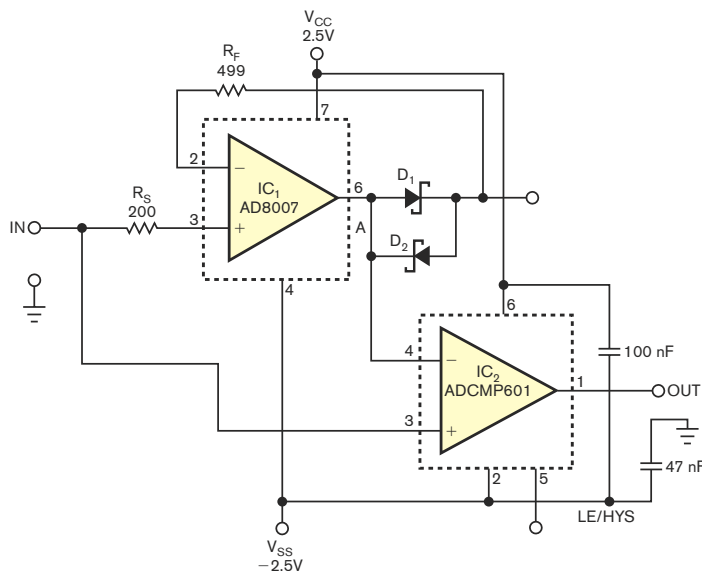You use a current-feedback amplifier as IC<sub>1</sub> because a dynamic current flows into its inverting input even when you




NOTE: D<sub>1</sub> AND D<sub>2</sub> ARE HSMS-282Ls OR HSMS-282Cs.

Figure 1 Comparator IC<sub>2</sub> produces an output that switches state at the positive and the negative peaks of the input-voltage waveform.

connect it as a voltage follower. The values of the  $R_S$  and  $R_F$  resistors are those that **Reference 2** recommends for a gain of 1. You needn't worry about instability due to the presence of anti-parallel diodes in the feedback path of the current-feedback amplifier. These diodes increase the value of feedback resistance to more than  $499\Omega$ . Whenever the input voltage is only approximately 0V, the frequency-gain response of  $IC_1$  for an  $R_F$  value greater than  $499\Omega$  remains flat.

An analysis of the response of the voltage follower in **Figure 1** to a harmonic input voltage uses  $\omega/\omega_T$  and  $\omega=2\pi f$ , where  $f$  is the input-voltage frequency and  $\omega_T$  is the radial transition frequency of the amplifier. At the radial-transition frequency, the ratio of  $Z_M$  (the magnitude of the amplifier's transimpedance) to  $R_F$  drops to one. This simplification leads to an **equation** for the delay,  $t_D$ , in **Figure 2**:

$$\Delta\phi = 2\sqrt{\frac{V_F}{V_m} \times \frac{R_F}{r_{m0}}}$$

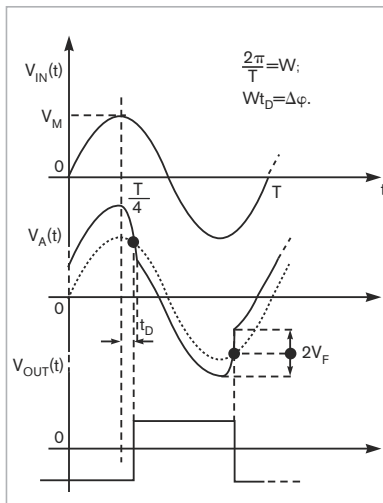

**Figure 2** The output of comparator  $IC_2$  switches a slight time delay,  $t_D$ , after the positive and the negative peaks of the input voltage.

where  $V_F$  is the forward voltage of diode  $D_1$ ,  $V_m$  is the amplitude of input voltage,  $R_{m0}$  is the dc transresistance of the current-feedback amplifier, and

$\Delta\phi$  is the electrical-error angle in radians. The period of input harmonic voltage,  $T$  in **Figure 2**, represents  $2\pi$  radians. The final error of the detector is  $\Delta\phi$ , which decreases by a factor of  $\sqrt{2}$ . This reduction occurs because the necessary operating overdrive over the midpoint of the steplike transition in the  $V_A(t)$  voltage that the comparator requires is more than an order of magnitude less than the value of  $V_F$ . **EDN**

## REFERENCES

- 1 "Rail-to-Rail, Very Fast, 2.5V to 5.5V, Single-Supply TTL/CMOS Comparators," ADCMP600/ADCMP601/ADCMP602 Preliminary Data Sheet, Analog Devices, March 2006, [www.analog.com/UploadedFiles/Data\\_Sheets/378991928ADCMP600\\_1\\_2\\_prra.pdf](http://www.analog.com/UploadedFiles/Data_Sheets/378991928ADCMP600_1_2_prra.pdf).
- 2 "Ultralow Distortion High Speed Amplifiers," AD8007/8008 Data Sheet, Analog Devices, 2003, [www.analog.com/UploadedFiles/Data\\_Sheets/AD8007\\_8008.pdf](http://www.analog.com/UploadedFiles/Data_Sheets/AD8007_8008.pdf).