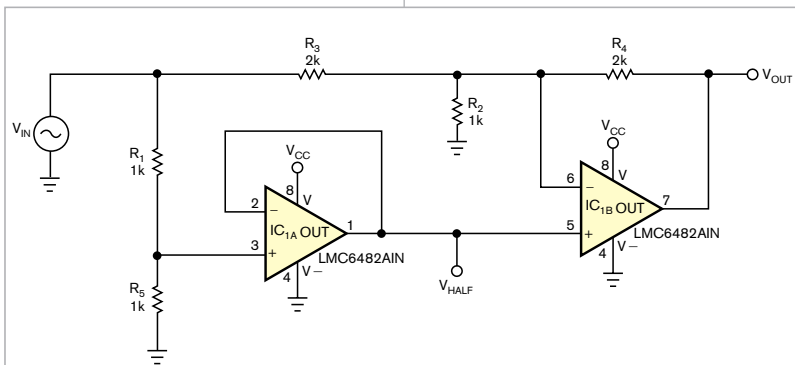


# Precision full-wave signal rectifier needs no diodes


José M Blanes and José A Carrasco,  
University Miguel Hernández, Elche, Spain

Rectifier circuits based on semiconductor diodes typically handle voltage levels that greatly exceed the diodes' forward-voltage drops,

which generally don't affect the accuracy of the rectification process. However, the rectified signal's accuracy suffers when the diode's voltage drop ex-



**Figure 1** This precision full-wave-rectifier circuit uses two op amps and no diodes. When altering the basic design, note that resistors  $R_3$  and  $R_4$  are both twice the value of  $R_2$  and that  $R_1$  and  $R_5$  are equal.

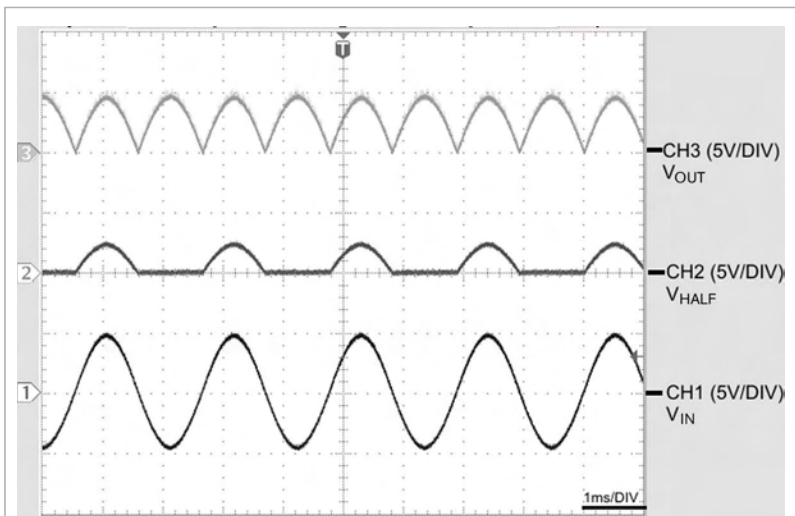

**Figure 2** From bottom to top, the waveforms show  $V_{IN}$  (CH1),  $V_{HALF}$  (CH2), and  $V_{OUT}$  (CH3).

## DIs Inside

**82** 1-Hz to 100-MHz VFC features  
160-dB dynamic range

**86** Cascode MOSFET increases  
boost regulator's input- and  
output-voltage ranges

ceeds the applied voltage. Precision rectifier circuits combine diodes and operational amplifiers to eliminate the effects of diode voltage drops and enable high-accuracy, small-signal rectification. By taking advantage of modern operational amplifiers that can handle rail-to-rail inputs and outputs, the circuit in **Figure 1** dispenses with diodes altogether, provides full-wave rectification, and operates from a single power supply.

The circuit operates as follows: If  $V_{IN} > 0V$ , then  $IC_{1A}$ 's output,  $V_{HALF}$ , equals  $V_{IN}/2$ , and  $IC_{1B}$  operates as a subtracter, delivering an output voltage,  $V_{OUT}$ , equals  $V_{IN}$ . In effect, the circuit operates as a unity-gain follower. If  $V_{IN} < 0V$ , then  $V_{HALF} = 0V$ , and the circuit behaves as a unity-gain inverter and delivers an output of  $V_{OUT} = -V_{IN}$ . **Figure 2** shows the circuit's input signal at  $V_{IN}$ ; its intermediate voltage,  $V_{HALF}$ ; and its output voltage,  $V_{OUT}$ .

The circuit uses a single National Semiconductor LMC6482 chip and operates in the linear regions of both operational amplifiers. Suggested applications include low-cost rectification for automatic gain control, signal demodulation, and process instrumentation. The circuit relies on only one device-dependent property: The amplifiers must not introduce phase inversion when the input voltage exceeds the negative power supply; the LMC6482 meets this requirement. **EDN**