

Originally published in the September 4, 1986, issue of EDN

AGC circuit uses an analog multiplier

Steve Lubs, Department of Defense, Washington, DC

In the AGC circuit of Fig 1, a 4-quadrant analog multiplier (IC₁), an amplifier stage (IC₂), an active, full-wave rectifier (D₁, D₂, R₄-R₇, and IC₃), and an integrator (IC₄) accomplish automatic gain control of V_{IN}'s amplitude variations in the audio-frequency range.

The multiplier's output is $-V_{IN} V_Y / 10$, where V_Y is a negative voltage generated by the integrator IC₄. Together, the integrator and the rectifier extract the dc component (V_Y) of V_{OUT} for use as a feedback signal to the multiplier. The integrator sums signal current from the rectifier and control current from

potentiometer R₉, which lets you adjust V_{OUT}'s signal level.


Circuit analysis yields the frequency-response equation

$$V_{OUT} = \frac{K_1 A V_C}{10 R C_3} \left(\frac{1}{s + \frac{10A}{RC_3}} \right),$$

or, in the time domain,

$$V_{OUT} = \left(\frac{K_1 A V_C}{10 R C_3} \right) \exp \left(- \frac{10 A t}{R C_3} \right).$$

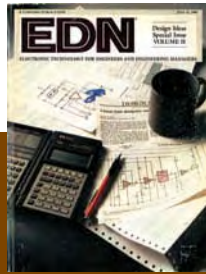In both equations, K₁ is the gain of amplifier IC₂, A is the peak amplitude of V_{IN}, and R is the resistance between



WANT TO SEE MORE OF THE CLASSICS?

Revisit 50 of the best Design Ideas from the Golden Age of electrical engineering.

<http://bit.ly/DesignIdeasClassics>

the integrator input and the rectifier output. (For this circuit, R equals R₆ in parallel with R₇.)

This AGC circuit is suitable for controlling the long-term variations of amplitude within a limited range. It doesn't respond uniformly over a wide dynamic range, however, because the time response is inversely proportional to input-signal amplitude. **EDN**

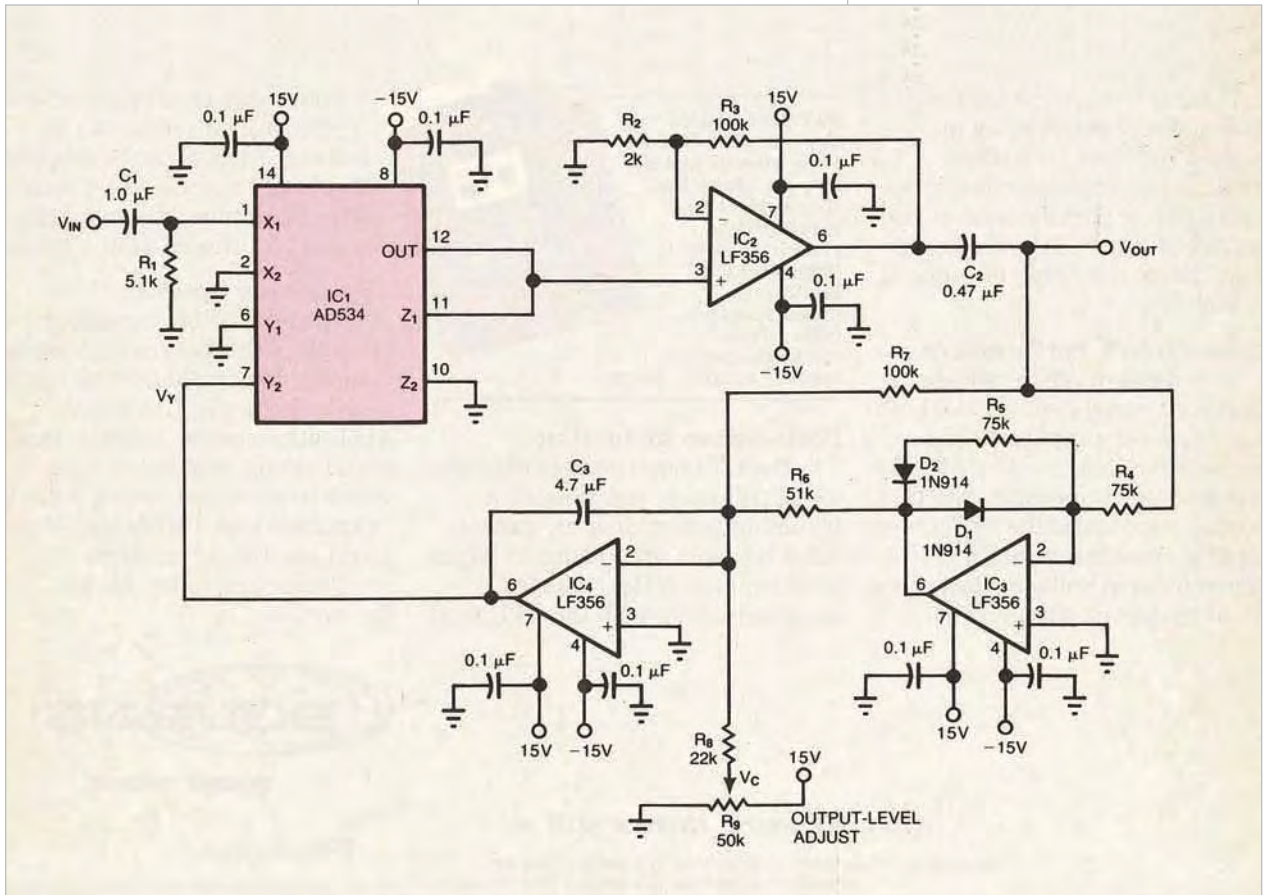


Figure 1 Analog multiplier IC₁ combines V_{IN} with a feedback signal V_Y to achieve automatic gain control.