

AGC amplifier features 60-dB dynamic range

Julius Foit, Department of Microelectronics, CTU Prague, Czech Republic

When processing signals from analog sensors, you frequently encounter wide variations in attenuation among communication channels or sensors. Or, you face situations in which several identical sensors within a supervised system return signals of roughly similar spectral composition and dynamic range but with considerably different maximum amplitudes. Sometimes, it's possible to predict these and other variations and adjust the gain of preprocessing amplifiers. More frequently, you encounter unpredictable signals and thus lose data associated with nonrepeatable events. In these circumstances, an adaptive preamplifier with AGC (automatic gain control) can prevent measurement-channel saturation and data loss.

AGC preprocessing suppresses the absolute amplitude of a sensed signal while preserving the best possible resolution of individual spectral components' relative amplitudes. The circuit in this Design Idea offers one relatively simple and efficient approach to per-channel AGC. The circuit uses a method of direct low-level signal control using a short-circuited bipolar transistor. In Figure 1, a variable voltage divider comprising a fixed resistance, R_1 , and a variable resistance controls the signal's ac amplitude. The variable resistance comprises the differential resistance of a bipolar transistor, Q_1 , short-circuited

from base to collector. To vary Q_1 's resistance, you force direct current into the shorted transistor from a current source comprising voltage source V_{REG} and a high-value resistor, R_2 . To prevent R_2 from affecting the circuit's ac-voltage-transfer characteristic, R_2 's resistance must greatly exceed R_1 's.

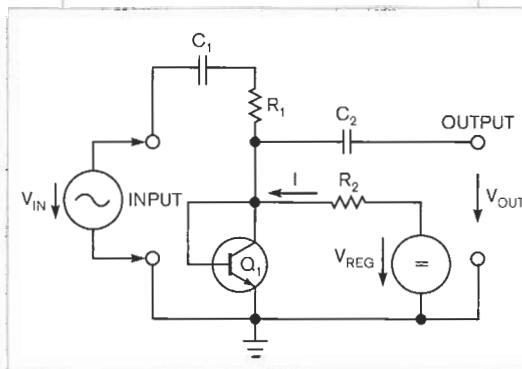


Figure 1 A short-circuited bipolar transistor forms one element of a basic attenuator circuit.

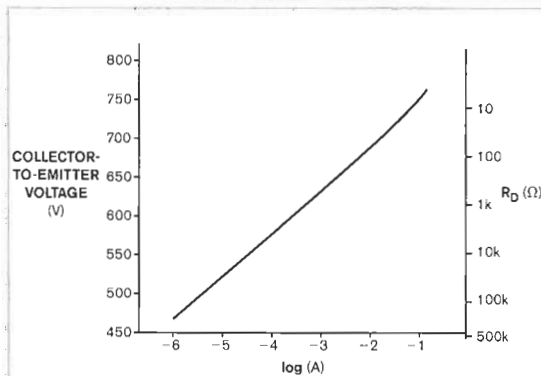


Figure 2 A VI characteristic shows the corresponding differential-resistance graph for a short-circuited BC337-16 transistor. (Note: The -16 denotes a sorted h_{FE} range of $100 < h_{FE} < 250$.)

DI Inside

94 Precision active load operates as low as 2V.

96 Squeeze extra outputs from a pin-limited microcontroller.

For all reasonable values of positive current I —generally, less than the transistor's maximum rated emitter current (I_E)—transistor Q_1 's collector-to-emitter

saturation voltage is less than its base-emitter threshold voltage, and the transistor operates in the active state. The shorted transistor's VI (voltage-versus-current) characteristic curve strongly resembles that of a PN diode and follows Shockley's Equation except for slightly higher dc-voltage values. That is, the device's voltage variation is proportional to the logarithm of the dc-current variation.

Therefore, the shorted transistor's differential resistance at every dc operating point along the VI curve is inversely proportional to the passing dc current; in other words, the device's differential conductance is directly proportional to the current. Because, in its active state, a common-emitter-connected bipolar transistor's current-amplification factor is typically 100 or more, the differential resistance accurately follows this rule over a broad range of currents.

Thus, varying V_{REG} in Figure 1 varies the current, I , and controls the R_1 - Q_1 voltage-division ratio. Coupling capacitors C_1 and C_2 separate the

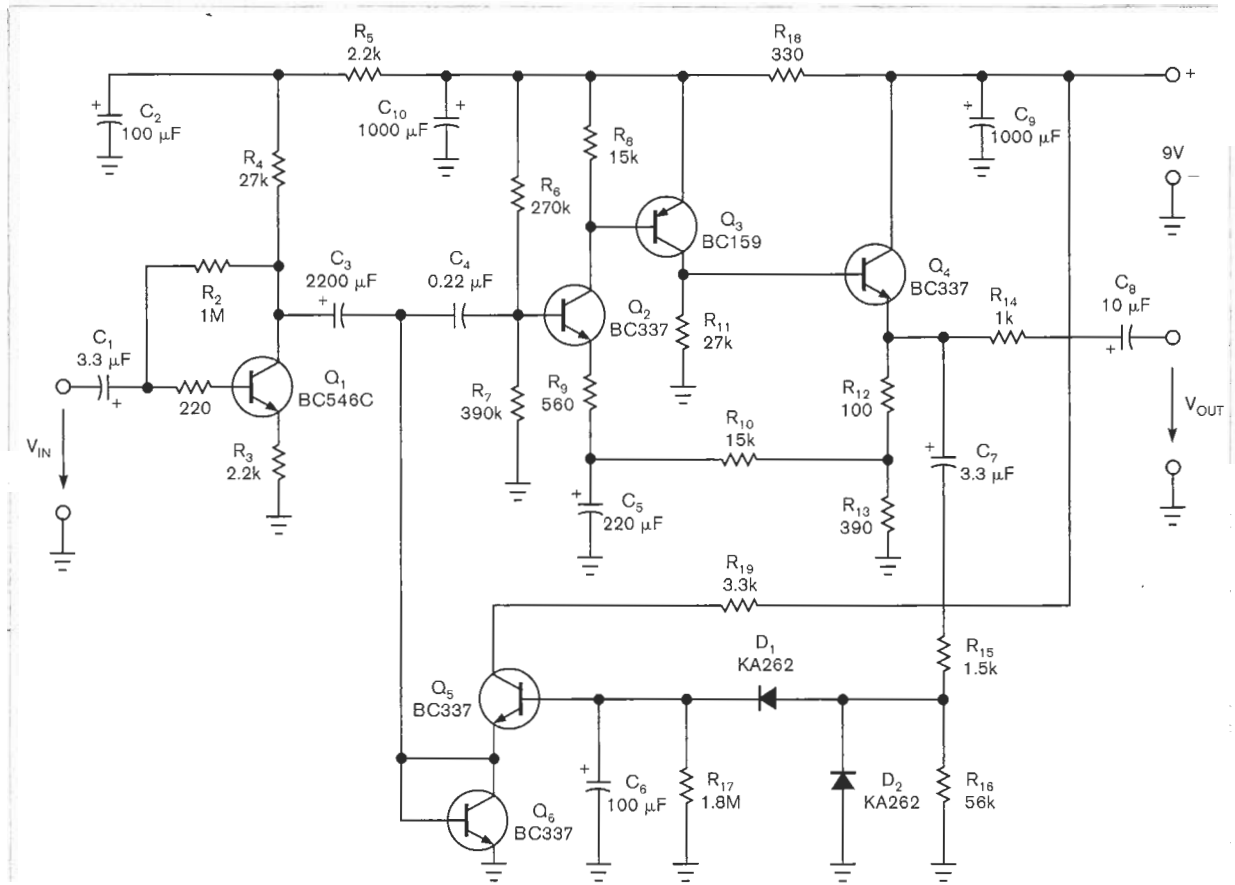


Figure 3 You can assemble this AGC circuit entirely from discrete components.

circuit's attenuator from the input-signal source and output load. **Figure 2** illustrates a typical small-signal bipolar transistor's short-circuited VI characteristic, showing that you can control differential resistance over at least five decades of range—that is, more than 100 dB.

In a practical circuit, the finite values of R_1 and R_2 limit the control range. For proper operation and to keep the signal's THD (total-harmonic-distortion) factor, k , below 5%, the output-voltage amplitude, V_{OUT} , should be just a few millivolts. Even with these limitations, this attenuator circuit appears to offer one of the best and simplest AGC circuits.

Figure 3 shows the completed circuit design. The input signal, V_{IN} , drives buffer stage Q_1 , whose unbypassed emitter resistor, R_3 , serves four purposes.

First, it increases Q_1 's differential output resistance to the approximate value shown in **Equation 1**:

$$R_{DI} \approx \frac{h_{11E} + h_{21E}R_3}{h_{11E}h_{22E}} \quad (1)$$

The increase in the circuit's differential output resistance is so large that the value of R_3 , 27 k Ω , almost exclusively determines the overall output resistance. Second, leaving R_3 unbypassed reduces Q_1 's voltage gain to:

$$A_{IC1} = \frac{(h_{22E}R_3 - h_{21E})R_4}{(R_3 + R_4)D_{hE} + [h_{21E} + 1 - h_{12E} + (R_3 + R_4)]R_3 + h_{11E}} \approx -R_4/R_3 \quad (2)$$

This equation simplifies to $A_{IC1} \approx R_4/R_3$. (Note that D_{hE} denotes the

determinant $(h_{11E} \times h_{32E} - h_{12E} \times h_{21E})$, which this Design Idea includes for theoretical accuracy. However, you can neglect the numerical value of D_{hE} for modern silicon transistors without significantly affecting the calculation's accuracy.) Third, as **Equation 2** shows, leaving R_3 unbypassed helps linearize the response of Q_1 's collector current-to-voltage drive. Fourth, Q_1 's differential base input resistance rises to: $R_{jBASE} = h_{11E} + h_{21E} \times R_3$, which is larger and less dependent on Q_1 's instantaneous operating point than h_{11E} alone.

In **Figure 3**, resistor R_4 forms the variable attenuator's fixed resistance, analogous to the upper resistor, R_1 , in **Figure 1**, and Q_6 forms the attenuator's variable-resistance element. Transistor Q_5 supplies Q_6 's collector-drive current, and Q_3 's common-emitter configura-

(continued on pg 92)

tion draws little base current. This approach enables use of a high value for AGC-release time-determining resistor R_{17} , thus permitting a long AGC-release time. Resistor R_{19} limits the maximum dc control current through Q_5 and Q_6 .

The large value of C_3 , when you compare it with Q_6 's minimum differential resistance—that is, its maximum signal amplitude—at full control, presents negligible reactance to the lowest frequency-signal-spectrum component. A voltage-doubler rectifier comprising D_1 and D_2 extracts a portion of the signal from output stage Q_4 and produces the control voltage for Q_5 . This arrangement accommodates both polarities of large peak amplitudes of nonsymmetrical signal waveforms. Resistor R_{15} determines the AGC's "attack" time. Too small values of R_{15} in combination with C_6 can lead to instability by creating a pole in the feedback-transfer function. Resistor R_{17} determines the AGC-release time.

To secure good response to high-frequency-signal components, use either Schottky or fast PN silicon diodes for D_1 and D_2 . The dc-coupled complementary cascade comprising Q_2 and Q_3 supplies most of the circuit's voltage gain. A 1-k Ω resistor, R_{14} , isolates Q_4 , the output-emitter follower, from the signal-output terminal. If necessary, you can use a lower resistance at R_{14} , but a large-capacitance connecting cable can provoke Q_4 into parasitic oscillation if R_{14} is too low.

Figure 4 shows the circuit's input-versus-output characteristics as measured with a sine-wave signal. The effective AGC range extends from 100- μ V- to 100-mV-rms input voltage, a 60-dB dynamic range. Output voltage varies less than 2 dB over this input range, reaching a nominal level of 775 mV rms at a -20-dB- (100- μ V-rms) input level. The input's 0-dB point is set arbitrarily at 1-mV-rms input, which corresponds to an 803-mV-rms output. The AGC attack time for a sinusoidal-input-signal step from 0 to 100 mV rms is approximately 0.3 sec, and the AGC

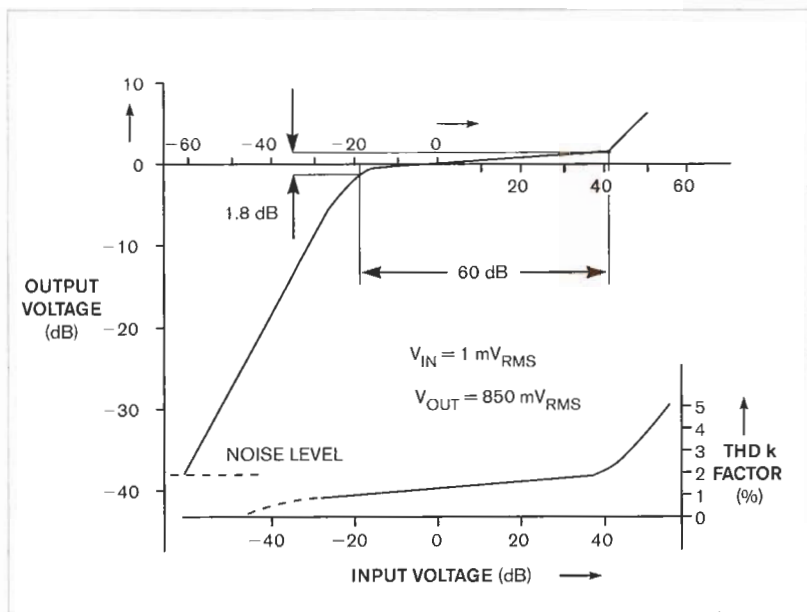


Figure 4 The circuit's input-versus-output characteristic shows a 60-dB control range (upper trace) and total harmonic distortion well below 5% over the control range (lower trace).

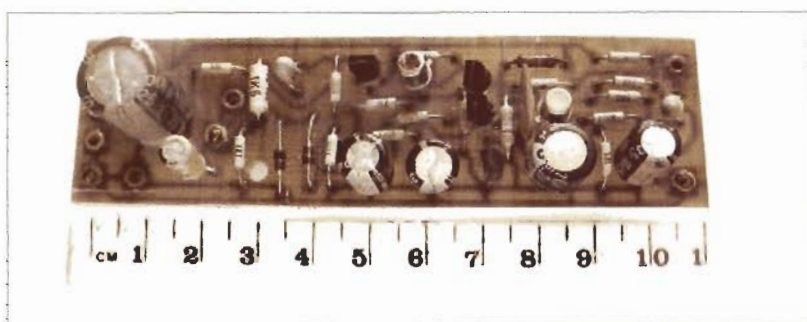


Figure 5 A single-sided pc board accommodates the assembled AGC amplifier.

release from 100-mV-rms input to -20 dB (100 μ V rms) is approximately 100 sec. Figure 4 also includes a graph of THD versus input voltage. The distortion is well below a 5% THD limit throughout the input-voltage range.

To measure the attenuator's baseline input noise, terminate the input with its nominal 1-k Ω source resistance. At low input voltages, input stage Q_1 's noise limits the processed signal's usable dynamic range. The rms noise level is about -38 dB relative to the nominal output for input signals below the AGC

threshold. When the AGC becomes active, the SNR increases in proportion to the AGC reduction. For example, with a 0-dB- (1-mV-rms) input signal, the SNR increases to approximately 60-to-1.

If you assemble the circuit using the passive-component values in Figure 3, the amplifier's -3-dB bandwidth spans 45 Hz to 35 kHz. At a power-supply voltage of 9V, no-signal current consumption is approximately 12 mA. Figure 5 shows a photograph of the assembled pc board. **EDN**