

Gyrator Audio Notch Filter

Using two op-amps from a 4136 quad package, you can implement a very effective notch filter with common component values, the notch frequency ranging from 20 Hz to 2 kHz. Capacitors should be good quality, low voltage metallised poly types.

