

Wien bridge and op amp select notch filter's bandwidth

by Dominique Fellot
Thomson-CSF, Gentilly, France

The band over which a notch filter provides rejection of unwanted frequencies can be selected with this circuit, which uses a Wien bridge plus an operational amplifier with fixed gain. Such a circuit represents one of the simplest configurations for easily adjusting the selectivity of the filter, which has a notch depth of nearly 60 decibels, independent of component precision.

Circuit operation is most easily described with the transfer function shown in the figure, which is:

$$\frac{V_o}{V_i} = \frac{1 - R^2 C^2 \omega^2}{1 - R^2 C^2 \omega^2 + j3(1-k)RC\omega} = \frac{1 - x^2}{1 - x^2 + j3(1-k)x} \quad (1)$$

where $x = \omega/\omega_c = f/f_c = RC\omega$, ω is the frequency of interest, f_c is the center frequency of the notch filter, and k is the percentage of the output voltage from A_1 that is introduced at the noninverting input of A_2 . This transfer function has a transmission zero at $f_c = 1/2\pi RC$, which

is the center frequency of the notch.

The amount of phase shift provided by the Wien bridge (A_1 and the RC components), from Eq. 1, is:

$$\tan\phi = [-3(1-k)x]/(1-x^2) \quad (2)$$

The width of the rejected band at the -3 -dB points can be easily expressed with respect to k by setting $\phi = 45^\circ$, so that Eq. 2 becomes:

$$|\tan\phi| = 1 = [3(1-k)x]/(1-x^2)$$

or:

$$k = (x^2 + 3x + 1)/3x, \text{ for } x < 1 \quad (3)$$

where $x = f_r/f_c$ and f_r is defined as the difference in frequency as measured at the -3 -dB points. Thus, for example, if $f_c = 10$ kilohertz and the desired $x = 0.9$ (or $f_r = 9$ kHz), then k must be set at 0.93.

It will be noted that although the transfer function for the popular twin-T variety of notch filter (not shown) is almost identical to that in Eq. 1 (the constant 3 is replaced by the number 4), in practice, the twin-T is not very easily adjusted. This is because a greater number of components must be trimmed, and more careful adjustments made, to achieve the desired degree of selectivity and notch depth required. \square

Designer's casebook is a regular feature in *Electronics*. We invite readers to submit original and unpublished circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. We'll pay \$50 for each item published.

Selectable stopper. Notch filter, which operates at up to 200 kHz, uses modified Wien bridge to select bandwidth over which frequencies are rejected. RC components determine filter's center frequency. P_1 selects notch bandwidth. Notch depth is fixed at about 60 dB.

