

categories

Alarms and security

Audio

- Audio amplifier
- Audio filter
- Audio mixer
- Audio preamplifier
- Sound level meter
- Speaker protection
- Tone and volume control

Automotive

Digital

For home

Fun and games

General electronics

High voltage

Infrared

LED and light

Metronome

Microcontroller

Miscellaneous

PC related

Power supply

PWM and power control

Radio

Sensor

Solar power

Sound and oscillator

Switches

Telephone related


Timer

Tools and measuring

Video

[home](#) :: [audio](#) :: [tone and volume control](#) :: [automatic loudness control circuit schematic](#)

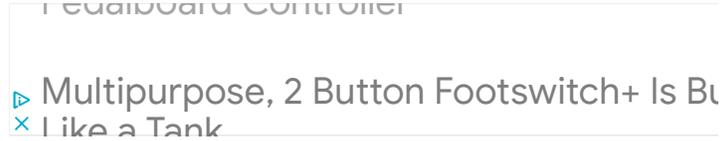Automatic Loudness Control Circuit Schematic



Description


In order to obtain a good audio reproduction at different listening levels, a different tone-controls setting should be necessary to suit the well known behavior of the human ear. In fact, the human ear sensitivity varies in a non-linear manner through the entire audible frequency band, as shown by Fletcher-Munson curves.

A simple approach to this problem can be done inserting a circuit in the preamplifier stage, capable of varying automatically the frequency response of the entire audio chain in respect to the position of the control knob, in order to keep ideal listening conditions under different listening levels.

Fortunately, the human ear is not too critical, so a rather simple circuit can provide a satisfactory performance through a 40dB range. The circuit is shown with SW1 in the "Control-flat" position, i.e. without the Automatic Loudness Control. In this position the circuit acts as a linear preamplifier stage, with the voltage gain set by means of Trimmer R7.

Switching SW1 in the opposite position the circuit becomes an Automatic Loudness Control and its frequency response varies in respect to the position of the control knob by the amount shown in the table below. C1 boosts the low frequencies and C4 boosts the higher ones. Maximum boost at low frequencies is limited by R2; R5 do the same at high frequencies.

Circuit diagram:

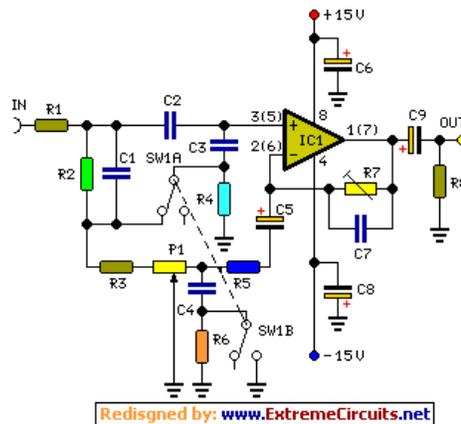

Redesigned by: www.ExtremeCircuits.net

Parts:

- P1 _____ 10K Linear Potentiometer (Dual-gang for stereo)
- R1,R6,R8 _____ 100K 1/4W Resistors
- R2 _____ 27K 1/4W Resistor
- R3,R5 _____ 1K 1/4W Resistors
- R4 _____ 1M 1/4W Resistor
- R7 _____ 20K 1/2W Trimmer Cermet
- C1 _____ 100nF 63V Polyester Capacitor
- C2 _____ 47nF 63V Polyester Capacitor
- C3 _____ 470nF 63V Polyester Capacitor
- C4 _____ 15nF 63V Polyester Capacitor
- C5,C9 _____ 1µF 63V Electrolytic or Polyester Capacitors
- C6,C8 _____ 47µF 63V Electrolytic Capacitors
- C7 _____ 100pF 63V Ceramic Capacitor
- IC1 _____ TL072 Dual BIFET Op-Amp
- SW1 _____ DPDT Switch (four poles for stereo)

Technical data:

Rapid PCBA

Done Fast in the USA

USA-based experts to help you with your rapid prototyping needs.

imscorp

OI

Frequency response referred to 1KHz and different control knob positions:

Knob	100Hz	10KHz
	+14dB	+9.5dB
	+12.6dB	+11.1dB
	+8.2dB	+11.1dB
	+7.2dB	+9.5dB
	+5.0dB	+6.8dB

Total harmonic distortion at all frequencies and 1V RMS output: <0.01%

Notes:

- SW1 is shown in "Control flat" position.
- Schematic shows left channel only, therefore for stereo operation all parts must be doubled except IC1, C6 and C8.
- Numbers in parentheses show IC1 right channel pin connections.
- R7 should be set to obtain maximum undistorted output power from the amplifier with a standard music program source and P1 rotated fully clockwise.

USA-based Experts to Help You With Your Rapid Prototyping Needs.

circuit from <http://www.extremecircuits.net/2010/02/automatic-loudness-control-circuit.html>

similar circuits

- Paraphase Tone Controller
- Digital Volume Control
- Automatic Loudness Control Circuit Schematic
- 10 Band Graphic Equalizer
- 6-Band Graphic Equalizer
- 5 Band Graphic Equalizer
- 3 Band Equalizer
- Equalizer with Parametric Mid
- Audio Auto Fade
- Stereo Preamplifier with adjustment tone
- Automatic Loudness Control
- Simple Digital Volume Control
- Bass-treble tone control circuit