

Audio Amplifier Output Power Meter

By N. Walker

THE CIRCUIT uses the LM3914 Bargraph Display IC which is capable of driving ten LEDs and is therefore ideally suited to the readily available bargraph modules.

The circuit shows a single channel meter but an identical circuit can easily be made up to provide a stereo power meter. The unit operates in a range of 3V to 18V.

