

Part two of this exciting electronic piano series

# LYREBIRD

We describe the touch sensing circuitry



Last month we introduced our Lyrebird 73-note piano which has touch-sensitive keys and soft and sustain pedals. The introductory article discussed the overall concept of the Lyrebird piano and described the circuitry and construction of the tone generator and divider board. In this article we continue by presenting the circuitry and construction of the envelope keying circuit boards.

by LEO SIMPSON & GREG SWAIN

Since the Lyrebird has 73 notes, it has 73 individual sets of contacts which control the keying and envelope of each note. By "keying", in this instance, we mean turning the note source on and off and by "envelope" we mean the way in which the note rises suddenly when first struck (the attack) and then dies away rapidly or slowly (the decay), depending on whether the soft or sustain pedals are used.

The most interesting feature of the keying and envelope circuitry is that it actually responds to the speed at which the individual key is depressed and thus controls the loudness of each note. The mechanism of this action is described below. Refer to Fig. 1.

Each key controls a single-pole single-throw switch,  $S_k$ , which is normally connected to earth when the key is not being pressed. When the player presses the key down, the moving contact of the switch takes a finite time between breaking contact on one side and making contact on the other side, to the +30V rail.

It is during this time between breaking and making contact that  $C_1$  begins to charge towards +VT via  $R_1$  (which is typically  $3.3k\Omega$ ) and  $R_5$ , a  $56\Omega$  resistor. Then, as switch  $S_k$  makes contact with the 30V rail, the positive electrode of  $C_1$  is "raised" by 30V and so  $C_2$  is charged via  $D_1$  to a voltage which is approximately half the difference between 30V and the voltage reached by  $C_1$  before  $S_k$  made contact. In practice, the voltage reached by  $C_2$  will be 14V or less.

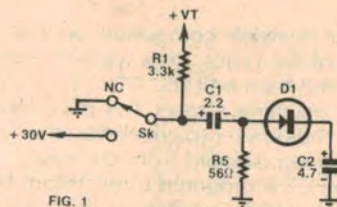


FIG. 1

Thus the charge received by  $C_2$  when  $S_k$  makes contact is inversely proportional to the time taken for the key to be fully depressed. The voltage

on  $C_2$  then controls the initial amplitude of the signal fed to the voicing filters. It does this via  $R_6$ ,  $R_7$ ,  $D_4$ ,  $D_5$  and the two diodes providing each key output on the divider board described last month. This is shown in Fig. 2.

Remember that last month we stated that these pairs of "diodes and the envelope keying circuit actually form an AND gate for each key". Well it is actually  $R_6$  and the two diodes just mentioned that form the AND gate. Current flows from  $C_2$  via  $R_6$  and  $R_7$ . When the respective Q outputs on the divider chip are low, the two associated diodes are forward-biased and the junction of  $R_6$  and  $R_7$  is pulled low. Similarly, when the respective Q outputs are high, the diodes will not conduct and the junction of  $R_6$  and  $R_7$  will be high.

From the foregoing, it follows that the higher the voltage on  $C_2$ , the greater the amplitude of the signal fed to the voicing

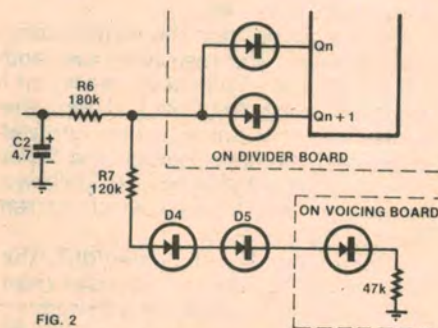


FIG. 2

board via diodes  $D_4$  and  $D_5$ . These two diodes merely provide isolation between the individual keying circuits which feed into common voicing inputs.



# Lyrebird electronic piano

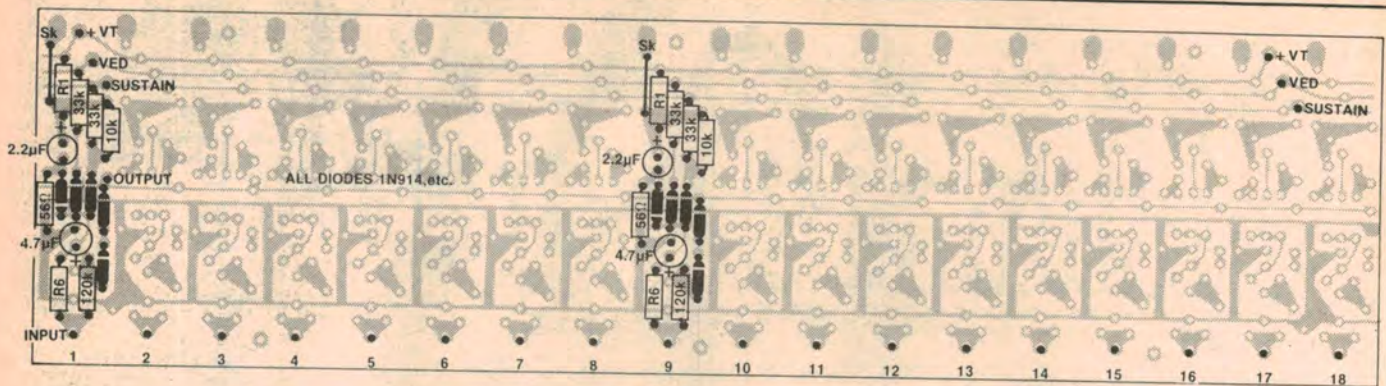


FIG. 8

For simplicity, only two of the 18 sets of components are shown on this envelope PC board. The VT, VED and Sustain points are linked across to the adjacent envelope boards.

extremely large number of opportunities for making mistakes in inserting wrong components and putting capacitors and diodes the wrong way round. You might like to amuse yourself by calculating just how many different combinations of mistakes that you could make but your time would be better spent in resolving to be careful when you assemble the boards.

We suggest that you work on one board at a time to avoid confusion. Start with board one which has to be trimmed to accommodate the 16-note circuit. Install the links and PC pins first, then the resistors and diodes. Remember that for notes one to 16, R1 is 3.3kΩ and R6 is 270kΩ. For notes nine to 16, R1 is 2.7kΩ and R6 is 220kΩ.

The links should be inserted and soldered so that they are about 1mm proud of the board surface. The links actually provide a soldering point for the contact spring associated with each note. While we mention the contact springs now, they are not to be soldered to the boards until the boards and busbars are assembled onto the keyboard chassis.

All the envelope boards should be very carefully inspected for assembly errors and poor soldering. Be very thorough as it is difficult to detect and correct mistakes once the boards are installed on the keyboard chassis.

## KEYBOARD ASSEMBLY

The keyboard assembly requires a fair amount of mechanical work, so you can put away your soldering iron for the time being and take out your electric drill. But

## PARTS LIST KEYBOARD & ENVELOPE BOARDS

- 1 73-note piano keyboard
- 1 set of busbar hardware including spacers, contact springs and self-tapping screws
- 4 18-way PC boards
- 1 three-way PC board
- 1 metre of adhesive-backed foam, 15mm square (Engels)
- 4 hinges to suit keyboard
- 111 PC pins
- 73 2.2µF/25VW PC-mounting electrolytic capacitors
- 73 4.7µF/25VW PC-mounting electrolytic capacitors
- 365 1N914, 1N4148 small-signal silicon diodes
- RESISTORS (10% tolerance, 1/2W rating) 8 x 270kΩ, 18 x 220kΩ, 18 x 180kΩ, 91 x 120kΩ, 11 x 82kΩ, 146 x 33kΩ, 73 x 10kΩ, 19 x 3.3kΩ, 54 x 2.7kΩ, 73 x 56Ω.

before you start brandishing the drill about, more mundane tasks beckon, such as disassembling the keyboard. Why do that when it is supplied in beautifully assembled form? Because the keyboard "action" is too light for a piano is why.

As supplied, the keyboard has one light spring to restore each key to its normal position when pressed. This gives such a light action that you need only brush a key to make a note sound. For a person

used to the inertia and "feel" of a normal piano keyboard which requires some physical effort to play, this makes the keyboard virtually unplayable. Put simply, we have to make it harder to press the keys down. We do this by installing a layer of foam rubber under the keyboard which has a suitable thickness and density.

Each key can be easily detached by removing the small spring at the rear, detaching it from its lug on the keyboard chassis. Note that each key is labelled with a moulded legend such as B4/6 or whatever. This should be noted on a sheet of paper or on the keyboard chassis itself so that when you re-assemble the keys it will not be like a giant jigsaw puzzle. Having removed all the keys you can then proceed to take pencil and rule and mark up the underside of the keyboard chassis with the hole positions shown in Fig. 8.

All the hole positions should be centrepunched and drilled with a 3/32-inch drill bit.

## ADDING FOAM RUBBER

With drilling complete, you can install the busbar blocks and busbars, using self-tapping screws which are not longer than 25mm. With busbars in place you can then install the five boards using 6mm spacers and self-tapping screws. Then you can install the foam rubber. We recommend a foam weatherstrip measuring approximately 15mm square, made by Engels (normally used for weatherproofing of doors and windows). This tape is run along the front edge of

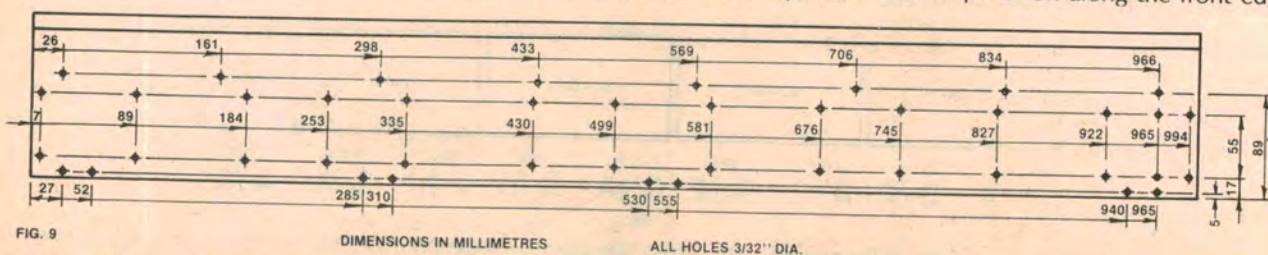


FIG. 9

DIMENSIONS IN MILLIMETRES

ALL HOLES 3/32" DIA.

This diagram shows the positions of all holes which need to be drilled on the underside of the keyboard chassis.

## Lyrebird electronic piano



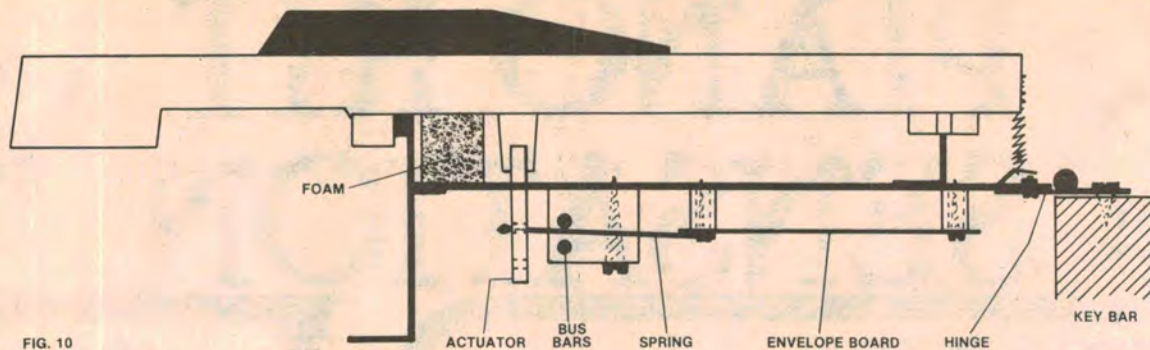


FIG. 10

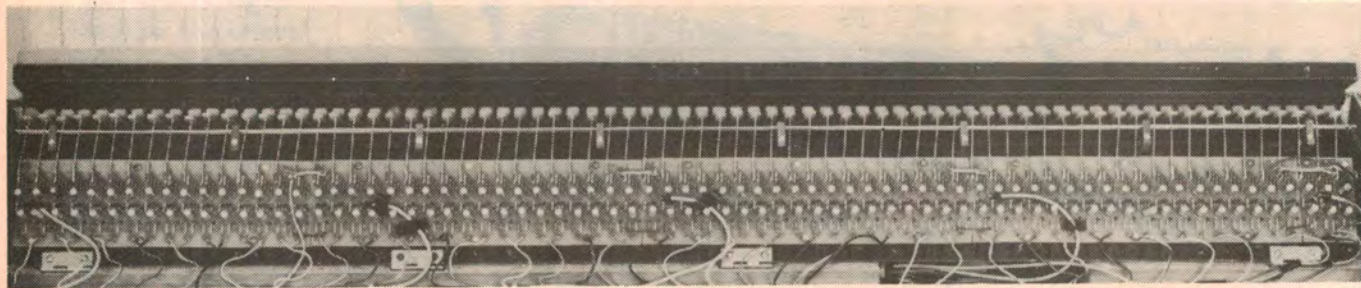This end elevation of the keyboard shows how the foam rubber is positioned and the mounting details of the envelope boards.



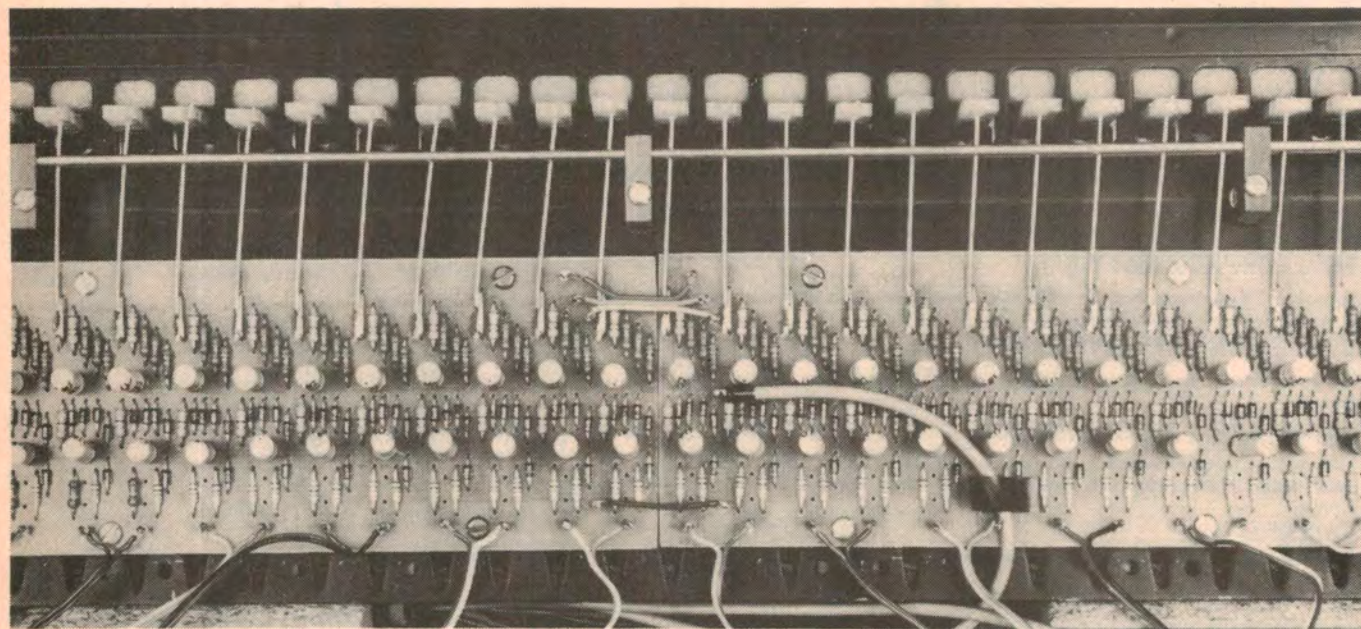This photo shows the five completed envelope boards installed on the underside of the keyboard chassis with each board linked to its neighbour.



Detail of the envelope boards and busbar mounting. Note the long contact spring running from each link to each key actuator. Each envelope board should be very carefully checked for soldering and component positioning before it is installed on the chassis as it is difficult to make alterations once the contact springs are attached.

the keyboard chassis so that it sits just in front of contact actuators.

Now reassemble the keys and you are ready to solder the spring contacts to the envelope boards. As supplied, the springs are about 50mm long (in the unstretched state) and they have a formed head at one end. Position the spring so that its head just protrudes through the busbars and hold it temporarily against the appropriate link

with a small alligator clip and solder the two together.

Now gently stretch the spring by hand and set the head into the key actuator recess. Do not use pliers for this task as you will damage the springs. Fig. 10 shows an end elevation of the keyboard showing how the boards and springs are assembled. Note that the spring should be in contact with the upper busbar when the key is in the rest position and

should contact the lower busbar when the key is pressed. Make sure that the springs do not rub against the busbar mounting blocks. This should not normally be a problem.

Finally, you may trim away the excess spring from the boards, using a pair of side cutters. That is all for this month. Next month we shall describe the voicing filter circuitry and construction of that PC board.