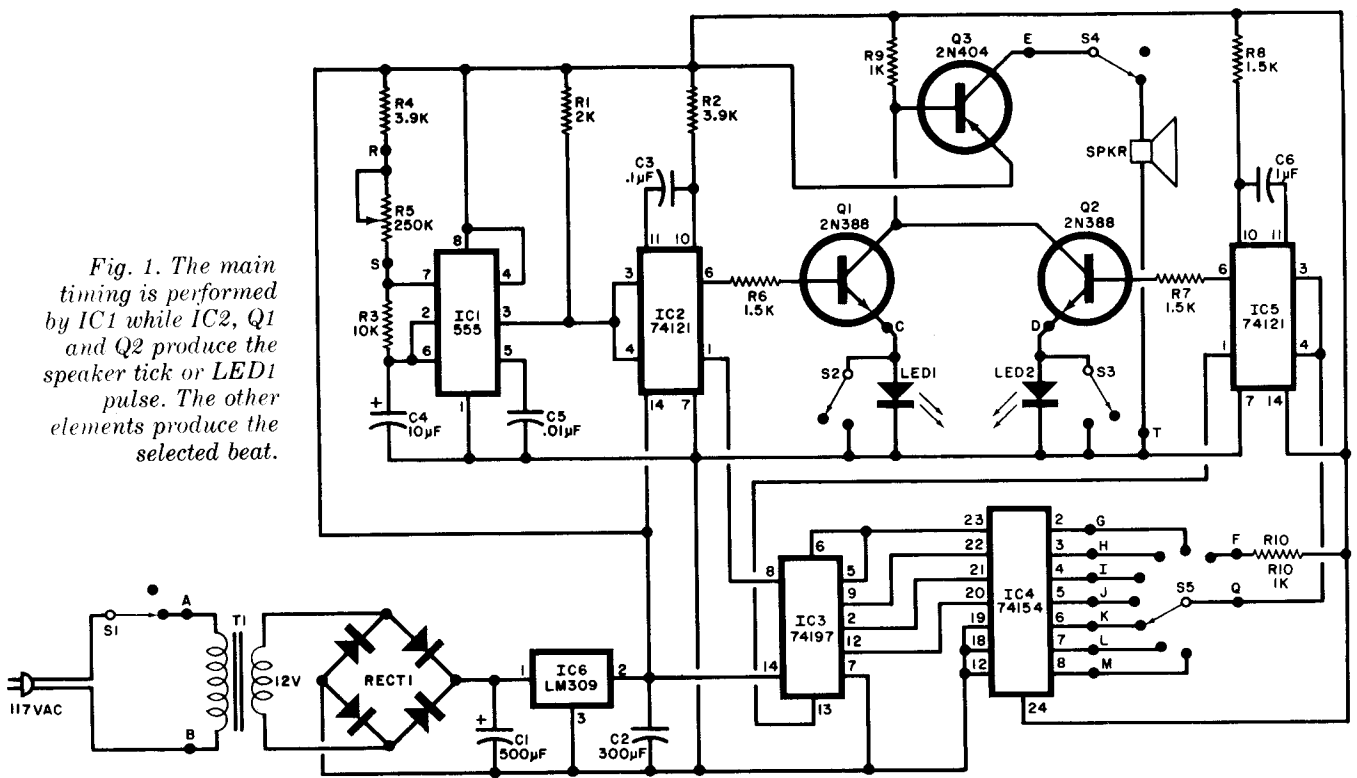


Fig. 1. The main timing is performed by IC1 while IC2, Q1 and Q2 produce the speaker tick or LED1 pulse. The other elements produce the selected beat.



PARTS LIST

- C1—500-µF, 16-V electrolytic capacitor
- C2—300-µF, 10-V electrolytic capacitor
- C3—0.1-µF, 50-V ceramic disc capacitor
- C4—10-µF, 6-V low-leakage electrolytic capacitor
- C5—0.01-µF, 50-V ceramic disc capacitor
- C6—1-µF ceramic capacitor
- IC1—555 timer
- IC2, IC5—74121
- IC3—74197
- IC4—74154

- IC6—LM309, 5-V, 1-A regulator
- LED1, LED2—Red light emitting diode
- Q1, Q2—General-purpose transistor npn (2N388 or similar)
- Q3—General-purpose transistor pnp (2N404 or similar)
- R1—2000-ohm ½-W, 10% resistor
- R2, R4—3900-ohm, ½-W, 10% resistor
- R3—10,000-ohm, ½-W, 10% resistor
- R5—250,000-ohm, linear-taper potentiometer

- R6, R7, R8—1500-ohm, ½-W, 10% resistor
- R9, R10—1000-ohm, ½-W, 10% resistor
- S1 to S4—Spst switch
- S5—Single-pole, 8-position, nonshorting rotary switch
- SPKR—8-ohm, 2" speaker
- T1—12-volt, 300-mA transformer (Radio Shack 273-1385 or similar)
- Misc.—Suitable enclosure, line cord, grommet, switch knob, mounting hardware, etc.

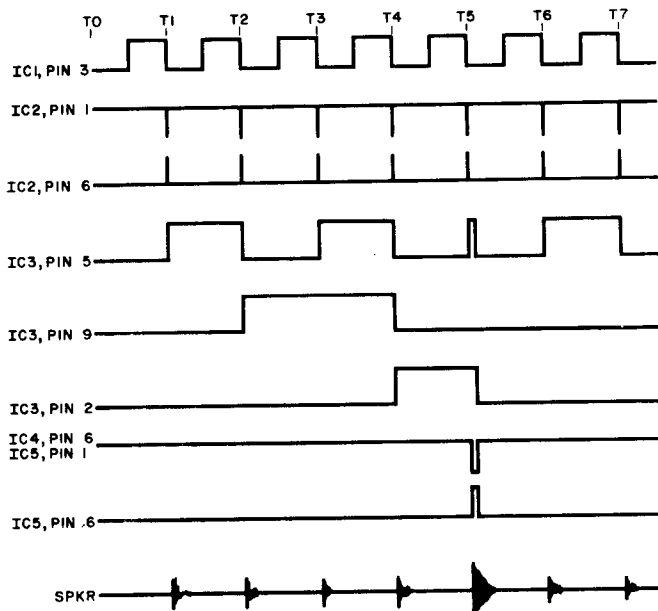


Fig. 2 Timing waveforms for the metronome.

The positive-going pulse from IC2 (pin 6) drives Q1 into conduction and, when S2 is open, causes LED1 to glow. When Q1 conducts, it also forward-biases Q3, causing a current surge through the speaker (when S4 is closed). This provides the main beat.

To generate the accented beat, the output from IC2 (pin 1) is fed to the clock-1 (pin 8) input of IC3, a binary-counter/latch. As shown in the timing diagram in Fig. 2, the IC3 output on pin 5 changes state with each input pulse. Pin 9 changes state every other input pulse, pin 2 every fourth input pulse, and pin 12 every eighth input pulse (not shown in Fig. 2). These four outputs thus make up a 4-bit binary count of the number of input pulses to IC3.

The four outputs are applied to IC4, a 4-to-16 decoder. The sixteen outputs of IC4 provide binary combinations from 0000 to 1111 of decimal 0 to 15. With the circuit shown in Fig. 1, only

the first 7 of these outputs can be selected by S5. The timing in Fig. 2 assumes that S5 is set to position 5 so that the accent pulse will occur every 5 beats.

The signal selected by S5 is used to trigger IC5, a monostable multivibrator that operates like IC2 except that the timing components (R8, C6) are selected to produce an output pulse of about 1 ms (instead of the 250 μ s of IC2). When pin 6 of IC5 goes high, Q1 is driven into saturation, causing LED2 to glow (S3 open) for about 750 ms after Q1 has stopped conducting due to the main beat. This action causes the speaker to produce a louder tone. When pin 6 of IC5 goes high, pin 1 goes low, resetting IC3 to a zero output. The next pulse from IC2 then counts as the first beat of the next series of pulses. This same action takes place regardless of the beats per minute or the setting of S5.

When S5 is in the F position, the trigger input of IC5 (pins 3 and 4) is held high by R10 to prevent any possibility of a stray accented beat. This also permits the use of the circuit as a conventional metronome. With S5 in position G, every beat is accented to provide a volume increase. As mentioned before, other outputs of IC4 and other positions of S5 can be used to select accented beats up to a rate of 1 in 15.

Construction. Any type of construction can be used to build the metronome; and surplus or junkbox components will do. However, the LED's should be selected for similar light output. The size of the transformer given in the Parts List will fit on a pc board. Mount the finished board in a small enclosure with the switches, R5 and LED's on the cover. Punch some holes in the cover for the speaker.

Calibration. Close S1 and S4 and set R5 to midscale with S5 in position F. Count the number of beats per minute (checking the operation of LED1 at the same time). Calibrate the dial of R5 accordingly. At higher speeds, use the accented beat to count. For example, with a 1-in-5 accent, count 27 accented beats in 60 seconds with R5 set for 135 beats per minute.

LED1 is for the main beat, while LED2 displays the accented beat. If you don't need these indicators, they and their associated switches can be omitted. ◆