

THE PROGRAMMABLE MUSIC BOX PART 2

How to add 256 words of memory, plus music box applications.

BY MITCHELL WAITE AND LARRY BROWN

In Part 1 of this article, we discussed the circuit and construction procedure for the basic programmable music box, which contains a 40-note static memory system. This month, we will describe a 256-word memory add-on that greatly expands the programmability and playing time of the music box.

Because the music box uses an un-addressed shift register for storage, increasing the size of the usable memory is simple. The add-on memory system is built around three dual 256-bit shift registers. The entire memory circuit can be assembled on a small printed circuit board and connected to the music box by a multi-conductor cable.

About the Circuit. The complete schematic diagram of the memory ex-

tender is shown in Fig. 1. Note that a 16-conductor cable is used to connect the memory module to the main music box circuit board. This cable carries all the required power, clock and input/output data. (Power is obtained from the music box.)


The clock signal from the music box board is fed to Q1, Q2, and Q3, which shape the leading edge of the clock signal to match the requirements of memory chips IC1, IC2, and IC3. All three IC's are clocked simultaneously. Information is stored when the RECIRC input is disabled.

The data on input lines I1 through I6 changes with instructions from the music box. The memory is clocked once for each change. Output lines O1 through O6 feed the stored data back to the music box when a tune or melody is to be played.

Construction. In Fig. 2 are shown the actual-size etching and drilling and component placement guides for the memory extender module. Wire the board as shown, reserving installation of the IC's for last. Mount and solder into place IC sockets or Molex Soldercons® at the IC locations. Then connect the leads on one end of a length of 16-conductor cable to the pads labelled 1 through 16 on the memory module. Remove IC1 from the basic music box, and solder the free ends of the cable to the same numbered pads in IC1's location on the main circuit board which is located inside the music box.


Next, exercising the usual precautions for handling MOS devices, install IC1, IC2, and IC3 in their sockets on the memory board. Check to make sure that all IC's, transistors, and

Fig. 1. Schematic of the memory extender. Numbered terminals are connected to main board in music box.

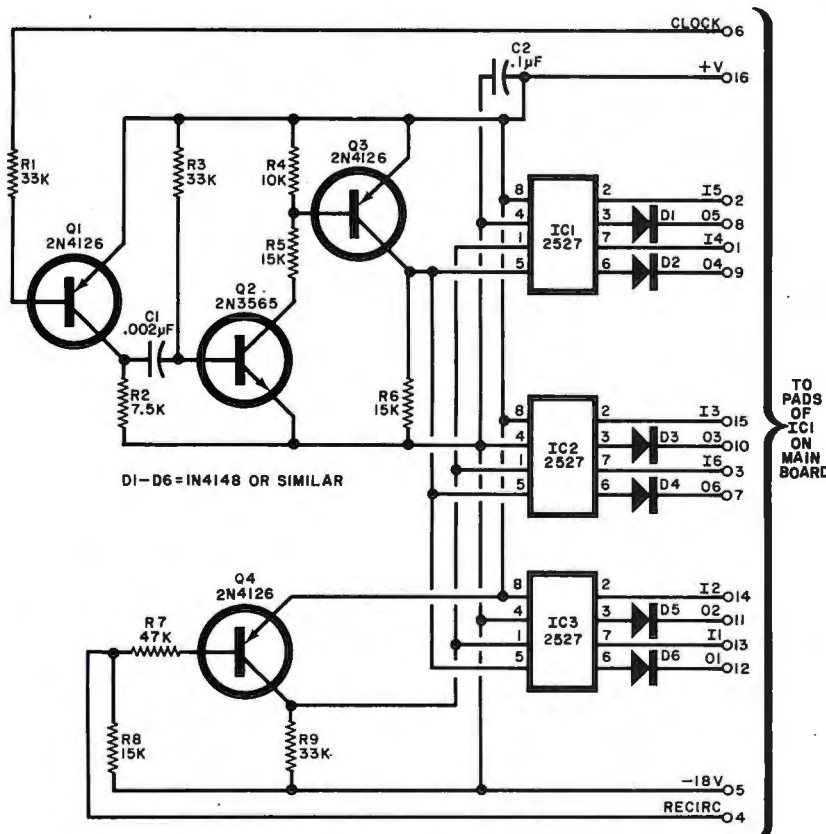

PARTS LIST


C1—0.002- μ F, 100-volt Mylar capacitor
 C2—0.1- μ F, 50-volt Mylar capacitor
 D1 through D6—1N4148 or similar diode
 IC1 through IC3—2527 dual 256-bit shift register IC (Signetics)
 Q1, Q3, Q4—2N4126 or similar transistor
 Q2—2N3565 or similar transistor
 The following resistors are $\frac{1}{4}$ watt, 5%.
 R1, R3, R9—33,000 ohms
 R2—7500 ohms
 R4—10,000 ohms
 R5, R6, R8—15,000 ohms
 R7—47,000 ohms
 Misc.—Printed circuit board; sockets or Molex Soldercons for IC's; 16-conductor cable; hookup wire; machine hardware; solder; etc.
 Note: The following items are available from Cal Kit, P.O. Box 877, Sebastopol, CA 95472: Complete kit of memory extender module parts, including drilled and solder-plated pc board, flat 16-conductor cable, and mounting hardware, No. MC1-6 for \$54.00, IC1, IC2, and IC3, No. MC1-8, for \$43.00; three IC sockets, No. MC1-11, for \$3.00; pc board No. MC1-7 for \$8.00; telephone interface kit No. MC1-5 for \$11.00. All items shipped postpaid and insured. California residents, please add 6% sales tax.

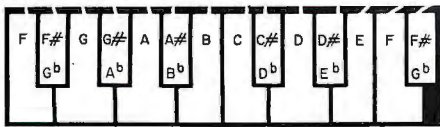

Keyboard of the music box.

Program for "If I Were A Rich Man" from "Fiddler on the Roof."

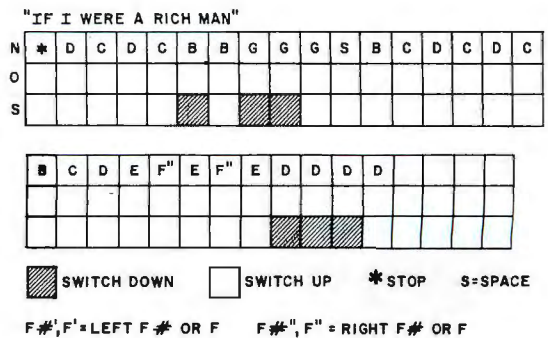(COPYRIGHT © 1964 The New York Times Music Corporation (Sunbeam Division). All rights administered by The New York Times Music Corp. Used by Permission. All rights reserved.)



blank in the SPACE row. You indicate this on your sheet music by entering a 3 after the "C4" entry. The entry "C43" is now interpreted as note C with four words of memory required and the first three spaces removed. Continue to calculate where to remove spaces for the rest of the notes in the melody. If a note is to be in the upper octave, indicate this by underlining the entry on the sheet music form.

In our example, the curved line between the two D notes on the scale forms the "spon" (of "irresponsible"), which means that the two notes are run together. Therefore, you must remove a space from the first D note.

All that remains now is to enter the data onto your programming form. We will use only the first note (C43) to illustrate how this is done; all other entries on the form are made in a similar manner. In the top row, enter a C in boxes 1 through 4. Since the note is not in the upper octave, leave blank the first four blocks in the second row. You want to remove the spaces between only the first three eighth notes, which means you have to fill in the first three boxes in the bottom row.

Programming this note is a relatively simple procedure. Touch the programming probe to the C key,

press the SPACE REMOVE switch and hold it, press the WRITE & STEP switch three times, release the SPACE REMOVE switch, and press the WRITE & STEP switch once again. Proceed to the next note. Programming form for another tune is shown above.

Applications. With the memory extender added to the music box, some interesting programming possibilities are possible. You can, for example, write a long melody into the memory. Alternatively, you can write several shorter tunes, which can be played on demand by touching the keyboard probe to the START key or having a doorbell switch close the same circuit. If each tune starts with a "stop" code, only one melody will play each time the start circuit is activated.

Another way you can use the music box, in either version, is to program the tune you want and accompany it on another instrument or by singing the tune. This approach is better than using a tape recorder because the playback rate of the music box can be increased or slowed down *without changing the pitch*. (Any time you change the speed of a tape recorder, you also change the pitch.)

You can even use the music box as a variable-speed metronome, with or

without accented beat. With a little imagination, it can be programmed to play the rhythm accompaniment to your music.

To use the music box as an unusual replacement for a conventional doorbell or chime system, locate and disconnect the doorbell's pushbutton switch leads at the transformer. Connect these two wires to the main circuit board in the music box via pads 36 (+V) and 35 (start). You can then feed the output of the music box to a power amplifier to obtain attention-getting volume.

If local laws permit, you can build the music box/telephone interface shown in Fig. 3. The actual-size etching and drilling guide and components placement diagram for this circuit are shown in Fig. 4. The telephone interface detects the 20-to-90-Hz ringing voltage that normally operates the phone's bell and uses this voltage to strike (ionize) neon lamp 17. The lamp is optically coupled, via a light-tight shield, to light-dependent resistor LDR1. The LDR is connected to the main board via pads 35 and 36. When the ringing signal occurs, the music box triggers on until the receiver is lifted off the hook or the ringing stops. Because the circuit has a high series resistance, it will not interfere with normal telephone operation. And the optical coupling eliminates any danger to the telephone system by accidental hookup of the power supply to the ac power line.

If you are a radio amateur, you can program short Morse code messages, such as a CQ followed by your call letters. By using a relay in the collector of the audio output circuit, you can key a transmitter.

You can wire two music boxes so that one clock controls both to allow you to play two-note chords in real time. If you have an electronic music synthesizer, you can use the output lines of the music box to drive the synthesizer's control circuits, creating some interesting sequences not possible with a conventional keyboard. ♦

Fig. 3. Schematic for a telephone interface to go with the music box.

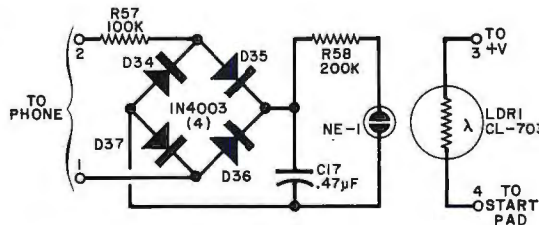


Fig. 4. Etching and drilling guide and component layout for the telephone interface.

