



Fig. 2. If you feel that the guitar bass is a little too pronounced, add this simple adjustable bass-cut filter to the circuit. The pot determines bass level.