

# Tape Noise Limiter

Cut down tape hiss by adding this unit to your cassette recorder.

DESPITE the small size, the performance obtainable from a cassette tape in a good recording deck is quite remarkable. In fact the latest top quality decks are so good that it is difficult to tell the difference between the recording and the original sound. ('is it live or . . .')


Unfortunately this is not true of the cheaper units — in which 'tape hiss' can be very prominent. Tape hiss is caused by random irregularities in a tape's surface coating. The effect is common to all tapes but some are marginally worse than others.

The annoying characteristic of tape hiss delayed the acceptance of cassette tape recorders in hi-fi systems for some years — until the advent of the Dolby system which was primarily developed as a cure for the phenomenon.

The Dolby system is often misunderstood — it *only works if the cassette tape itself has been recorded using the Dolby process* — and few commercially produced tapes are. Unless the tape cassette says specifically that it is Dolby processed then it's not! You can of course record your own tapes using Dolby if you own a Dolby machine.

To overcome this limitation a number of cassette recorders are fitted with noise reduction circuitry which reduces the level of hiss on non-Dolby recordings. Most of these noise reducing circuits work by progressively reducing all high frequency signals when the output level falls below a preset minimum. Above that minimum level all sounds are allowed through because tape hiss cannot be heard once the sound level is substantially louder than the hiss. This effect is called 'acoustic masking'.

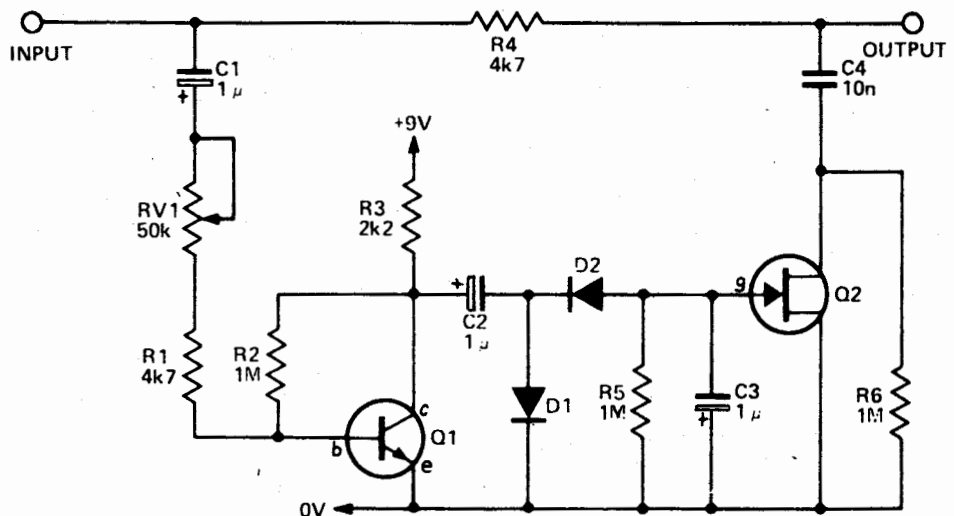The circuit described in this project is a simple but very effective unit which may be used with any cassette recorder which is connected to a hi-fi system.



The unit should preferably be connected between the cassette recorder and the amplifier input — using short lengths of screened cable and suitable connecting plugs. If you really know what you're doing it may be actually built into the tape recorder or amplifier. Alternatively it may be connected between the pre-amplifier and power amplifier on those units which are so separated (note that many apparently integral amplifiers still have 'pre-amp out' and 'power-amp in' connectors on the rear panel. These connectors are normally bridged by 'U' shaped links — which should be removed to enable this unit to be plugged in).

## CONSTRUCTION

As with most projects in this series you can use either Veroboard or the special printed circuit board shown here.

This project may be built using any neat construction method. We have provided both a printed circuit board pattern, and a Veroboard layout showing foil breaks (drilled) and connections.

Take the usual precautions about inserting components the right way round — taking particular care with the field effect transistor Q2. Note that the cathode lead of the diodes (shown as a horizontal bar on the circuit diagram) will be identified on the component by a black band or similar marking.

Unless the leads between this unit and the tape deck and amplifier are very short it is advisable to connect it via screened cable. Note that the 0V line shown on the diagram is also the ground side of the input/output connections.

To set up the unit simply choose a recording with a longish quiet passage and then adjust RV1 for the best compromise between tape hiss reduction and minimum loss of high frequency programme content.

**NOTE:** If you listen only to hard rock — where there aren't any quiet passages — then this unit will be of little value to you. Its main effect is to reduce annoying tape hiss during otherwise quiet programme material.

