

Five-state LED display monitors paging system

by D. F. Fleshren
Springfield, Va.

This paging station circuit uses a single red- or green-light-emitting diode to alert the user to any of five distinct paging conditions. It is a simple, extremely easy-to-build monitor designed to be part of a large paging system. Two relays and a 555 timer send a signal to the LED (a Monsanto MV5491 or Xciton XC5491) to produce the following signals:

- Off (no power) indicates that paging has been cut off to that station or the region in which it is located.
- Steady green signifies that the station is operational, but is not being paged.
- Steady red is the individual station's paging signal.

- Flashing green tells the user that all stations in the system are being alerted.
- Flashing red signals an emergency situation to all monitoring stations.

An external signal triggering relay A controls the color of the LED, changing it from its green (idle) condition to red. Relay B is excited when all stations are to be called. This second relay puts the 555 timer in the astable mode, changing the LED's usual dc state to an on-off oscillation of about 7.5 hertz at a duty cycle of 50%. The frequency of oscillation can be adjusted by suitably selecting R_1 and C_1 . In the emergency red flashing mode, both relays must be tripped by external signals.

This circuit can readily be adapted to signal a single panel-mounted lamp. To derive the five operating modes, the relay contacts must be replaced by the contacts on a suitably wired rotary switch.

Supply voltage for the 555 may vary from 9 to 15 volts; with a 12-v supply, current drain is about 40 milliamperes. □

