

RAY MARSTON

AN AUDIO POWER AMPLIFIER CAN boost weak signals from a tuner, CD player, or tape deck to fill a room with sound. This article focuses on the operating principles and circuitry of low-frequency power amplifiers based on the bipolar junction transistor (BJT). Recent articles in this series have discussed multi-vibrators, oscillators, audio pre-amplifiers, and tone-control circuits, all based on the BJT.


Power amplifier basics

A transistorized audio power amplifier converts the medium-level, medium-impedance AC output voltage of a preamplifier into a high-level, amplified signal that can drive a low-impedance audio transducer such as a speaker. A properly designed power amplifier will do this with minimal signal distortion.

Audio can be amplified with one or more power transistors in either of three configurations: Class A, Class B, and Class AB. Figure 1-a shows a single BJT Class A amplifier in a common-emitter configuration with a speaker as its collector load. A Class A amplifier can be identified by the way its input base is biased.

Fig. 1-a shows that BJT Q1's collector current has a *quiescent* value that is about halfway between the zero bias and cutoff positions. (The quiescent value is that value of transistor bias at which the negative- and positive-going AC input signals are zero.) This bias permits the positive and negative swings of the output collector AC current to reach their highest values without distortion. If the AC and DC impedances of the speaker load are equal, the collector voltage will assume a quiescent value that is about half the supply voltage.

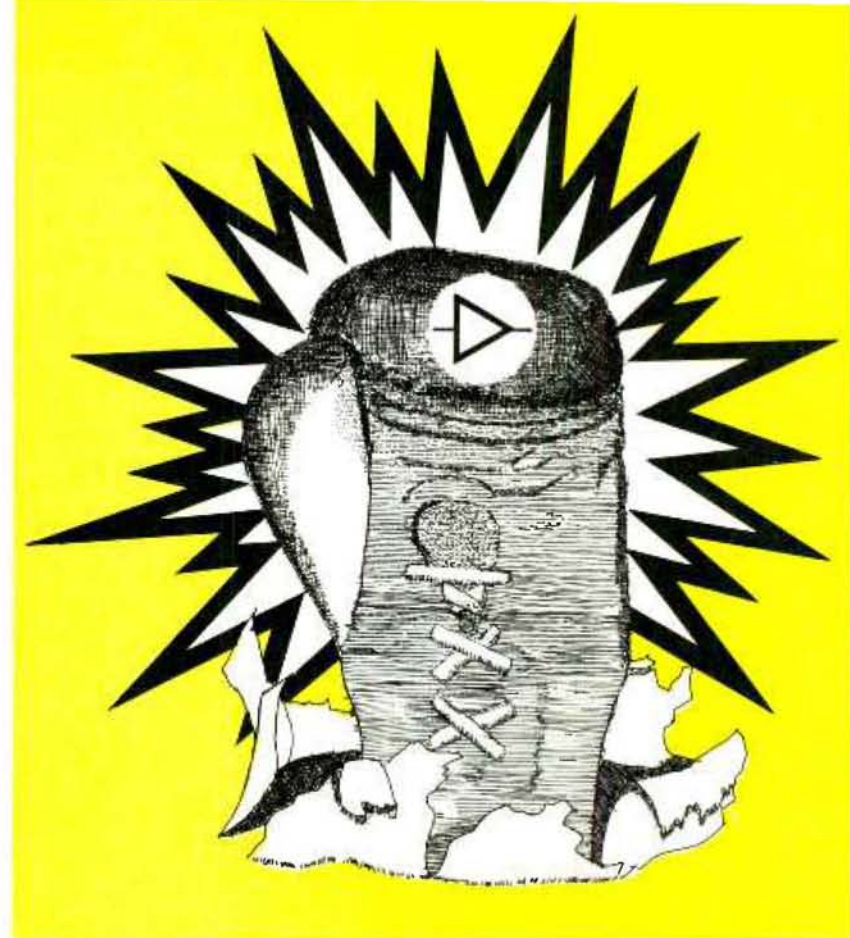The Class A circuit amplifies audio output with minimum distortion, but transistor Q1 consumes current continuously—even in the quiescent state—giving it low efficiency. Amplifier *efficiency* is defined as the ratio of AC power input to the load divided by the DC



POWER AMPLIFIERS

**Learn about audio power amplifiers
and apply this knowledge to your circuit
designs and experiments.**

power consumed by the circuit.

At maximum output power, the efficiency of a typical Class A amplifier is only 40%, about 10% less than its theoretical 50% maximum. However, its efficiency falls to about 4% at one-tenth of its maximum output power level.

A typical Class B amplifier is shown in Fig. 2-a. It has a pair of BJTs, Q1 and Q2, operating 180° out-of-phase driving a common output load, in this example another speaker. In this topology, the BJTs operated as common-emitter amplifiers drive the speaker through push-pull transformer T2. A

phase-splitting transformer, T1, provides the input drives for Q1 and Q2 180° out-of-phase.

The outstanding characteristic of any Class B amplifier is that both transistors are biased off under quiescent conditions because they are operated without base bias. As a result, the amplifier draws almost no quiescent current. This gives it an efficiency that approaches 79% under all operating conditions. In Fig. 2-b, neither Q1 nor Q2 conducts until the input drive signal exceeds the base-emitter zero-crossing voltage of the transistor. This occurs at about 600 millivolts for typical

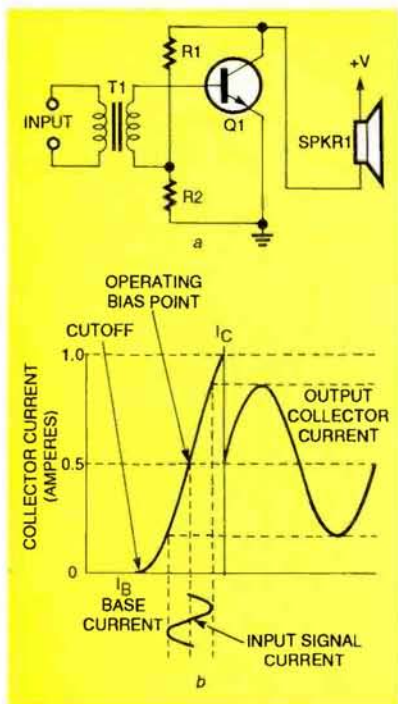


FIG. 1—CLASS A POWER AMPLIFIER circuit (a), and its dynamic transfer curve (b).

power transistor.

The major disadvantage of the Class B amplifier is that its output signal is seriously distorted. This can be seen from its dynamic transfer curve, also shown in Fig. 2-b.

Class AB fundamentals

Audio distortion caused by the crossover between two out-of-phase transistors is annoying. To overcome this defect, the classic Class B amplifier is modified into the third category called Class AB for most high-fidelity audio equipment. Fortunately, Class B distortion can usually be eliminated by applying slight forward bias to the base of each transistor, as shown in Fig 3-a. This modification sharply reduces the quiescent current of a Class B amplifier and converts it into a Class AB amplifier.

Many early transistorized power amplifiers were Class AB, as shown in Fig. 3-a, but that circuit is rarely seen today. That circuit requires one transformer for input phase-splitting and another for driving the speaker, both costly electronic components.

In addition, the electrical

characteristics of both Q1 and Q2 must be closely matched. The amplification of each transistor will be unequal if they are not, and it will be impossible to minimize output distortion. Figure 3a shows a dynamic transfer characteristic for a Class AB power amplifier.

The Class AB amplifier shown in Fig. 4 avoids both transformers and the need to match transistors. A complementary pair of transistors (Q1 an NPN and Q2 a PNP) is connected as an emitter follower. Powered by a split (dual) supply, the circuit's two emitter followers are biased

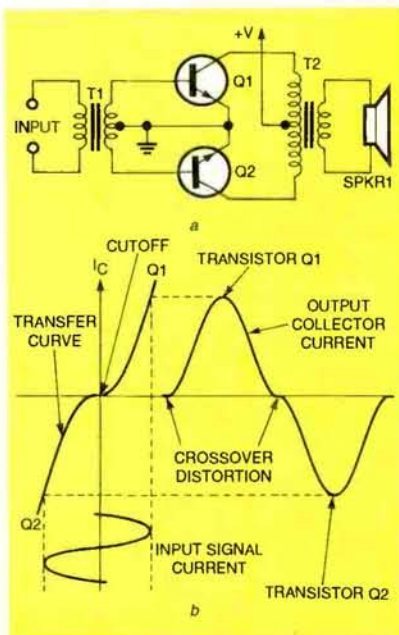


FIG. 2—CLASS B POWER AMPLIFIER circuit (a), and its dynamic transfer curve (b).

through R1 and R2 so that their outputs are at zero volts; no current flows in the speaker under quiescent conditions.

Nevertheless, a slight forward bias can be applied with trimmer potentiometer R3 so that Q1 and Q2 pass modest quiescent currents to prevent crossover distortion. Identical input signals are applied through C1 and C2 to the bases of the emitter followers, which avoid a split-phase drive.

When an input signal is applied to the Fig. 4 circuit, the positive swing drives PNP Q2 off while driving NPN Q1 on. Tran-

sistor Q1 acts as a current source with a very low output (emitter) impedance; it feeds a faithful unity-gain copy of the input voltage signal to the speaker. The transistor characteristics have little or no effect on this response.

Similarly, negative swings of the input signal drive Q1 off and Q2 on. Because Q2 is a PNP BJT, it becomes a current sink with minimal input (emitter) impedance. It also produces a faithful unity-gain copy of the voltage signal to the speaker, again with Q2's characteristics having little or no effect on the circuit's response.

As a result, the Fig. 4 circuit does not require that Q1 be matched to Q2, and neither input nor output transformers are required. Modification of this circuit, as shown in Figs. 5-a and b, work from single-ended power supplies. In Fig. 5-a, one side of the speaker is connected to the amplifier through high-value blocking capacitor C3, and the other end is connected to ground; in Fig. 5-b, one side is connected to C3 and the other side is connected to the positive supply. All three circuits are popular in modern high-fidelity audio

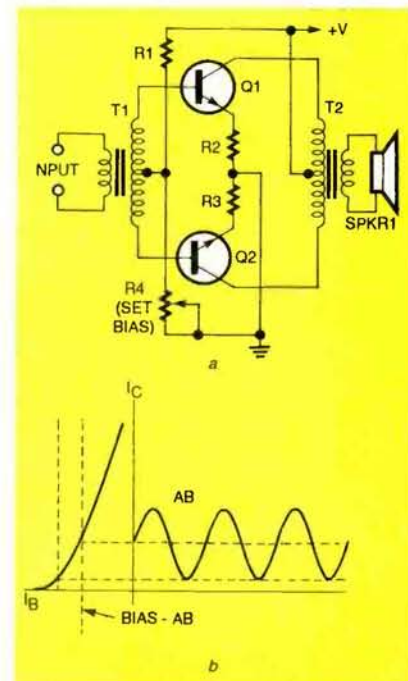


FIG. 3—CLASS AB POWER AMPLIFIER circuit (a), and its dynamic transfer curve (b).

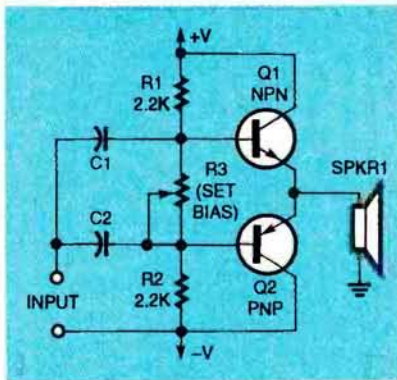


FIG. 4—CLASS AB POWER AMPLIFIER with a complementary emitter-follower output that must be powered by a dual supply.

power amplifiers based on integrated circuitry.

Class AB variations

The circuit in Fig. 4-a is a unity-voltage gain amplifier so one obvious improvement is to add a voltage-amplifying driver stage, as shown in Fig. 6. Transistor Q1, configured as a common-emitter amplifier, drives two emitter followers, Q2 and Q3, through its collector load resistor R1.

Note that Q1's base bias is derived from the circuit's output through resistors R2 and R3. This configuration provides DC feedback to stabilize the circuit's operating points and AC feedback to minimize signal distortion.

The Fig. 6 circuit illustrates how a form of auto-bias can be applied to Q2 and Q3 through the silicon diodes D1 and D2. If the simple voltage-divider biasing method in Fig. 4 is used in the Fig. 6 circuit, its quiescent current will increase as ambient temperature rises and decrease as it falls. (This is caused by the thermal characteristics of a transistor's base-emitter junctions.)

The biasing in Fig. 6 is derived from the forward voltage drop of series diodes D1 and D2 whose thermal characteristics are closely matched to those of the base-emitter junctions of Q2 and Q3. Consequently, this circuit offers excellent thermal compensation.

Practical amplifiers include a pre-set trimmer potentiometer in series with D1 and D2. This

component makes it possible to adjust bias voltage over a limited range. Low-value resistors R4 and R5 in series with the emitters of Q2 and Q3 provide some negative DC feedback.

The impedance of the Fig. 4 circuit equals the product of the speaker load impedance and the current gain of either Q1 or Q2. The circuit can be improved by replacing transistors Q1 and

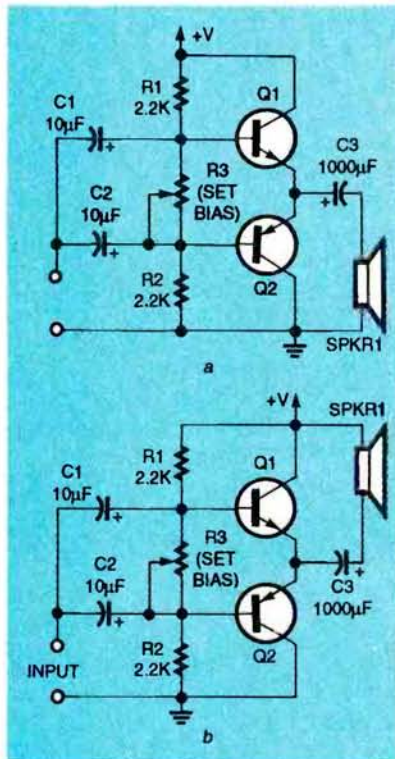


FIG. 5—ALTERNATIVE CLASS AB power amplifier that can be powered with a single-ended supply.

Q2 with Darlington pairs which will significantly increase the circuit's input impedance and increase the amplifier's collector load capacity.

Figures 7 to 9 show three different ways of modifying the Fig. 6 circuit by replacing individual transistors with Darlington pairs. For example, in Fig. 7, transistors Q2 and Q3 form a Darlington NPN pair, and Q4 and Q5 form a Darlington PNP pair. There are four base-emitter junctions between the bases of Q2 and Q4, and the output circuit is biased with a string of four silicon diodes, D1 to D4, in series to compensate for the Darlington pairs.

In Fig. 8, Q2 and Q3 are a Darlington NPN pair, but Q4 and Q5 are a complementary pair of common-emitter amplifiers. They operate with 100% negative feedback, and provide unity-voltage gain and very high input impedance. This *quasi-complementary* output stage is probably the most popular Class AB power amplifier topology today. Notice the three silicon biasing diodes, D1, D2, and D3.

Finally, in Fig. 9, both pairs Q2 and Q3 and Q4 and Q5 are complementary pairs of unity-gain, common-emitter amplifiers with 100% negative feedback. Because the pairs produce outputs that are mirror images of each other, the circuit has a complementary output stage. Notice that this circuit

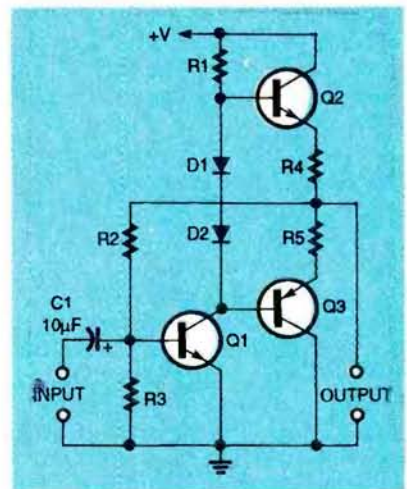


FIG. 6—COMPLEMENTARY power amplifier with a driver and auto-bias.

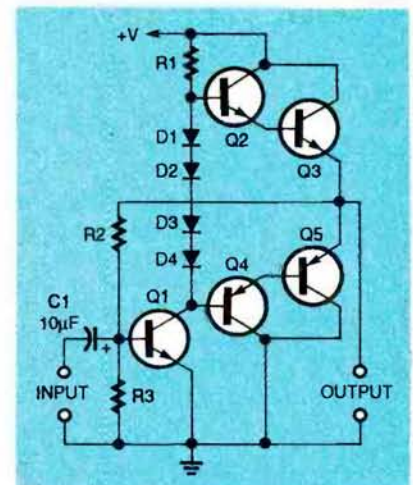


FIG. 7—POWER AMPLIFIER with Darlington output stages.

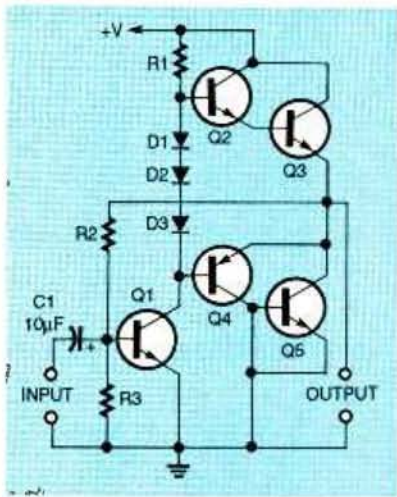


FIG. 8—POWER AMPLIFIER with partial complementary output stages.

has only two silicon biasing diodes, D1 and D2.

Amplified diodes

The circuits in Figs. 6 to 9 include strings of two to four silicon biasing diodes. Each of those strings can be replaced by a single transistor and two resistors configured as an *amplified diode*, as shown in Fig. 10.

The output voltage of the circuit, V_{OUT} , can be calculated from the formula:

$$V_{OUT} = V_{BE} \times R1 + R2/R2$$

If resistor R1 is replaced by a short circuit, the circuit's output will be equal to the base-emitter junction "diode" voltage of Q1 (V_{BE}). The circuit will then have the thermal characteristics of a discrete diode.

If resistor R1 equals R2, the circuit will act like two series-connected diodes, and if R1 equals three times R2, the circuit will act like four series-connected diodes, and so on. Therefore, the circuit in Fig. 10 can be made to simulate any desired whole or fractional number of series-connected diodes, depending on how the R1/R2 ratios are adjusted.

Figure 11 shows how the circuit in Fig. 10 can be modified to act as a fully adjustable "amplified diode," with an output variable from 1 to 5.7 times the base-emitter junction voltage (V_{BE}).

Bootstrapping

The main purpose of the Q1

driver stage in Fig. 6, the basic complementary amplifier, is to give the amplifier significant voltage gain. At any given value of Q1 collector current, this voltage gain is directly proportional to the effective Q1 collector load value. It follows that the value of resistor R1 should be as large as

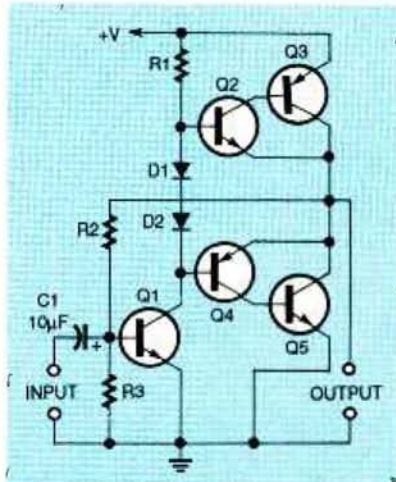


FIG. 9—POWER AMPLIFIER with complementary output stages.

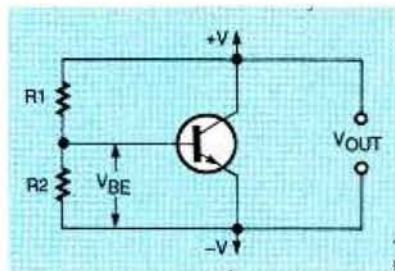


FIG. 10—FIXED-GAIN AMPLIFIED diode circuit.

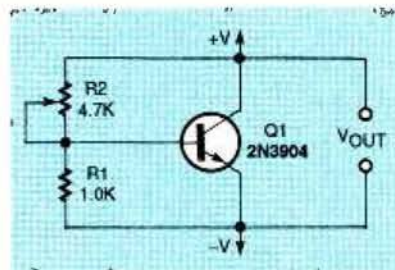


FIG. 11—ADJUSTABLE AMPLIFIED diode circuit.

possible to maximize voltage gain. However, there are several reasons why this does not work.

First, the *effective* or AC value of R1 equals the actual R1 value shunted by the input impedance of the Q2-Q3 power amplifier stage. Therefore, if R1 has a

high value, the power amplifier input impedance must be even greater. That can usually be done by replacing Q2 and Q3 with high-gain transistor pairs, as was done in Figs. 7 to 9.

The second reason is that Q1 in Fig. 6 must be biased so that its collector assumes a quiescent half-supply voltage value to provide maximum output signal swings; this condition is set by the Q1's collector current and resistor R1's value.

The true value of R1 is predetermined by biasing requirements. To achieve high voltage gain, a way must be found to make the AC impedance of R1 much greater than its DC value. This is accomplished with the *bootstrapping* technique shown in Figs. 12 and 13.

In Fig. 12, Q1's collector load consists of R1 and R2 in series. The circuit's output signal, which also appears across SPKR1, is fed back to the R1-R2 junction through C2. This output signal is a near unity-voltage-gain copy of the signal appearing on Q1's collector.

If resistor R1 has a value of 1 kilohm, the Q2-Q3 stage provides a voltage gain of 0.9. As a result, an undefined signal voltage appears at the low end of resistor R2, and 0.9 times that undefined voltage appears at the top of R2. In other words, only one tenth of the unknown signal voltage is developed across R2. Therefore, it passes

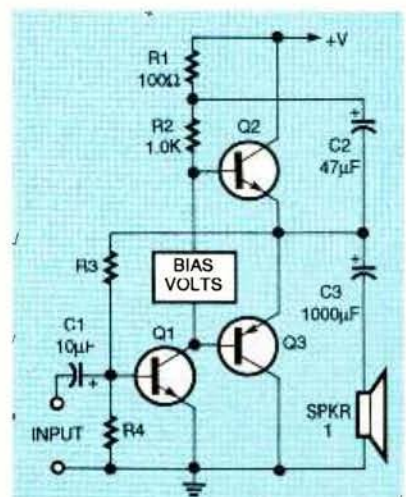


FIG. 12—POWER AMPLIFIER with a bootstrapped driver stage.

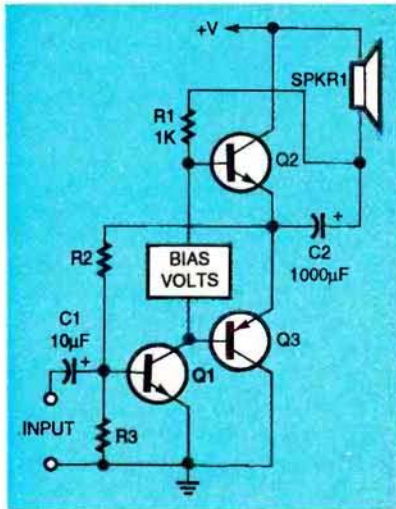


FIG. 13—ALTERNATIVE POWER amplifier with a bootstrapped driver stage.

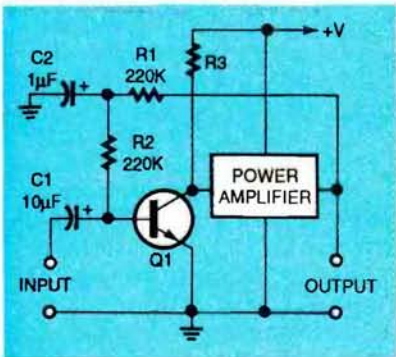


FIG. 14—DRIVER STAGE with decoupled parallel DC feedback.

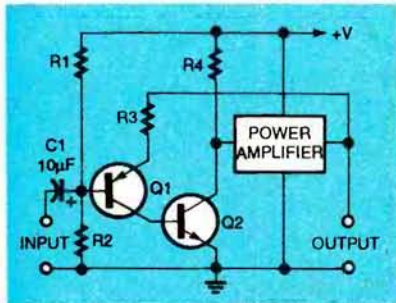


FIG. 15—DRIVER STAGE with series DC feedback.

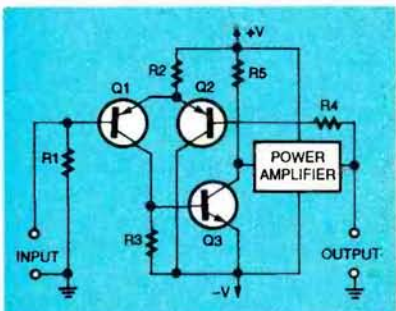


FIG. 16—DRIVER STAGE with a long-tailed pair input.

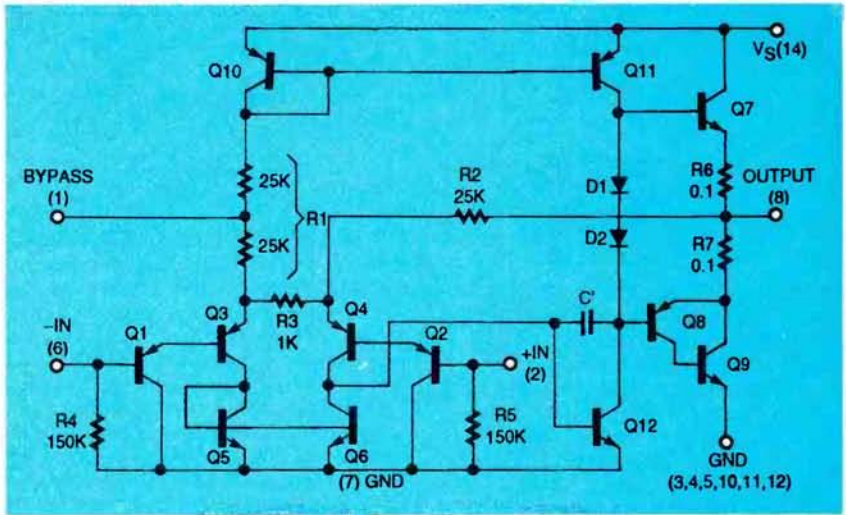


FIG. 17—SCHEMATIC FOR THE LM38 POWER AMPLIFIER IC from National Semiconductor. It has a 2-watt output rating.

only one-tenth of the signal current that would be expected from a 1-kilohm resistor.

This means that the AC signal impedance value of R2 is ten times greater (10 kilohms) than its DC value, and the signal voltage gain is increased correspondingly. In practical circuits, "bootstrapping" permits the effective voltage gain and collector load impedance of Q1 to be increased by a factor of about twenty.

Fig. 13 is the schematic for an alternative version of Fig. 12 without one resistor and one capacitor. In this circuit, SPKR1 is part of Q1's collector load, and it is bootstrapped through capacitor C2.

As an alternative to bootstrapping, the load resistor can be replaced with a simple transistor constant-current generator. This design is found in many integrated circuit audio power amplifiers.

Alternative drivers

Returning once again to Fig. 6, notice that parallel DC and AC voltage from the R1-R2 divider network is fed back to the Q1 driver stage. This is a simple and stable circuit, but its gain and input impedance are low. Moreover, it will work only over a limited power supply voltage range.

Figure 14 is a variation of the Fig. 6 circuit intended to function as a driver stage. Current feedback through resistors R1

and R2 allows the circuit to work over a wide supply voltage range. The feedback resistors can be AC decoupled (as shown) through C2 to increase the gain and input impedance, but at the expense of increased signal distortion. Transistor Q1 can be replaced with a Darlington pair if very high input impedance is desired.

Another alternative driver stage, Fig. 15, depends on series DC and AC feedback to give it more gain and higher input impedance than can be obtained from the Fig. 6 circuit. In this circuit, PNP transistor Q1 is directly coupled to NPN transistor Q2.

Finally, Fig. 16 is the schematic for a driver circuit specifically intended for use in amplifiers with dual or split power supplies that have direct-coupled input and output stages referenced to ground. The input stage of this driver stage is a long-tailed pair. Both the input and output will be centered on DC ground if the values of resistors R1 and R4 are equal. This circuit is found in many integrated circuit power amplifiers.

An IC power amplifier

Improvements in the power-handling capabilities of monolithic integrated circuits have permitted power amplifiers to be integrated on a single silicon substrate or chip. The techniques for designing integrated



CRYSTAL-CONTROLLED! 5 MINUTE ASSEMBLY! MONEYBACK GUARANTEE! Attach 3 wires and hear every whisper up to 2 miles away on any programmable scanner or VHF surveillance receiver. Pre-tested surface mount module uses standard 9V battery for 100mW output! Includes battery box and crystal for 140MHZ. Custom frequencies available for Law Enforcement. Model VX-100 only \$79.95 + 2.00 S&H. VISA, MC, MO. COD add \$5.00. **DECO INDUSTRIES, BOX 607, BEDFORD HILLS, NY 10507. 914-232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

2 Year
Warranty




ULTRA LOW COST LINEAR PROGRAMMABLE POWER SUPPLIES, User-Friendly with LCD Readouts at Analog Prices. Output Voltage/Current Programming and Readback via LCD Panel • Data Entry with Front-Panel Keypad • Power-off Memory • Voltage and Current Step-up/Step-down Function • Microprocessor Controlled • Superior Line/Load Regulation • Output Enable/Disable • Optional RS-232 Interface for Remote Operation (standard on LPS-305) • Intelligent Forced-Air Fan Operation. **AMERICAN RELIANCE, INC., 11801 Goldring Road, Arcadia, CA 91006. Tel: (818) 303-6688 • Fax: (818) 358-3838**

CIRCLE 186 ON FREE INFORMATION CARD



GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from \$9.95 in qty and you can sell recharged toner cartridges for \$40.00 to \$55.00 each. Printers include HP LaserJet Series I, II, III, IV, Apple LaserWriter, QMS, etc. Canon PC Copiers also. **CHENESKO PRODUCTS, 2221 Fifth Ave., Suite #4, Ronkonkoma, NY 11779, 516-467-3205. FAX 516-467-3223, 1-800-221-3516**

CIRCLE 110 ON FREE INFORMATION CARD

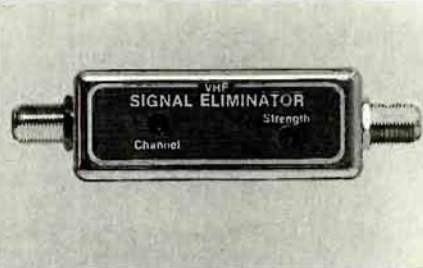

CABLE TV 50dB NOTCH FILTERS for interference removal or channel censoring. Filters are user-adjustable to desired channel # or frequency. Eight Models available, each for certain channels: 2 & 3; 4 to 6; 7 to 13; 14 to 17; 18 to 22; 23 to 29; 30 to 36; 95 to 99 plus 0 & 1. Just \$30 each or 3 for \$75, includes shipping. **ONE MONTH MONEY BACK**, fast delivery. Visa, MC, check or M.O. (C.O.D. is \$5 extra) Huge discounts for higher quantities. **STAR CIRCUITS, P.O. Box 94917, Las Vegas, NV 89193. Call 24 hours 1-800-535-7827.**

circuit power amplifiers are similar to those for discrete device circuits. It turns out that the similarities between discrete and IC power amplifier design are closer than for most other linear circuits.

Figure 17 is a simplified circuit diagram for the LM380, an IC power amplifier, drawn in the manufacturer's data book style. The LM380 was developed by National Semiconductor Corporation for consumer applications. It features an internally fixed gain of 50 (34 dB) and an output that automatically centers itself at one-half of the supply voltage.


An unusual input stage permits inputs to be referenced to the ground or AC coupled, as required. The output stage of the LM380 is protected with both short-circuit current limiting and thermal-shutdown circuitry.

The LM380 has two input terminals. Both Q1 and Q2 are connected as PNP emitter followers that drive the Q3 and Q4 differential amplifier transistor pairs. The PNP inputs reference the input to ground, thus permitting direct coupling of the input transducer.

The output is biased to half the supply voltage by resistor ratio R1/R2 (resistor R1 is formed by two 25-kilohm resistors and R2 has a value of 25 kilohms). Negative DC feedback, through resistor R2, balances the differential stage with the output at half supply, because $R1 = 2R2$.

The output of the differential amplifier stage is direct coupled into the base of Q12, which is a common-emitter, voltage-gain amplifier with a constant current-source load provided by Q11. Internal compensation is provided by the pole-splitting capacitor C'. Pole-splitting compensation permits wide power bandwidth (100 kHz at 2 watts, 8 ohms).

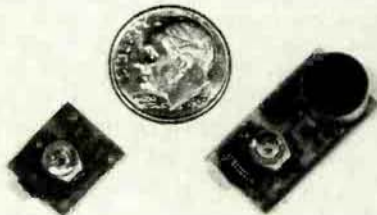The collector signal of Q12 is fed to output pin 8 of the IC through the combination of emitter-coupled Q7 and the quasi-complementary pair of emitter followers Q8 and Q9. The short-circuit current is typically 1.3 amperes. Ω



WORLD'S SMALLEST FM TRANSMITTERS! New Surface Mount Technology (SMT) makes all others obsolete! XST500 Transmitter—powerful 3 transistor audio amplifier, transmits whispers up to 1 mile. XSP250 Telephone Transmitter—line powered, transmits conversations up to ¼ mile. Both tune 88-108 MHz. Easy to assemble E-Z KITS (SMT components pre-assembled to circuit board!) XST500—\$44.95, XSP250—\$34.95, VISA/MC. COD add \$6. **XANDI ELECTRONICS, 201 E. Southern Ave., Suite 111, Tempe, AZ 85282. 1-800-336-7389.**

CIRCLE 177 ON FREE INFORMATION CARD



AFFORDABLE LABORATORY POWER SUPPLIES. Direct keyboard data entry for Voltage and current settings—or slew up/down to sweep outputs. DC enable/disable control. Large LED readouts. RS232 is standard. Program Voltage with your PC and read back the current. Free communications software provided. Models from 12.5V to 125V; 75 Watts. \$429.00—\$449. MC, VISA, and AMEX are OK. **KEPCO INC., Flushing, NY 11352. 718-461-7000; FAX: 718-767-1102.**

CIRCLE 192 ON FREE INFORMATION CARD