



The LT1056 is there as an impedance buffer

The BF245 is there to improve the positive drive capability of the comparator output

These four small signal transistors do the level-shifting; they transform +5V PWM to +- 25V with very low latency (~10ns)

The BD829/BD830 pair is there to perform a necessary extra current amplification

Copyright (c) 2001 Johan Sørensen.
 Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.1 or any later version published by the Free Software Foundation; with the Invariant Sections being this copyright & license notice, with no Front-Cover Texts, and with no Back-Cover Texts.
 A copy of the license is included in the file entitled "License.htm".