



The LT1056 is there as an impedance buffer

The BF245 is there to improve the positive drive capability of its comparator output.
The single inverter U19A is just a buffer, feeding the filters/skew circuits that adjust the turn on of the MOSFET outputs

See the accompanying design description document for more information about the output circuit.

Copyright (c) 2001-2002 Johan Sørensen.
Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License Version 1.1 or any later version published by the Free Software Foundation;
with the Invariant Sections being this copyright & license notice, with no Front-Cover Texts, and with no Back-Cover Texts.
A copy of the license is included in the file entitled "License.htm".