

Improving the Mugen amplifier

Dear Editor — I believe the linearity of cathode follower V2a in the Mugen amplifier (*Elektor* October 2007, Ed.) may be improved by connecting the lower end of R7 (22k Ω) to output of the amplifier (junction 21,22) instead of to ground. The modification enables R7 to function as a real current source, reducing the current fluctuations in the ECC88. The result is better cathode tracking and reduced distortion.

Guido Tent (Netherlands)