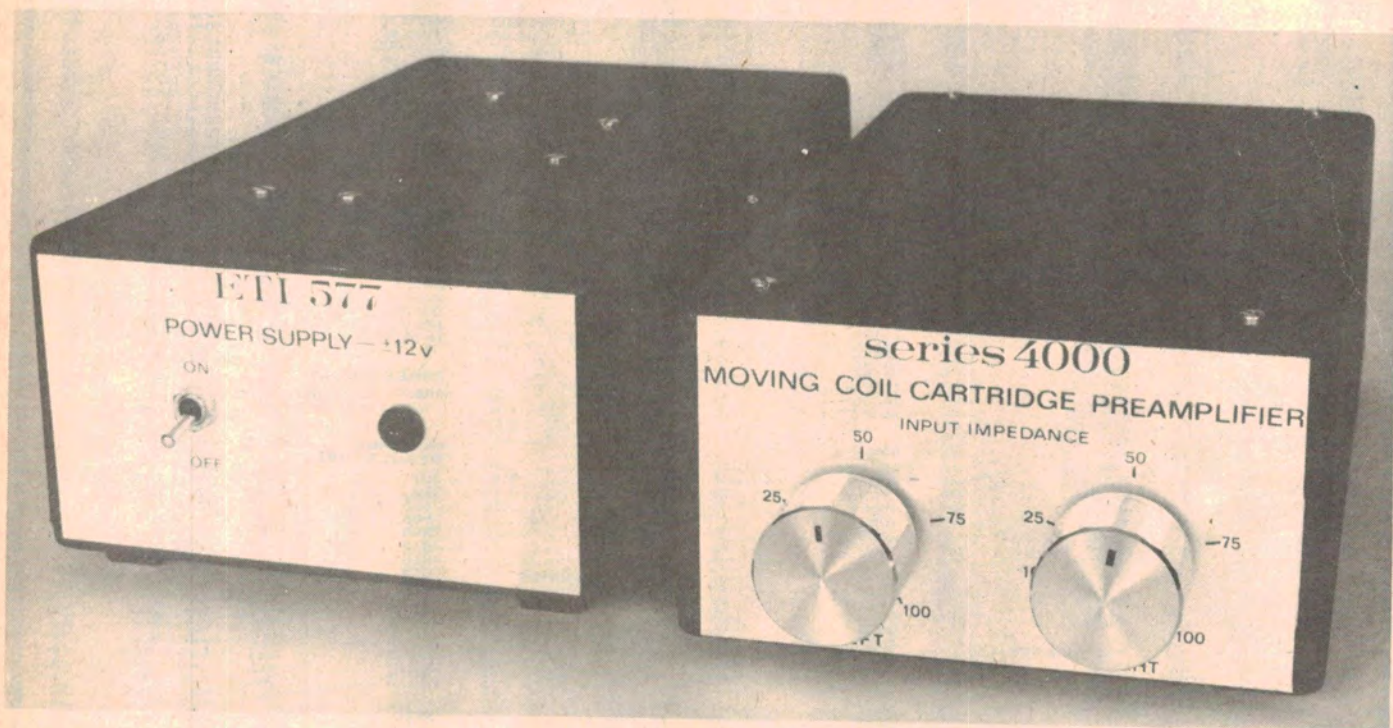


Series 4000 moving-coil cartridge preamplifier

David Tilbrook

Designed to complement our popular Series 4000 stereo amplifier, this project features performance equal to, or better than, top quality commercial preamps currently available.



OVER THE LAST several years there has been a dramatic increase in the number of moving coil cartridges released. The design of this type of cartridge results in a number of advantages over the more usual phono cartridge which works on a moving magnet principle.

Modulations on the wall of the record are tracked with a diamond stylus attached to a long arm called a cantilever. In the moving-magnet cartridge a small magnet is attached to the cantilever so that stylus movement causes movement of the magnet. Two pick-up coils are mounted close to the

magnet so that the windings of the coils intersect the lines of magnetic flux from the magnet. As the stylus moves the magnetic flux seen by the pick-up coils varies in direct proportion to the stylus movement, and small electrical signals are generated in the coils.

The moving-coil cartridge works in a similar way but inverts the roles of the pick-up coils and magnet. The magnet assembly is held stationary while the pick-up coils are mounted on the cantilever assembly and move with the stylus modulations (hence the name 'moving coil').

The pick-up coils are reduced

drastically in size and weight compared to the coils used in moving magnet cartridges. This results in a total cantilever weight that is much smaller than in the typical moving magnet cartridge. Since the weight is greatly reduced the ability of the stylus to react to transients is increased and an overall improvement in signal accuracy results. Moving coil cartridges generally have superior frequency response characteristics and improved phase response at high frequencies. But they also have disadvantages.

The small pick-up coils have a very low impedance resulting in much lower

signal levels than available from normal phono cartridges. In fact, the voltages present on the typical moving-coil cartridge at a recording velocity of 10 cm/sec can be in the order of 150 μ V! This is generally insufficient to drive an amplifier to anything like full power. Furthermore, since the output level is some 30 dB below that expected by the amplifier then a great reduction in the signal-to-noise ratio will result. An amplifier with a short circuit signal to noise ratio of 80 dB for example, which is quite a good figure, will end up with a signal noise ratio of about 50 dB — which is distinctly *bad*.

The internal impedance of moving-coil cartridges is around 5 ohms and to achieve the low recommended load impedance required it is clearly not satisfactory to simply load down the input of the average phono input with a resistor since this does nothing to overcome the signal-to-noise ratio problems.

The solution to these problems is to insert some voltage gain between the output of the cartridge and the phono input. This can be done in two ways. Firstly, it is possible to use a transformer to boost the voltages up to the desired level and they are capable of very good results. But, transformers are still limited in transient performance and noise. To obtain the necessary voltage gain the turns ratio must be relatively high. Since the impedance ratio is related to the square of the turns ratio, the output impedance must, of necessity, be high also — usually around 30 k for a 50 Ω input impedance. This is substantially higher than the output impedance of normal phono cartridges and degrades the noise figure of the phono input stage. A solution to this is to use a pre-amplifier instead of a transformer to achieve the necessary voltage gain.

Preamp requirements

Preamplifiers have their disadvantages also. The biggest problem by far is the design of an extremely low noise input stage with the correct input impedance to load the cartridge according to the manufacturers' recommendations. The distortion must be kept to a minimum and the frequency response should be as flat as possible. These design goals are not unique to a moving coil cartridge preamplifier but they are difficult to achieve owing to the very low output voltage of the moving coil cartridge.

The required low input impedance can be achieved in several ways. Firstly, we can make the input stage a common

SPECIFICATIONS — ETI 473 moving coil cartridge preamp.	
Gain	28 dB (x 25 approx).
Frequency response	29 Hz to 48 kHz \pm 1 dB.
Input impedance	Adjustable 3.3 to 100 ohms.
Noise	Total equivalent input noise 0.3 nV/ $\sqrt{\text{Hz}}$. Over a 20 kHz noise bandwidth—42nV. Signal-to-noise ratio, with respect to an input level of 150 μ V: -71dB.
Total Harmonic distortion.	With respect to an input level of 0.2mV, unmeasurable (below noise). Calculated to be 0.0015% (see text). Rising to 0.015% for a 30 mV input signal at 1 kHz.
Channel separation	Better than 61 dB.
Input overload margin	better than 80 dB.

base configuration. In this type of circuit the input is connected to the emitter of the transistor so that the input impedance is determined by the emitter resistor in parallel with the base-emitter junction of the input transistor, which can be quite low. However, this does not solve the problem of input stage noise.

The other possibility, and the one I elected to use in this design, is common emitter configuration. The impedance of the base-emitter junction of a bipolar transistor is a function of the amount of current flowing in the emitter of the transistor. This will be largely determined by the collector current and not by the base current, which will contribute only a small amount of the total emitter current. A study of base-emitter turn-on characteristics shows that the impedance of the base-emitter junction is approximately equal to:

$$\frac{26\beta}{I_e \text{ (mA)}}$$

where ' β ' is the small signal current gain of the transistor. and ' I_e ' is the current in the emitter of the transistor in mA.

So, to reduce the input impedance of the first stage it is simply necessary to increase the emitter current. But this increases the current density in the input transistors, increasing the noise generated by the input stage.

To understand why this happens it is necessary to look more closely at the causes of noise.

Noise

There are two main sources of noise in transistors: shot noise and 1/f noise. Shot noise is the main cause of noise at middle and high frequencies and is generated when an electron attempts to cross a potential barrier. It is therefore directly related to the amount of charge flowing in the device. More specifically, it is given by the equation:

$$I_s^2 = 2qI_{dc}B \text{ (amps)}^2$$

(mean shot noise current)

where 'q' is the charge of an electron, in coulombs

' I_{dc} ' is the dc current in amps and 'B' is the noise bandwidth in Hz.

1/f noise has a random amplitude like shot noise but its spectral density has a 1/f characteristic. This means that the noise amplitude increases as frequency decreases and becomes the dominant source of noise at low frequencies. As with shot noise, its equation reveals that it is directly related to the current flowing in the transistor.


$$I_f^2 = K \frac{(I_{dc})^a}{f} B$$

where ' I_{dc} ' is the dc current in amps 'K' and 'a' are constants that are a function of the particular device

'f' is the frequency in Hz and 'B' is the noise bandwidth.

Notice that as I_{dc} is increased, so too is the 1/f noise (I_f^2)

It is clear from this that, in order to keep noise generated by shot and 1/f noise to a minimum, it is necessary to keep the current density in the input stage low. But, as we saw earlier, to obtain the necessary low input impedance we have to increase the emitter current. The solution to this is to use several transistors in parallel to form the input device. This decreases the current density in each of the transistors since the necessary emitter current can be shared by all of the input devices. It also places the impedances of the base-emitter junctions in parallel, further decreasing the input impedance of the first stage. Furthermore, since each transistor is a completely independent noise generator their noise voltage will tend to reduce each other (a process too complex to examine in detail here).

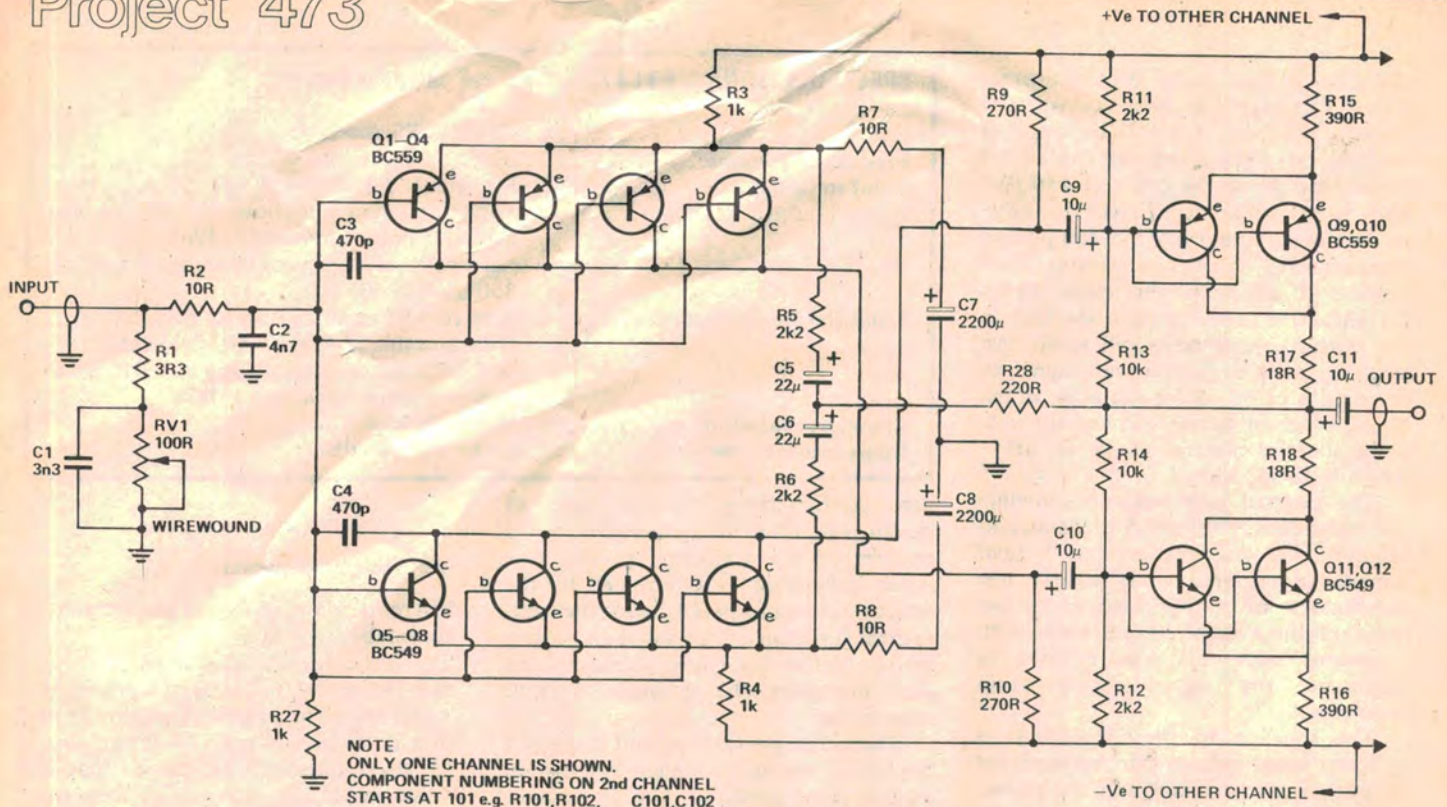

HOW IT WORKS - ETI473

The input stage consists of Q1 to Q8 plus associated circuitry. Q1 to Q4 and Q5 to Q8 are in parallel to reduce the current density providing a low input impedance stage having very low noise. A detailed account of how this works is given in the text.

Capacitor C1 and C2 fix the upper frequency roll-off characteristics as well as shunting the input with the desired load capacitance for the moving-coil cartridge. The configuration of R1 and R2, C1 and C2 was found to give the best loading for a variety of moving-coil cartridges.

The potentiometer RV1 allows the input impedance to be varied over the range most commonly recommended by cartridge manufacturers.

Negative feedback is applied via the network consisting of R28, capacitors C5 and C6 and resistors R5 and R6. Some degenerative feedback for the input stage is applied to the first stage by the

emitter resistors R7 and R8. Capacitors C9 and C10 are coupling capacitors to the second stage while bias for this stage is determined by R11, R12, R13 and R14.

The power supply consists of a series regulator Q13 and Q14. The potential dividers R21/R23 and R22/R24 divide the voltage present at the output of the regulator and drive the transistors Q15 and Q16, and the LEDs. The transistor base-emitter junction in series with the LED will drop 0.6 + 1.65 volts. Therefore, whenever the voltage present at the centre of the potential divider tries to increase above 2.3 volts the transistor increasingly, conducts decreasing drive to the pass transistors Q13 and Q14.

This is a relatively low noise regulator since the voltage reference is LED and not a zener diode which is a noisy device. Resistors R19 and R20, together with capacitors C12 and C13 form 6 dB per octave low-pass filters on the supply rails to further reduce noise that may be generated by the regulated supply. . .

This configuration works very well and the noise levels of this preamplifier rival any of the commercially available units.

To see just how difficult it is to obtain a satisfactory signal to noise ratio at these signal levels it is necessary to look at another form of noise called 'thermal noise'. This is caused by the agitation of charged particles in any conductor due to their temperature. Every passive component will generate thermal noise and short of dunking the

whole thing in liquid helium to cool it off, there is simply no way of getting rid of it. Thermal noise is given by the equation:

$$e_R^2 = 4kTRB \text{ volts}^2$$

where 'T' is the temperature in degrees Kelvin (K).

'R' is the value of the resistance.

'B' is the noise bandwidth

'k' is Boltzmann's constant, equal to 1.38×10^{-23} W-sec/K.

From this equation we can calculate the theoretical noise that will be generated by the moving coil cartridge itself. This clearly is the absolute lowest noise figure that is possible with the input stage generating no noise of its own (which is very unlikely!).


If we let the temperature of the transistor be 300 Kelvin (i.e.: mean atmospheric temperature) and the noise bandwidth be 20 kHz (the hi-fi audio band), then since the dc resistance of the cartridge is about 5 ohms the equation becomes:

$$e_R^2 = 4 \times (1.38 \times 10^{-23}) \times 300 \times 5 \times (20 \times 10^3)$$

$$\text{Therefore } e_R = 4.07 \times 10^{-8} \text{ volts or } 41 \text{ nV.}$$

So, the thermal noise of the cartridge itself is 41 nV.

Actually, this calculation is not quite right since the noise bandwidth is defined as having a 'brick wall' response. An amplifier with 3 dB point of 20 kHz that is falling at a rate of 6 dB per octave will actually have a noise bandwidth much greater than 20 kHz. Furthermore, if we want to be able to quote noise figures to enable comparison between different input stages, it is valuable to quote noise voltages independently of noise bandwidth. This can be done quite easily by dividing the noise voltage by the square root of the bandwidth. The dimensions of this new figure will be "volts per root Hz",

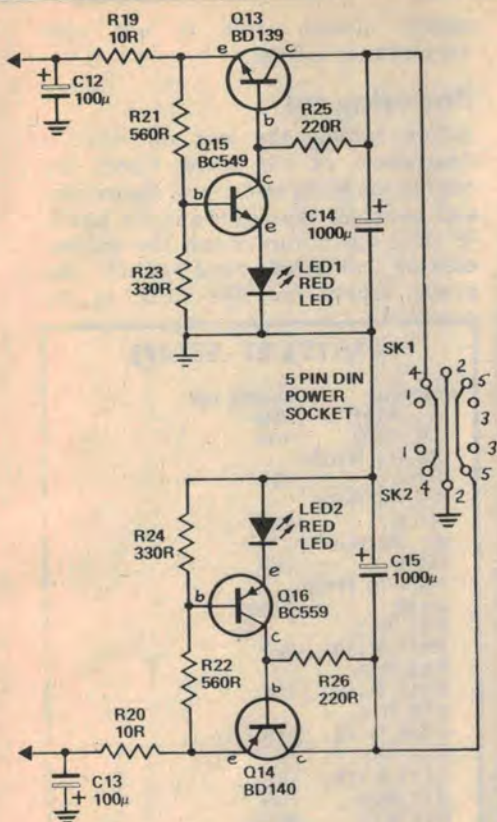

and our result for the thermal noise of a moving coil cartridge becomes:

$$\frac{41}{\sqrt{20\,000}} \text{ nV}/\sqrt{\text{Hz}}$$

or 0.29 nV/ $\sqrt{\text{Hz}}$

Now, if we are aiming at a signal to noise ratio of 70 dB with respect to a signal voltage of 150 nV (0.15 mV), which is the expected signal level at a recording velocity of 10 cm/sec., then the equivalent input noise of the amplifier will be given by the equation:

$$-70 = 20 \log \left(\frac{N}{0.15 \times 10^{-3}} \right)$$

and is equal to 0.33 nV/ $\sqrt{\text{Hz}}$.

The necessary equivalent input noise is in the same order of magnitude as the noise being generated by the cartridge itself!

Designing an input stage with this sort of noise isn't easy, especially when it is considered that the noise generated by even the quietest transistor is in the order of several nV/ $\sqrt{\text{Hz}}$ for usable emitter current. This is substantially worse than the requirement.

Performance features

The total equivalent input noise of this unit was measured at 0.3 nV/ $\sqrt{\text{Hz}}$. With respect to a noise bandwidth of 20 kHz, this corresponds to an input noise of 42 nV, giving a signal to noise ratio with respect to an input signal of 150 nV

(0.15 mV) of 71 dB. At this level, the noise generated by the cartridge itself will be one of the dominant noise sources.

The circuit uses a symmetrical configuration with NPN and PNP transistors set up in such a way that asymmetrical distortions tend to cancel. Normally distortion products are generated differently for positive and negative signal excursions and this tends to produce second harmonic distortion products. The configuration used in this circuit results in very low second and third harmonic distortion. This has enabled a total harmonic distortion figure of around 0.0015% to be obtained.

The problem with quoting distortion figures of this order is that they are too low to be measured directly, being well hidden under the noise level. The only way a figure can be obtained is to remove the overall negative feedback, measure the distortion and then divide by the gain difference when the feedback is reapplied. Unfortunately, feedback does not affect all the distortion products equally, but the figure is still meaningful.

Another advantage of the symmetrical design of the input stage is that it does away with the need for an input capacitor. This is a definite advantage when dealing with low input impedances since the value of the capacitor would have had to be very large to obtain a flat frequency response at low frequencies.

The signal voltages present in the pre-amplifier are naturally extremely low and for this reason the power supply has been kept as a separate unit to reduce the possibility of 50 Hz induction from the power transformer.

A voltage regulator supplies the necessary ± 6 volts. As it is critical to achieve low noise it is important that the regulator does not put noise onto the supply rails which would degrade the noise performance of the unit. Normally the voltage reference used for regulators of this type is a zener diode but, as the zener is reverse biased, it generates a comparatively large amount of noise. In this design an LED was used as the voltage reference. A red LED operated in the forward-biased mode drops a constant 1.65 volts and generates very little noise.

Construction

Construction is relatively straightforward since most components are on the mounted pc board. Other construction methods are possible but performance may not match that of


our prototype.

Mount the resistors and capacitors first, followed by the transistors. Since there are quite a few transistors on the board placed close to each other, don't make the mistake I did and get them mixed up! Cut the necessary lengths of shielded cables and solder them onto the board keeping the ends as short as possible. Solder the necessary lengths of hookup cable to the board and after checking all components mount the board in the chassis.

I used a diecast aluminium box and quite frankly wish I hadn't. The shielding to external magnetic fields really isn't good enough. I found I had to be careful where the preamp was placed or it would pick up hum from the magnetic field produced by the power amp's transformer. Use a steel box if you can, if not, just be careful where it is placed.

Once the board is mounted in the chassis, the pots and rear panel hardware can be mounted and the wiring completed according to the wiring layout diagram shown. Here again I came unstuck. The first system I used to ground the shielded cables caused a monumental hum loop (and I still don't really understand why!). The final method tried is shown in the wiring diagram and this works very well. The shielded cables coming from the outputs on the board have only one of their shields connected to the output RCA sockets which are wired together and connected to the chassis at the ground terminal. This type of terminal is supplied with the necessary hardware to insulate them from the chassis. In this case however, we want the terminal to connect firmly to the case to provide the necessary ground connection. It is important that the RCA sockets be insulated from the case and that the ground connection made to them is according to the wiring diagram. If the unit is going to be used with the recommended power supply there should be no hum problems. This power supply, ETI 557, is described later in this issue. It is wired so that the 0 volt line is not connected to the chassis of the power supply. This is important, otherwise a hum loop around the units' mains grounds will result. If you wish to use a power supply other than the 577 then it will be necessary to ensure that the 0 volt line from the supply does not connect to the power supply chassis. Do not 'cure' the problem by disconnecting the ground wire at the 240 volt plug as this will remove any ground connection from the power

Project 473

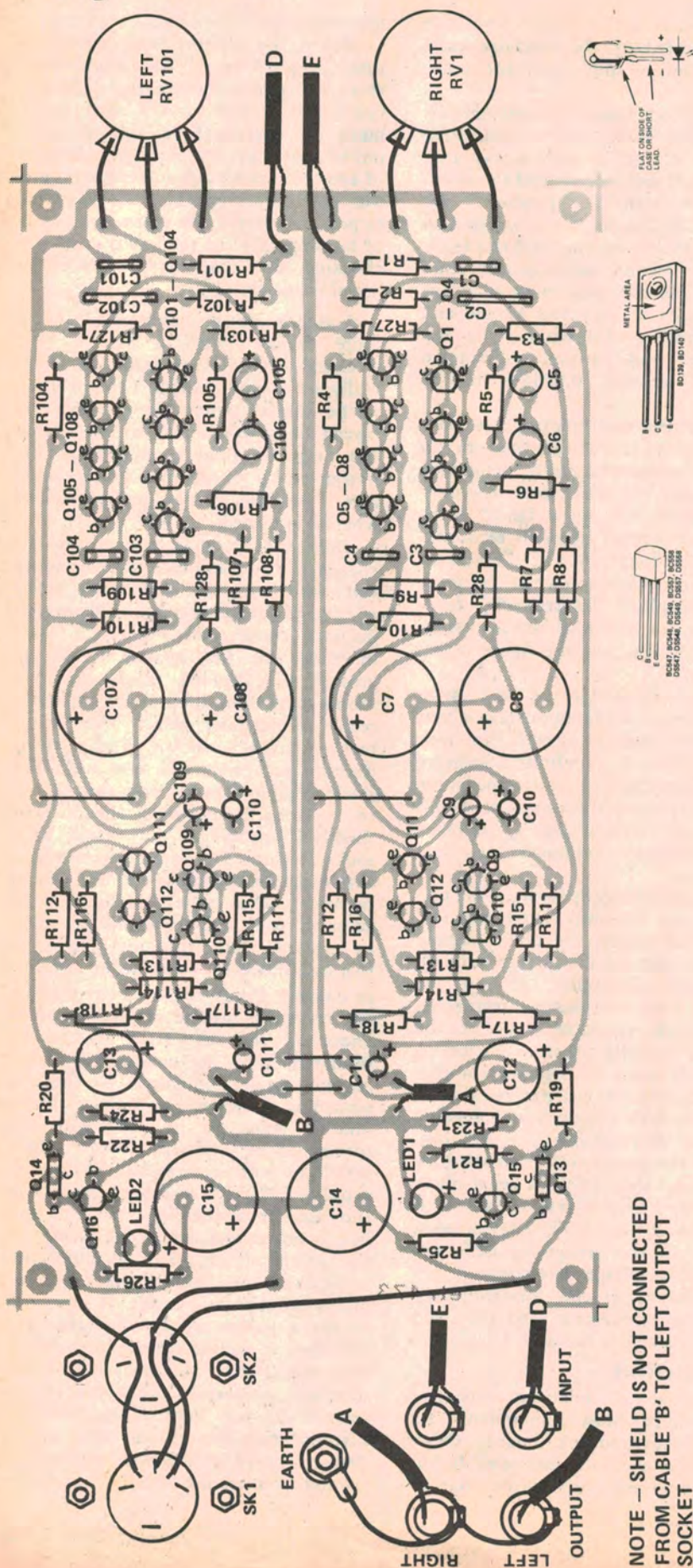

supply chassis. This is not only dangerous, it's illegal.

Powering up

Before turning the unit on make a final check of the board. Check the orientation of the transistors, electrolytic and tantalum capacitors and the LEDs. If all is right, turn down the volume control completely and switch the power supply on. The LEDs in the

PARTS LIST - ETI 473

Resistors

- all 1/2W, 5%
- R1, R101 . . . 3R3
 - R2, R102 . . . 10R
 - R3, R4, R103, R104 1k
 - R5, R6, R105, R106 2k2
 - R7, R8, R107, R108 10R
 - R9, R10, R109, R110 270R
 - R11, R12, R111, R112 . . 2k2
 - R13, R14, R113, R114 . . 10k
 - R15, R16, R115, R116 . . 390R
 - R17, R18, R117, R118 . . 18R
 - R19, R20 . . . 10R
 - R21, R22 . . . 560R
 - R23, R24 . . . 330R
 - R25, R26 . . . 220R
 - R27, R127 . . . 1k
 - R28, R128 . . . 220R

Capacitors

- C1, C101 3n3 ceramic
- C2, C102 4n7 ceramic
- C3, C4, C103, C104 470p ceramic
- C5, C6, C105, C106 22µF 16V tantalum
- C7, C8, C107, C108 2200µF 25V electro
- C9-C11, C109-C111 . . 10µF 16V tantalum
- C12, C13 100µF 25V electro
- C14, C15 1000µF 25V electro

Transistors

Use only types specified - substitutes may result in inferior performance.

- Q1-Q4, Q101-Q104 . . BC559
- Q5-Q8, Q105-Q108 . . BC549
- Q9, Q10, Q109, Q110 . . BC559
- Q11, Q12, Q111, Q112 . . BC549
- Q13 BD139
- Q14 BD140
- Q15 BC549
- Q16 BC559

LED1, LED2 . standard red LED


Potentiometers

- RV1, RV101 . 100R wirewound linear

Miscellaneous

- SK1, SK2 . . . 5 Pin DIN socket
- Four RCA sockets (insulated from case), One black terminal, mains lead, plug and mains cord securing grommet, two knobs, box to suit, 190 x 60 x 110 mm.


m.c. cartridge preamp

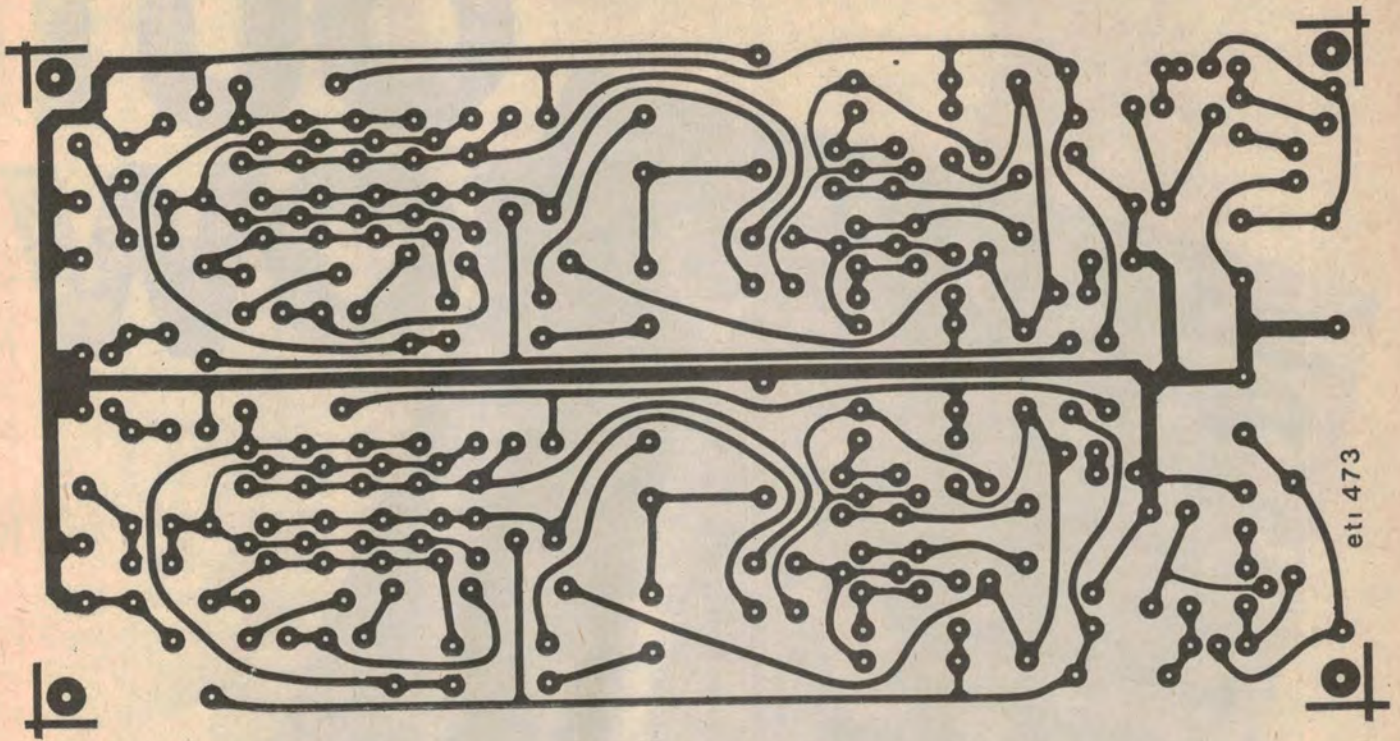

eti 473

preamp's regulator should come on immediately. I used standard RCA to RCA cables from the output of the preamp to the phono input and had some trouble with hum induction into the leads. Fortunately, we had been sent a set of Audio-Technica type AT620 cables for evaluation several days before and these cured the problem completely.

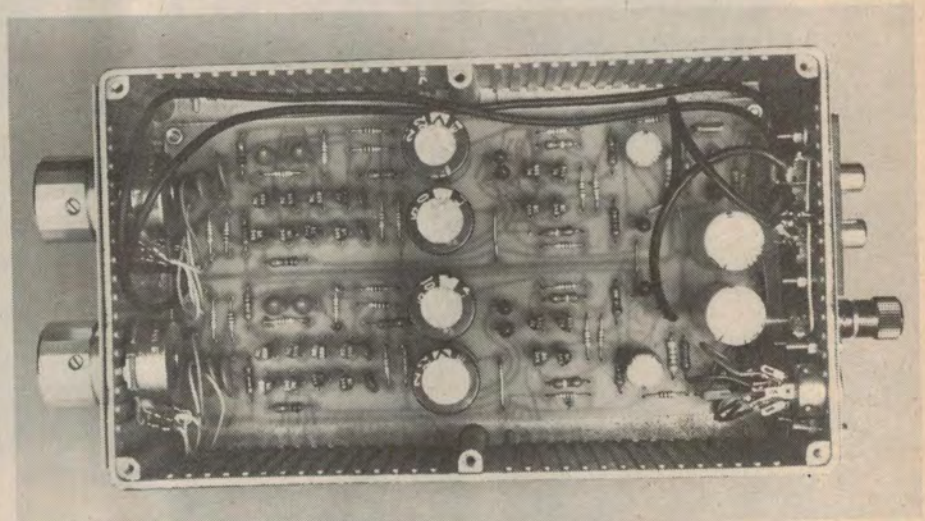Perhaps I am biased, but the sound quality of this preamp is extremely good! Using a Nakamichi MC1000 cartridge, this preamp showed distinct improvement over the transformer I was using previously. There is an openness that never existed before and the bass end showed a great improvement being firmer and much more defined. I trust you'll be as satisfied with your project as I have been.



series 4000 MOVING COIL CARTRIDGE PREAMPLIFIER

