

3/16/2018

Guide to Audio Engineering--Preamplifiers and Input Signals

Preamplifiers and Input Signals

1 Requirements

Most high-quality audio systems are required to operate from a variety of signal inputs, including radio tuners, cassette or reel-to-reel tape recorders, compact disc players, and more traditional record player systems. It is unlikely at the present time that there will be much agreement between the suppliers of these [ancillary](#) units on the standards of output impedance or signal voltage that their equipment should offer.

Except where a manufacturer has assembled a group of such units, for which the interconnections are custom designed and there is in-house agreement on signal and impedance levels-and, sadly, such ready-made groupings of units seldom offer the highest overall sound quality [available](#) at any given time-both the designer and the user of the power amplifier are confronted with the need to ensure that their system is capable of working satisfactorily from all of these likely inputs.

For this reason, it is [conventional](#) practice to interpose a versatile preamplifier unit between the

power amplifier and the external signal sources to perform the input signal switching and signal level adjustment functions.

This preamplifier either forms an integral part of the main power amplifier unit or, as is more common with the higher quality units, is a free-standing, separately powered unit.

2 Signal Voltage and Impedance Levels

Many different conventions exist for the output impedances and signal levels given by ancillary units. For tuners and cassette recorders, the output is either that of the German Deutsches Industrie Normal (DIN) standard, in which the unit is designed as a current source, which gives an output voltage of 1 mV for each 1000 ohms of load impedance, such that a unit with a 100-K input impedance would see an input signal voltage of 100 mV, or the line output standard, designed to drive a load of 600 ohms or greater, at a mean signal level of 0.775 V rms, often referred to in tape recorder terminology as OVU.

Generally, but not invariably, units having DIN type interconnections, of the styles shown in FIG. 1 , will conform to the DIN signal and impedance level [convention](#), whereas those having " phono " plug/socket outputs, of the form shown in FIG. 2 , will not. In this case, the permissible minimum load impedance will be within the range 600 to 10,000 ohms, and the mean output signal level will commonly be within the range 0.25-1 V rms.

An exception to this exists regarding compact disc players, where the output level is most commonly 2 V rms.

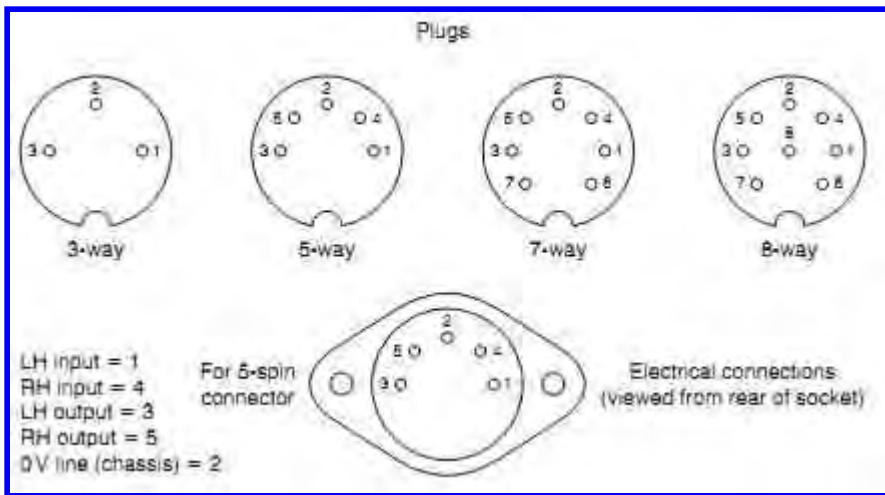


FIG. 1: Common DIN connector configurations.

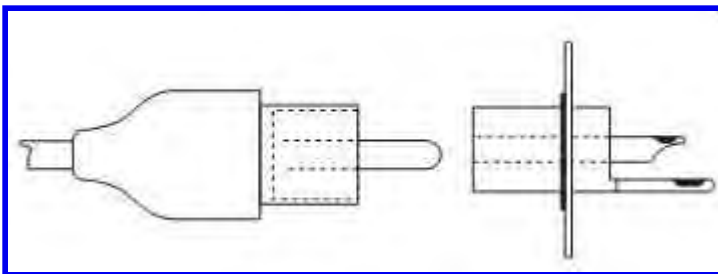


FIG. 2: The phono connector.

3 Gramophone (phono) Pick-Up Inputs

Three broad categories of pick-up (PU) cartridges exist: the ceramic, the moving magnet or variable reluctance, and the moving coil. Each of these has different output [characteristics](#) and load requirements.

3.1 Ceramic Piezo-Electric Cartridges

These units operate by causing the movement of the stylus due to groove modulation to flex a resiliently mounted strip of piezo-electric ceramic, which then causes an electrical voltage to be developed across metallic contacts bonded to the surface of the strip. They are commonly found only on low-cost units and have a relatively high output signal level, in the range 100-200 mV at 1 kHz.

Generally, the electromechanical characteristics of these cartridges are tailored so that they give a fairly flat frequency response, although with some unavoidable loss of HF response beyond 2 kHz, when fed into a preamplifier input load of 47,000 ohms.

Neither the HF response nor the tracking characteristics of ceramic cartridges are particularly good, although circuitry has been designed with the specific aim of optimizing the performance obtainable from these units.

However, in recent years, the continuing development of PU cartridges has resulted in a substantial fall in the price of the less exotic moving magnet or variable reluctance types so that it no longer makes economic sense to use ceramic cartridges, except where their low cost and robust nature are of importance.

3.2 Moving Magnet and Variable Reluctance Cartridges

These are substantially identical in their performance characteristics and are designed to operate into a 47-K load impedance, in parallel with some 200-500 pF of anticipated lead capacitance. Since it is probable that the actual capacitance of the connecting leads will only be of the order of 50-100 pF, some [additional](#) input capacitance, connected across the phono input socket, is customary. This also will help reduce the probability of unwanted radio signal breakthrough.

PU cartridges of this type will give an output voltage that increases with frequency in the manner shown in FIG. 3(a) , following the velocity characteristics to

which LP records are produced, in conformity with the Recording Industry Association of [America](#) (RIAA) recording standards. The preamplifier will then be required to have a gain/frequency [characteristic](#) of the form shown in FIG. 3(b) , with the deemphasis time constants of 3180, 318, and 75 μ s, as indicated in the figure.

The output levels produced by such PU cartridges will be of the order of 0.8-2 mV/cm/s of groove modulation velocity, giving typical mean outputs in the range of 3-10 mV at 1 kHz.

3.3 Moving Coil Pick-Up Cartridges

These low-impedance, low-output PU cartridges have been manufactured and used without particular comment for very many years. They have come into considerable prominence in the past decade because of their superior transient characteristics and dynamic range as the choice of those audiophiles who seek the ultimate in sound quality, even though their tracking characteristics are often less good than is normal for MM and variable reluctance types.

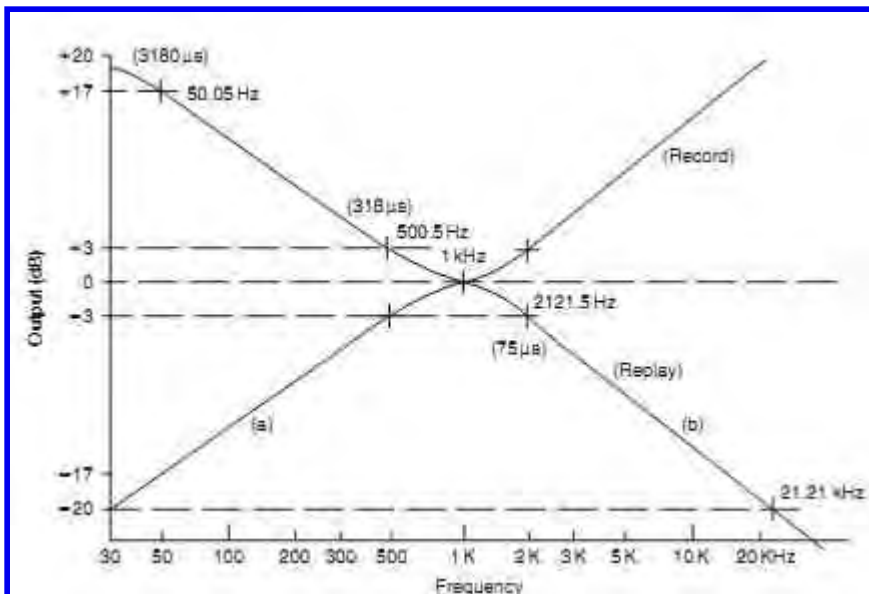


FIG. 3: The RIAA record/replay characteristics used for 33/45 rpm vinyl discs.

Typical signal output levels from these cartridges will be in the range 0.02-0.2 mV/cm/s into a 50- to 75-ohm load impedance. Normally, a very low-noise head [amplifier circuit](#) will be required to increase this signal voltage to a level acceptable at the input of the RIAA equalization circuitry, although some of the high output types will be capable of operating directly into the high-level RIAA input. Such cartridges will generally be designed to operate with a 47-K load impedance.

4 Input Circuitry

Most of the inputs to the preamplifier will merely require [appropriate amplification](#) and impedance transformation to match the signal and impedance levels of the source to those required at the input of the power amplifier. However, the necessary equalization of the input frequency response from a moving magnet, moving coil, or variable reluctance PU cartridge, when replaying an RIAA

preemphasized vinyl disc, requires special frequency shaping networks.

Various circuit layouts have been employed in the preamplifier to generate the required

RIAA replay curve for velocity sensitive PU transducers, and these are shown in FIG. 4 . Of these circuits, the two simplest are the " passive " equalization networks shown in

FIGs. 4(a) and 7.4(b) , although for accuracy in frequency response they require that the source impedance is very low and that the load impedance is very high in relation to R_1 .

The required component values for these networks have been derived by Livy 2

in terms of RC time constants and set out in a more easily applicable form by Baxandall 3 in his [analysis](#) of the various possible equalization circuit arrangements.

From the equations quoted, the component values required for use in the circuits of

FIGs. 4(a) and 7.4(c) would be $R_1 R_2 C_1 C_2 = 12 \times 11 \times 22 \times 6$
 $818 \times 2187 \times 109 / \text{s}$ and $s \text{ --- } \cdot \text{ --- } \mu\mu$

For the circuit layouts shown in FIGs. 4(b) and 7.4(d) , the component values can be derived from the relationships: $R_1 R_2 C_1 C_2 = 12 \times 11 \times 22 \times 12 \times 38 \times 2937 \times 81 \times 1$
 $/\text{s}$ and $s \text{ --- } \cdot \text{ --- } \mu\mu$

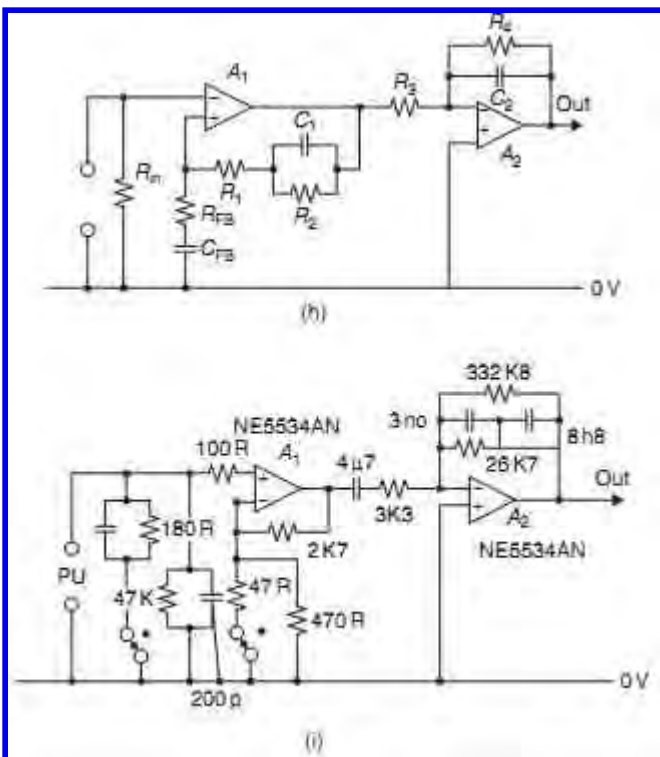
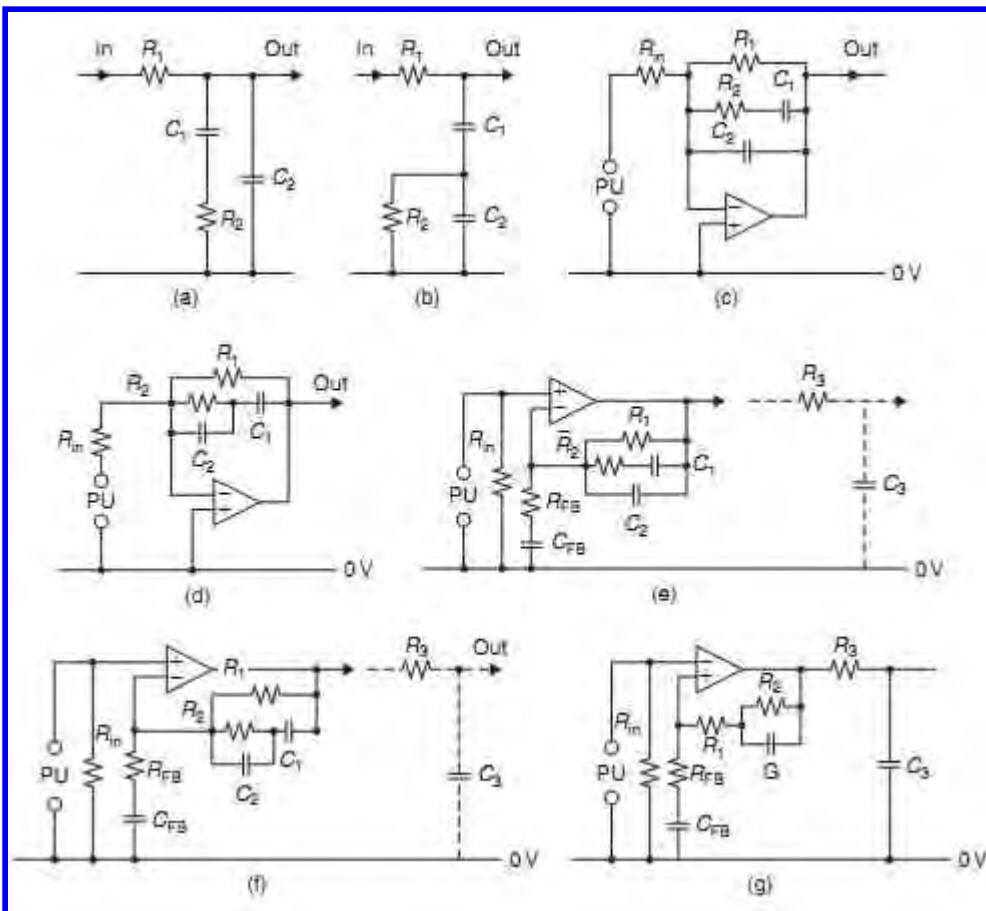


FIG. 4: Circuit layouts that will generate the type of frequency response required for RIAA input equalization.

The circuit arrangements shown in FIGs. 4(c) and 4(d) use "shunt" type negative feedback (i.e., that type in which the negative feedback signal is applied to the amplifier in parallel with the input signal) connected around an internal gain block.

These layouts do not suffer from the same limitations with respect to source or load as the simple passive equalization systems of FIGs. 4(a) and 4(b) .

However, they do have the practical snag that the value of R_{in} will be determined by the required PU input load resistor (usually 47k for a typical moving magnet or variable reluctance type of PU cartridge), and this sets an input " resistor noise " threshold, which is higher than desirable, as well as requiring inconveniently high values for R_1 and R_2 .

For these reasons, the circuit arrangements shown in FIGs. 4(e) and 7.4(f) are found much more commonly in commercial audio circuitry. In these layouts, the frequency response shaping components are contained within a "series" type feedback network (i.e., one in which the negative feedback signal is connected to the amplifier in series with the input signal), which means that the input circuit impedance seen by the amplifier is essentially that of the PU coil alone and allows a lower midrange " thermal noise " background level.

The snag, in this case, is that at very high frequencies, where the impedance of the frequency-shaping feedback network is small in relation to R_{FB} , the circuit gain approaches unity, whereas both the RIAA specification and the accurate reproduction of transient waveforms require that the gain should asymptote to zero at higher audio frequencies.

This error in the shape of the upper half of the response curve can be remedied by the addition of a further CR network, $C3 / R3$, on the output of the equalization circuit, as shown in FIGs. 4(e) and 4(f) . This amendment is sometimes found in the circuit designs used by the more perfectionist of the audio amplifier manufacturers.

Other approaches to the problem of combining low input noise levels with accurate replay equalization are to divide the equalization circuit into two parts, in which the first part, which can be based on a low noise series feedback layout, is only required to shape the 20-Hz to 1-kHz section of the response curve. This can then be followed by either a simple passive RC roll-off network, as shown in FIG. 4(g) , or by some other circuit arrangement having a similar effect, such as that based on the use of a shunt feedback connected around an inverting amplifier stage, as shown in FIG. 4(h), to generate that part of the response curve lying between 1 kHz and 20 kHz.

A further arrangement, which has attracted the interest of some Japanese circuit designers-as used, for example, in the Rotel RC-870BX preamp, of which the RIAA equalizing circuit is shown in a simplified form in FIG. 4 -simply employs one of the recently developed very low noise IC op-amps as a flat frequency response input buffer stage. This is used to amplify the input signal to a level at which circuit noise introduced by succeeding stages will only be a minor problem and also to convert the PU input impedance level to a value at which a straightforward shunt feedback equalizing circuit can be used, with resistor values chosen to minimize any

thermal noise background rather than being dictated by the PU load requirements.

The use of " application-specific " audio ICs, to reduce the cost and component count of RIAA stages and other circuit functions, has become much less popular among the designers of higher quality audio equipment because of the tendency of the semiconductor manufacturers to discontinue the supply of such specialized ICs when the economic basis of their sales becomes unsatisfactory or to replace these devices by other, notionally equivalent, ICs that are not necessarily either pin or circuit function compatible.

There is now, however, a degree of unanimity among the suppliers of ICs as to the pin layout and operating conditions of the single and dual op-amp designs, commonly packaged in eight-pin dual-in-line forms. These are typified by the Texas Instruments TL071 and TL072 ICs or their more recent equivalents, such as the TL051 and TL052 devices; there is a growing tendency for circuit designers to base their circuits on the use of ICs of this type, and it is assumed that devices of this kind would be used in the circuits shown in FIG. 4 .

An incidental advantage of the choice of this style of IC is that commercial rivalry between semiconductor manufacturers leads to continuous improvements in the specification of these devices. Since these nearly always offer plug-in physical and electrical interchangeability, the performance of existing equipment can be upgraded easily, either on the production line or by the service department, by the replacement of existing op-amp ICs with those of a

5 Moving Coil Pick-up Head Amplifier Design

The design of preamplifier input circuitry that will accept the very low signal levels associated with moving coil PUs presents special problems in attaining an adequately high signal-to-noise ratio, in respect to the microvolt level input signals, and in minimizing the intrusion of mains hum or unwanted radio frequency (RF) signals.

The problem of circuit noise is lessened somewhat with respect of such RIAA-equalized amplifier stages in that, because of the shape of the frequency response curve, the effective bandwidth of the amplifier is only about 800 Hz. The thermal noise due to amplifier input impedance, which is defined by the following equation, is proportional to the squared measurement bandwidth, other things being equal, so that the noise due to such a stage is less than would have been the case for a flat frequency response system.

Nevertheless, the attainment of an adequate S/N ratio, which should be at least 60 dB, demands that the input circuit impedance should not exceed some 50 ohms.

$V_{KTFR} _ 4 d$

...where dF is the bandwidth, T is the absolute temperature (room temperature being approximately $300^{\circ}K$), R is resistance in ohms,

and K is Boltzmann's constant (1.38×10^{-23}).

The moving coil PU cartridges themselves will normally have winding resistances that are only of the order of 5-25 ohms, except in the case of the high output units where the problem is less acute anyway, so the problem relates almost exclusively to the circuit impedance of the MC input circuitry and the semiconductor devices used in it.

6 Circuit Arrangements

Five different approaches are in common use for moving coil PU input [amplification](#).

6.1 Step-Up Transformer

This was the earliest method to be explored and was advocated by Ortofon, which was one of the pioneering companies in the manufacture of MC PU [designs](#). The advantage of this system is that it is substantially noiseless, in the sense that the only source of wide-band noise will be the circuit impedance of the transformer windings and that the output voltage can be high enough to minimize the thermal noise contribution from succeeding stages.

The principal disadvantages with transformer step-up systems, when these are operated at very low signal levels, are their proneness to mains "hum" pick up, even when well shrouded, and their somewhat less good handling of "transients" because of the effects of stray capacitances and leakage inductance. Care in their design is also needed to overcome the magnetic nonlinearities associated with the core, which are particularly significant at low signal levels.

6.2 Systems Using Paralleled Input Transistors

The need for a very low input circuit impedance to minimize thermal noise effects has been met in a number of commercial designs by simply connecting a number of small signal transistors in parallel to reduce their effective base-emitter circuit resistance.

Designs of this type came from Ortofon, Linn/Naim, and Braithwaite and are shown in FIGs. 5-7 .

If such small signal transistors are used without selection and matching-a time consuming and expensive process for any commercial manufacturer-some means must be adopted to minimize the effects of the variation in base-emitter turn-on voltage that exist between nominally identical devices because of variations in the doping level in the silicon crystal slice or to other differences in manufacture.

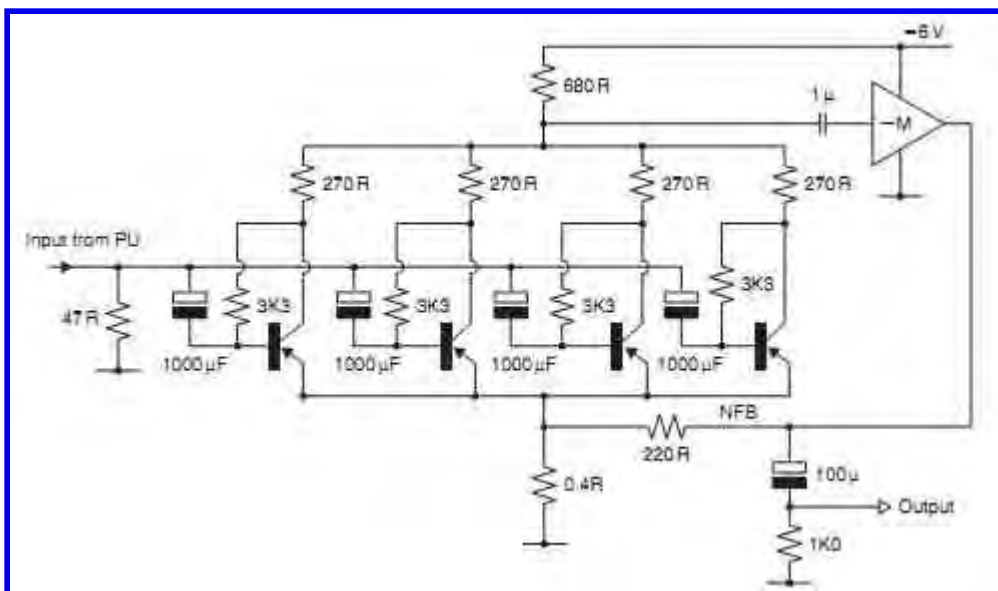


FIG. 5: Ortofon MCA-76 head amplifier.

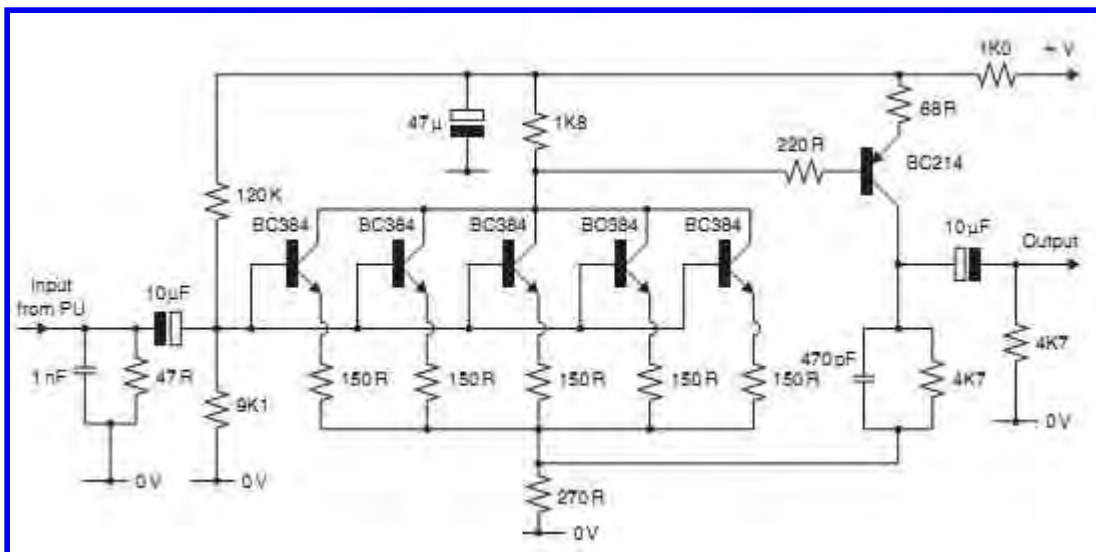


FIG. 6: The Naim NAC 20 moving coil head amplifier.

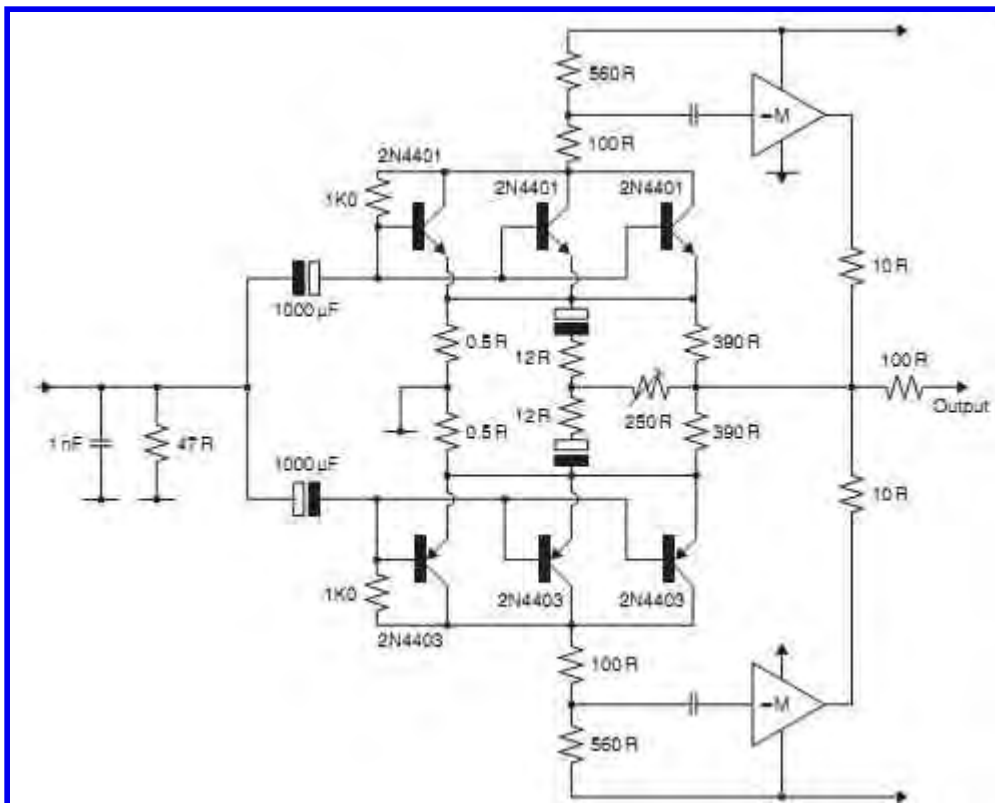


FIG. 7: Braithwaite RA14 head amplifier. (The output stage is shown in a simplified form.)

This is achieved in the Ortofon circuit by individual collector-base bias current networks, for which the penalty is the loss of some usable signal in the collector circuit. In the Linn/Naim and Braithwaite designs, this evening out of transistor [characteristics](#) in circuits having common base connections is achieved by the use of individual emitter resistors to swamp such differences in device characteristics. In this case, the penalty is that such resistors add to the base-emitter circuit impedance when the task of the design is to reduce this.

6.3 Monolithic Super-Matched Input Devices

An alternative method of reducing the input circuit impedance, without the need for separate bias systems or emitter circuit-swamping resistors, is to employ a monolithic (integrated circuit type) device in which a multiplicity of transistors has been simultaneously formed on the same silicon chip. Since these can be assumed to have virtually identical characteristics, they can be paralleled, at the time of manufacture, to give a very low impedance, low noise, matched pair.

An example of this approach is the National Semiconductors LM 194/394 super-match pair, for which a suitable circuit is shown in FIG. 8. This input device probably offers the best input noise performance currently [available](#), but is relatively expensive.

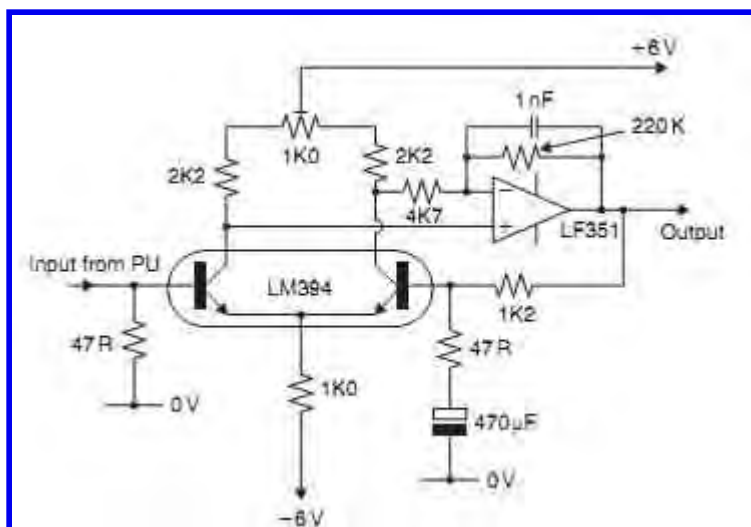


FIG. 8: Head amplifier using a LM394 multiple transistor array.

6.4 Small Power Transistors as Input Devices

The base-emitter impedance of a transistor depends largely on the size of the junction area on the silicon chip. This will be larger in power transistors than in small signal transistors, which mainly employ relatively small chip sizes. Unfortunately, the current gain of power transistors tends to decrease at low collector current levels, making them unsuitable for this [application](#).

However, use of the plastic encapsulated medium power (3-4A I_c max.) styles, in T0126, T0127, and T0220 packages, at collector currents in the range of 1-3 mA, [achieves](#) a satisfactory compromise between input circuit impedance and transistor performance and allows the design of very linear low-noise circuitry. Two [examples](#) of MC head amplifier designs of this type, by the author, are shown in FIGs. 9 and 10 .

The penalty in this case is that, because such transistor types are not specified for low noise operation, some preliminary selection of the devices is desirable, although, in the writer's experience, the bulk of

the devices of the types shown will be found to be satisfactory in this respect.

In the circuit shown in FIG. 9 , the input device is used in the common base (cascode) [configuration](#) so that the input current generated by the PU cartridge is transferred directly to the higher impedance point at the collector of this transistor so that the stage gain, prior to the application of negative feedback to the input transistor base, is simply the impedance transformation due to the input device.

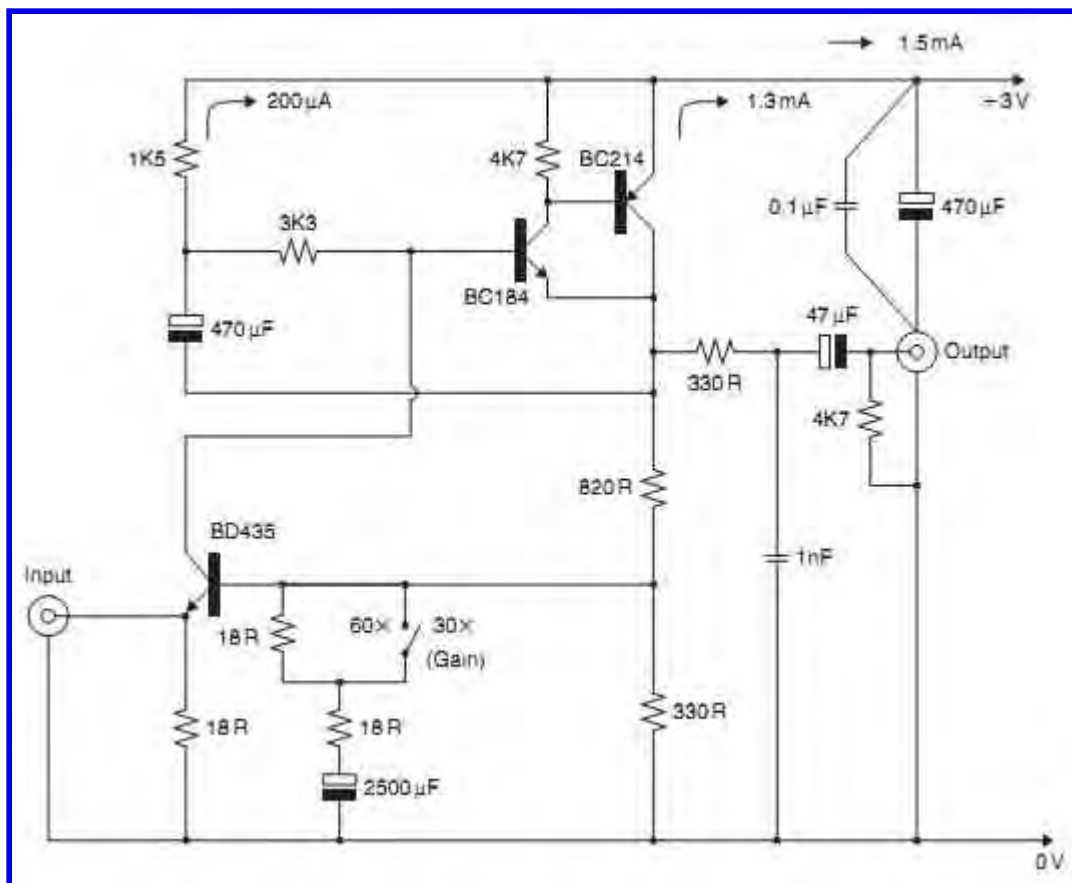


FIG. 9: Cascode input moving coil head amplifier.

The penalty in this case is that, because such transistor types are not specified for low noise operation, some preliminary selection of the devices is desirable, although, in the writer's experience, the bulk of the devices of the types shown will be found to be satisfactory in this respect.

In the circuit shown in FIG. 9 , the input device is used in the common base (cascode) configuration so that the input current generated by

the PU cartridge is transferred directly to the higher impedance point at the collector of this transistor so that the stage gain, prior to the application of negative feedback to the input transistor base, is simply the impedance transformation due to the input device.

In the circuit of FIG. 10 , the input transistors are used in a more [conventional](#) common-emitter mode, but the two input devices, although in a push-pull configuration, are effectively connected in parallel so far as the input impedance and noise figure are concerned. The very high degree of symmetry of this circuit assists in minimizing both harmonic and transient distortions.

Both of these circuits are designed to operate from 3-V DC "pen cell" battery supplies to avoid the introduction of mains hum due to the power supply circuitry or to earth loop effects. In mains-powered head [amps](#), great care is always necessary to avoid supply line signal or noise intrusions in view of the very low signal levels at both the inputs and the outputs of the amplifier stage.

It is also particularly advisable to design such amplifiers with single point "0-V " line and supply line connections, which should be coupled by a suitable combination of good quality decoupling capacitors.

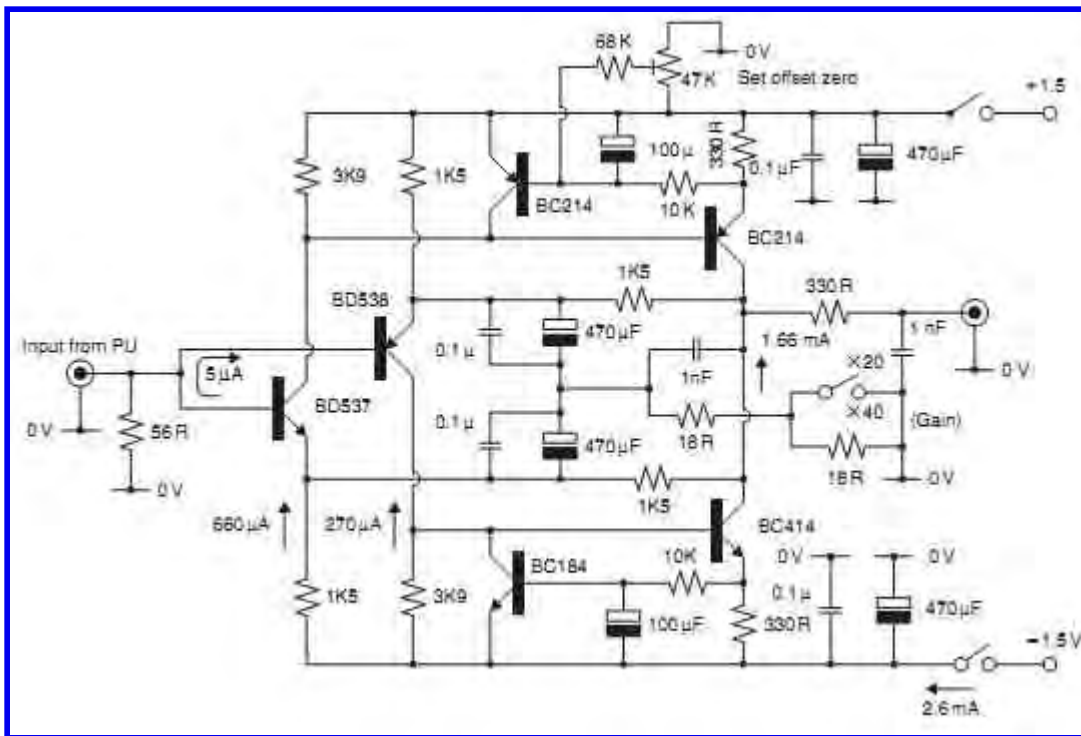


FIG. 10: Very low-noise, low-distortion, symmetrical MC head amplifier.

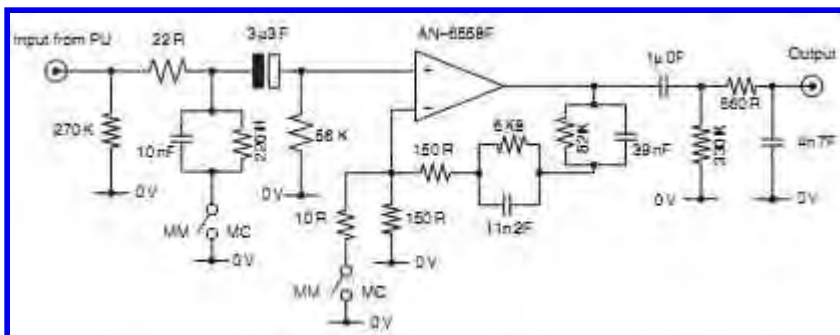


FIG. 11: Moving coil/moving magnet RIAA input stage in a Technics SU-V10 amplifier.

6.5 Very Low Noise IC Op-Amps

The development, some years ago, of very low noise IC operational amplifiers, such as the Precision Monolithics OP-27 and OP-37 devices, has led to the proliferation of very high-quality, low-noise, low-distortion ICs aimed specifically at the audio market, such as the Signetics NE-5532/ 5534, the NS LM833, the PMI SSM2134/2139, and the TI TL051/052 devices.

With ICs of this type, it is a simple matter to design a conventional RIAA input stage in which the provision of a high-sensitivity, low-

noise, moving coil PU input is accomplished by simply reducing the value of the input load resistor and increasing the gain of the RIAA stage in comparison with that needed for higher output PU types. An example of a typical Japanese design of this type is shown in FIG. 11 .

6.6 Other Approaches

A very ingenious, fully symmetrical circuit arrangement that allows the use of normal circuit layouts and components in ultralow noise (e.g., moving coil PU and similar signal level) inputs has been introduced by "Quad" (Quad Electroacoustics Ltd.) and is employed in all their current series of preamps. This exploits the fact that, at low input signal levels, bipolar junction transistors will operate quite satisfactorily with their base and collector junctions at the same DC potential and permits the type of input circuit shown in FIG. 12 .

In the particular circuit shown, that used in the " Quad 44 " disc input, a two-stage equalization layout is employed, using the type of structure illustrated in FIG. 4(g) , with the gain of the second stage amplifier (a TL071 IC op-amp) switchable to suit the type of input signal level available.