

NEW IDEAS

Automobile locator

HAVE YOU EVER HAD TROUBLE FINDING your car in a crowded parking lot? If so, here's a device that will be of some help.

This automobile locator is made up of two parts. The first is an RF oscillator, whose circuit is shown in Fig. 1. The second is a sensitive receiver; that circuit is shown in Fig. 2.

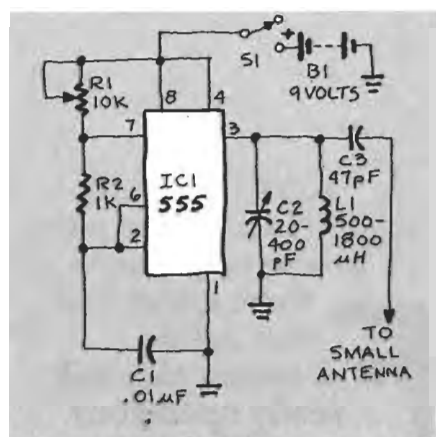


FIG. 1

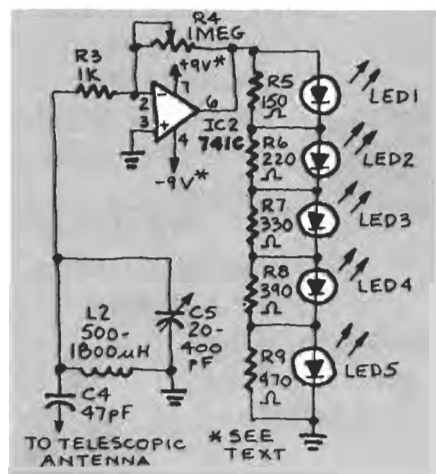


FIG. 2

The heart of the oscillator is a 555 timer IC. Its frequency—just below the AM broadcast-band—is determined by R1, R2, and C1. A tank circuit (C2 and L1) is used to tune the transmitter. The antenna is coupled to the transmitter through C3. Since efficiency is not very important here (output power should be kept under 100 mW), the length of the antenna can be kept short.

A telescopic antenna or a length of hookup wire will work quite well. The only thing that is important is that the antenna be vertically polarized.

At the receiver, the incoming signal is tuned by C5 and L2 before being passed on to the 741 IC. That IC amplifies the signal up to 1000 times; the amount of amplification is controlled by adjusting R4, a linear-taper potentiometer (more on that later). The five LED's are used to indicate signal strength, they light up in order (1 to 5) as the signal gets stronger.

The 741 requires two 9-volt batteries for power. The positive terminal of one battery is connected to pin 7. The negative terminal of the other battery is connected to pin 4. The remaining terminals (one positive and one negative) are connected together and grounded.

Keep in mind that you will be carrying the receiver with you as you go about your business, so it should be installed in a case that is as small as possible.

After the devices are built, the receiver and transmitter will need to be tuned. Once that is done, however, you should not need to do it again unless the settings are tampered with. Placing the transmitter and receiver next to each other, detune the receiver so that none of the LED's light. Then tune the transmitter until all of the receiver's LED's light, indicating maximum signal strength. Potentiometer R4 should be adjusted for the minimum amplification that will give you a usable signal. Too much amplification will give you a maximum-strength indication over too wide a range. Separate the receiver and the transmitter (the farther apart they are the better) and adjust R4 until you get a maximum strength reading only when the receiver's antenna is pointed directly at the transmitter. The RF locator is now ready for use.

Since the locator will not be able to work through the metal body of your car, you will need to set up the transmitter so that the signal can radiate through a glassed-in area. That is really not much of a problem. If you are using a hook-up-wire antenna, simply tape the free end to the top of either the front or rear windshield. If you're using a telescopic antenna, place the trans-

mitter on the dashboard and extend the antenna so that it is as long as possible. In either case remember to switch the transmitter on before you leave, and remember that the antenna should be aligned vertically for best results.

To find your car, just extend the telescopic antenna of the receiver to its full length and hold it parallel to the ground. Point the antenna to your far left, then swing it to your far right. Do that until you find in which direction the strongest signal lies, as indicated by the LED's. The antenna will be pointing at your car.—Doug Krause

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, Panavise will donate their model 324 Electronic Work Center, having a value of \$49.95. It combines their circuit-board holder, tray base mount, and solder station. Selections will be made at the sole discretion of the editorial staff of **Radio-Electronics**.

I agree to the above terms, and grant **Radio-Electronics** Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State

ZIP

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,
200 Park Ave. South,
New York, NY 10003

AUTOMOBILE LOCATER

In reference to the automobile locator ("New Ideas," **Radio-Electronics**, April 1982), I would like to offer the following comments. I tried the above-mentioned circuit myself, and a few of my friends experimented with it, too. We all reached the same conclusion: When R1 is set to 10K, the frequency output is 12 kHz. With the 10K pot set at 0, although the IC timer 555 had a tendency to heat up, the operating frequency was 72 kHz. The tuning range of the output tank with a 20-pF to 400-pF capacitor and 500 μ H to 1800 μ H coil is between 188 kHz to 1.59 MHz. With an 1800 μ H coil and 20-400-pF variable capacitor, the tuning range is 188 kHz – 839 kHz. Now there is a problem with the IC timer output of 12 kHz to 72 kHz, which falls below the tuning range of the author's circuit.

Also, I see a problem with the antenna-coupling capacitor of 47-pF with the IC timer output of 12 kHz. The capacitance reactance of the coupling capacitor is 282K ohms and with 72 kHz, $X_c = 47K$. Obviously, it will attenuate the signal transmission.

We found the following modifications appropriate: Capacitor C1 should be dropped to .001 μ F, and that will give an operating range of 120 kHz to 481 kHz. The tuning range of the output tank with 13-pF to 365-pF variable capacitor and 1800 μ H coil is from 196 kHz to 1.04 MHz; the capacitive reactance has also markedly decreased.

Please note the following manufacturer's data on the open-loop gain of the 741 operational amplifier:

1 KHz = 1000 or 60 db;

10 KHz = 100 or 40 db;

100 KHz = 10 or 20 db,

1000 KHz = 1 or 0 db.

As you see from the above data, there is a serious attenuation of the received signal as the transmitter frequency increases.

MOHINDER S. GOOMAR, M.D., F.R.C.S.

Saratoga Springs, NY

R-E