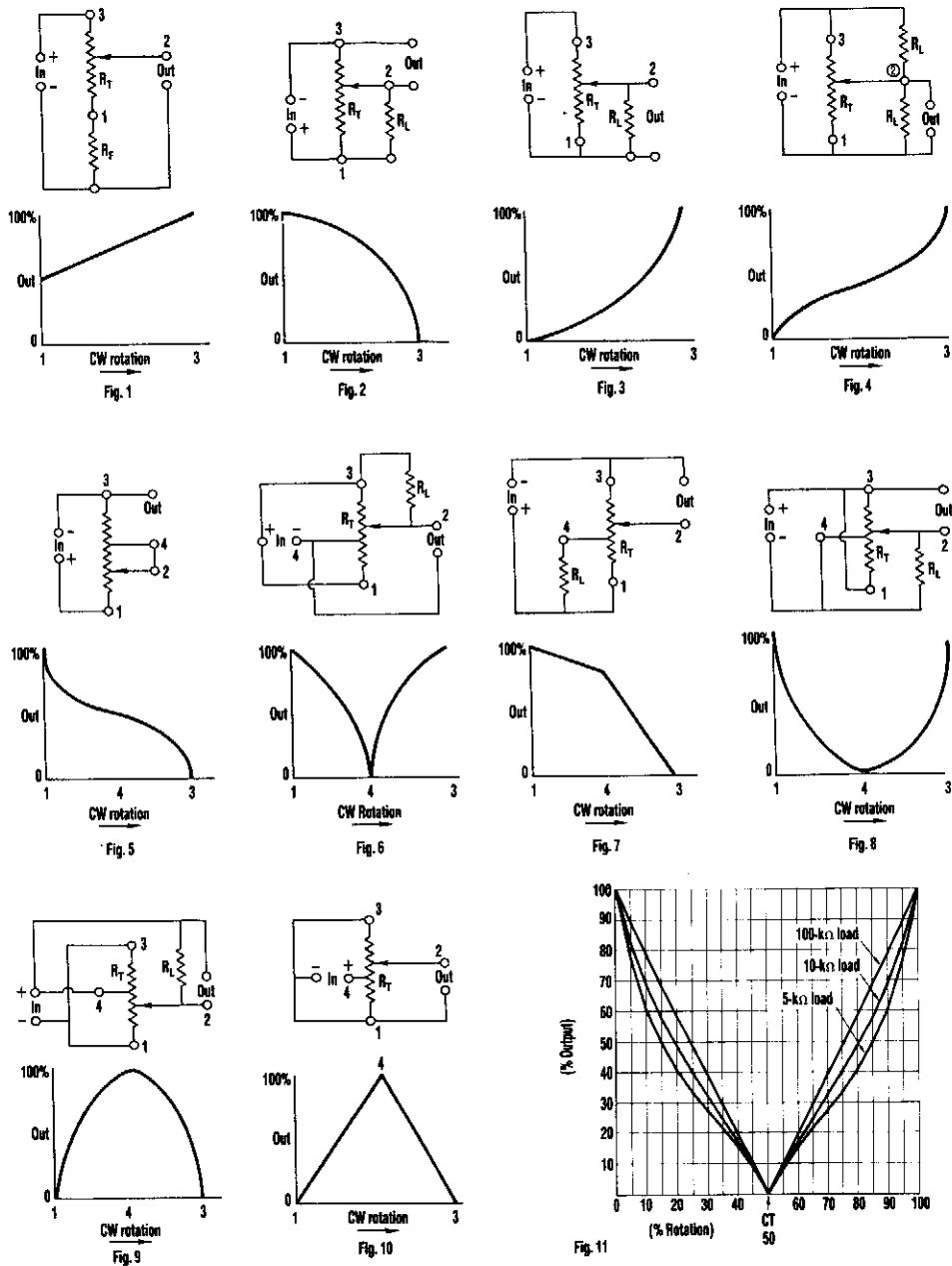


## NONLINEAR POTENTIOMETER OUTPUTS



ELECTRONIC DESIGN

Fig. 34-2

Using these illustrated configurations, various rotation output characteristics can be obtained from potentiometers and one or two resistors.