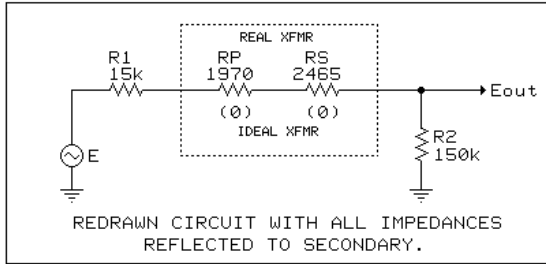
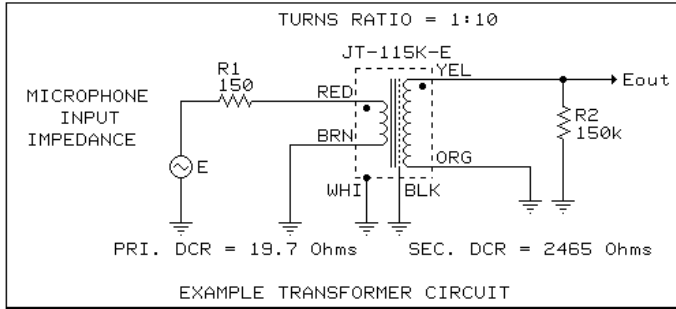


# HOW TO CALCULATE TRANSFORMER RELATED NOISE FIGURE



PRIMARY SIDE IMPEDANCES GET MULTIPLIED BY THE SQUARE OF THE TURNS RATIO.

- 1)  $R1 = 150 \text{ Ohms} \times (10)^2 = 15k$
- 2)  $RP = 19.7 \text{ Ohms} \times (10)^2 = 1970$
- 3)  $RS = \text{SECONDARY DCR} = 2465$
- 4)  $R2 = 150k \text{ (LOAD)}$

3) TOTAL NF = 1.01dB + 0.232dB = 1.233dB

THE TRANSFORMER NOISE FIGURE IS CALCULATED BY COMPARING A REAL TRANSFORMER WITH ITS WINDING RESISTANCES TO AN IDEAL TRANSFORMER WITH NO WINDING RESISTANCES.

FIRST, TRANSFORM ALL IMPEDANCES TO THE SECONDARY AS SHOWN TO THE LEFT.

THERE ARE TWO COMPONENTS TO THE CALCULATION:

1) THE ADDITIONAL NOISE DUE TO THE INCREASED OUTPUT IMPEDANCE.

$$\text{REAL } Z_{out} = \frac{150k \times (15k + 1970 + 2465)}{150k + 15k + 1970 + 2465} = 17k206$$

$$\text{IDEAL } Z_{out} = \frac{150k \times 15k}{150k + 15k} = 13k636$$

$$NF = 20 \text{ Log} \sqrt{\frac{17k206 \text{ (REAL)}}{13k636 \text{ (IDEAL)}}} = 1.01\text{dB}$$

2) THE DECREASE IN SIGNAL LEVEL AT THE OUTPUT DUE TO THE INCREASED SERIES LOSSES.

$$\text{IDEAL } E_{out} = \frac{150k}{150k + 15k} = 0.909$$

$$\text{REAL } E_{out} = \frac{150k}{150k + 15k + 1970 + 2465} = 0.885$$

$$NF = 20 \text{ Log} \frac{0.909 \text{ (IDEAL)}}{0.885 \text{ (REAL)}} = 0.232\text{dB}$$

**jensen**

AS040

11/21/96

7135 HAYVENHURST AVE.  
VAN NUYS, CALIFORNIA 91406  
(818) 374-5857